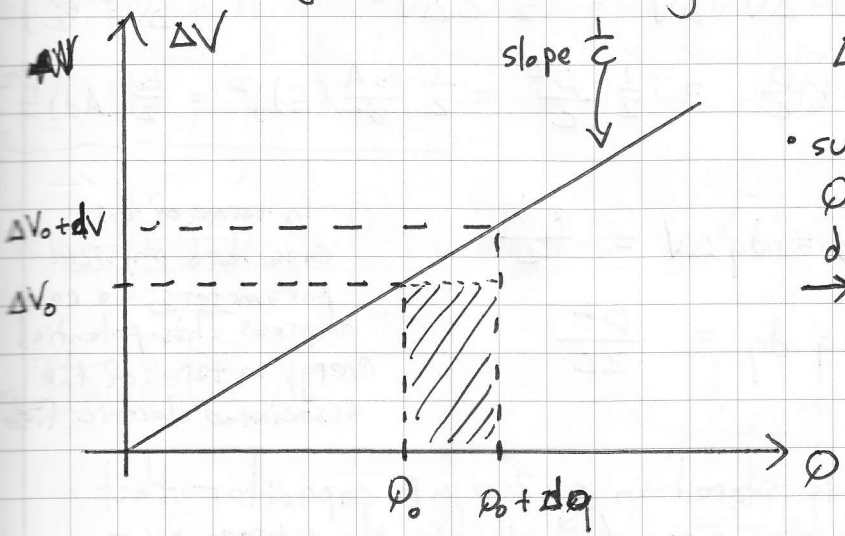


Energy Storage in Capacitors

- Imagine two (initially uncharged) parallel plates and we start moving electrons from one plate to the other.
- This will set up an electric field and we will need to increasingly do more and more work to get those electrons across
- Thus, the plates (i.e. a parallel-plate capacitor) is essentially storing up the energy that we did work on to move those charges to create the electric field
 → analogous to compressing a spring!



$$\Delta V = \frac{1}{C} Q$$

- suppose the plates have charge Q_0 and thereby a potential difference ΔV_0 .
- How much energy is required to charge up the capacitor by an extra amount of charge dq ?

→ essentially we have to move charge dq across the plates through the electric field $E = \Delta V_0/d$

Since $U = qV$, the $\Delta U \approx dq \Delta V_0$

↑ change in potential energy

↑ only approx. unless dq is small!

↑ area of shaded rectangle

NOTE: Unless dq is small, we neglect the triangle!

11/23/13

- So the change in energy is ΔU , that is we did work to move dq such that the capacitor changes its potential from ΔV_0 to $\Delta V_0 + dV$ (i.e. the capacitor stored the energy ΔU)
- So we could add up all the contributions along these lines, which essentially means determining the area under the ΔV vs. Q curve (just a simple triangle!)

$$\begin{aligned}
 U_{\text{capacitor}} &= \frac{1}{2} Q \cdot \Delta V_0 \rightarrow \frac{1}{2} Q \Delta V \\
 &= \frac{1}{2} C \cdot \Delta V \cdot \Delta V = \frac{1}{2} C \Delta V^2 \quad (\text{since } \Delta V = \frac{Q}{C}) \\
 &= \frac{1}{2} Q \cdot \frac{Q}{C} = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{\epsilon_0 A}{d} (E d)^2 = \frac{\epsilon_0}{2} (A d) E^2
 \end{aligned}$$

Calculus Aside

$$dU = dq \Delta V = \frac{q dq}{C}$$

$$U_C = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C}$$

in terms of the capacitor's physical parameters, we can express this potential energy in terms of the associated electric field

ex How much energy is stored in a $2.0 \mu\text{F}$ capacitor that has been charged to 5000 V ? What is the average power dissipation if it's discharged in 10 ms ?

$$U_C = \frac{1}{2} C \Delta V^2 = \frac{1}{2} (2.0 \times 10^{-6} \text{ F}) (5000 \text{ V})^2 = 25 \text{ J}$$

$$P = \frac{\Delta E}{\Delta t} = \frac{25 \text{ J}}{1.0 \times 10^{-5} \text{ s}} = 2.5 \times 10^6 \text{ W} = 2.5 \text{ MW}$$

(equivalent to dropping a 1 kg mass 2.5 m)

→ this is the basic idea underlying a defibrillator (which stores $\sim 300 \text{ J}$ to release over $\sim 2 \text{ ms}$)

ex The spacing between the plates of a 1.0 μF capacitor is 0.050 mm

• what is the surface area of the plates?

$$C = \frac{\epsilon_0 A}{d} \rightarrow A = \frac{dC}{\epsilon_0} = 5.65 \text{ m}^2$$

→ this is an enormous surface area!

definition of capacitance!

• If attached to a 1.5V battery, how much charge is on the plates?


$$Q = C \Delta V = 1.5 \times 10^{-6} \text{ C} = 1.5 \mu\text{C}$$

→ we will soon see how we can reduce this surface area by means of dielectrics, (i.e. something to sandwich between the plate to affect the electric field)

∴

Combinations of Capacitors (series vs. parallel)

Parallel

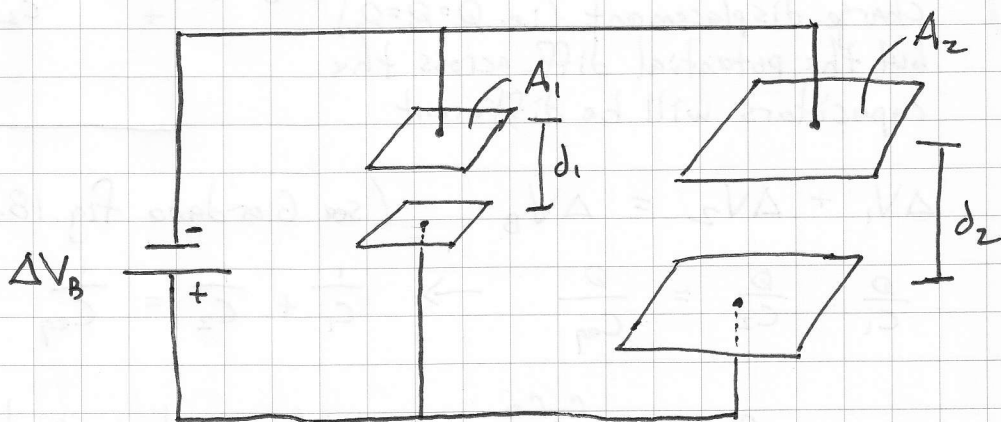

→ the same potential difference (ΔV_B) appears across both capacitors, but a different amount of charge is displaced (to see *why* ΔV is the same for both, think about the way they are connected to one another → charge would move to equilibrate any

1/23/13


Parallel (cont.)

$$Q_1 = C_1 \Delta V_B \quad \text{and} \quad Q_2 = C_2 \Delta V_B$$

$$Q_{\text{total}} = Q_1 + Q_2 = C_1 \Delta V_B + C_2 \Delta V_B = (C_1 + C_2) \Delta V_B$$
$$= C_{\text{eq}} \Delta V_B$$

[C_{eq} is the 'equivalent' capacitance if you were to consider the 'whole' as one capacitor]

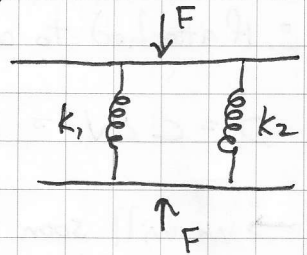
→ the combined system acts like one capacitor with a (bigger!) capacitance $C_{\text{eq}} = C_1 + C_2$



⇒ If this seems a bit odd/unintuitive, think about what happens when you place two springs between two boards and try to compress them

Series

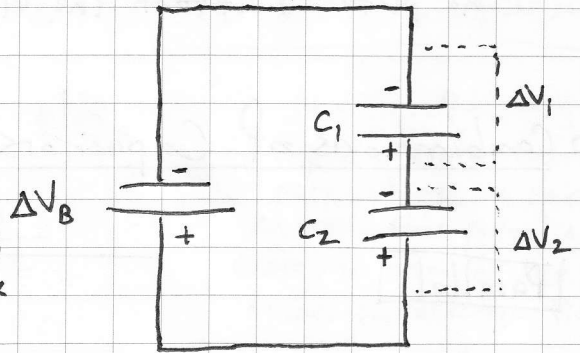• this case is a bit trickier, as the two now have the same charge displacement (i.e. $Q = Q_1 = Q_2$) but the potential diff. across the capacitors will be different



$$\Delta V_1 + \Delta V_2 = \Delta V_B \quad (\text{see Giordano Fig. 18.25})$$

$$\frac{Q}{C_1} + \frac{Q}{C_2} = \frac{Q}{C_{\text{eq}}} \rightarrow \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_{\text{eq}}}$$

$$\text{or } C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$$

(again think of the mechanical spring analogy)

→ very different re 'parallel' case in that if $C_1 \gg C_2$, C_{eq} is small (i.e. since C_2 can't hold much charge, the combined system is limited)

