




# Circuits 101

□ Circuits are 'closed' in the sense that current flows in loops (see Giordano's water pump analogy in Fig. 19.11); when a circuit is 'open' (i.e. a switch is not closed), no current will flow (see Giordano's bird-on-wire in Fig. 19.12)


NOTE: A circuit can be 'closed' by connecting to ground (that is, electrons can flow to the earth, which is considered to have zero potential)

□ Circuits can have various elements (e.g. batteries, capacitors, resistors, etc...) connected via 'ideal wires'; these connections are crucial to know in order to understand the circuits behavior

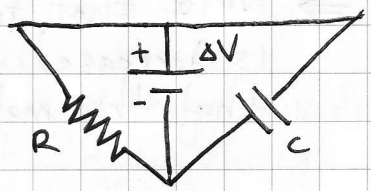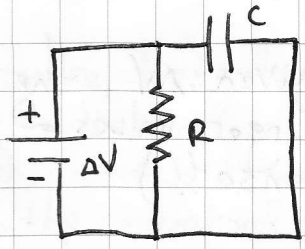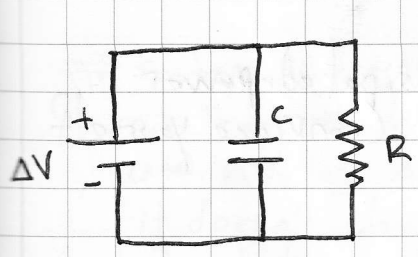→ circuits can have different branches and be drawn in a variety of ways. For example, all the following are equivalent (think about why!):




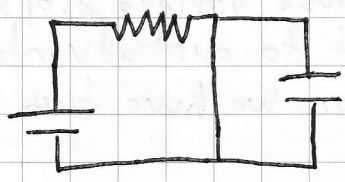Note that these are different from (this circuit will have a very different behavior from the others!)



2/1/13

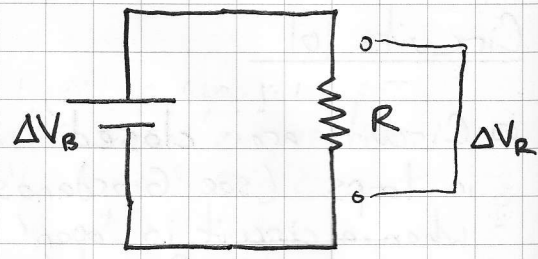□ Consider a simple circuit to start: a battery connected to a resistor



→ battery creates a potential difference across R ( $\Delta V_R = \Delta V_B$ ) such that electrical potential energy fueled by the battery is 'dissipated' (i.e. burned off) due to the current flowing through it

$$\text{power} = \frac{\text{dissipated energy}}{\text{time}}$$

→ During time  $\Delta t$ , we have charge  $\Delta q = I \Delta t$  dropping in energy by  $\Delta E = \Delta q \Delta V$  ~~( $\Delta E = I \Delta t \Delta V$ )~~

$$\text{so } \Delta E = \Delta q \Delta V = I \Delta t \Delta V = \frac{\Delta V}{R} \Delta t \Delta V$$

$$\text{so } P = \frac{\Delta E}{\Delta t} = I \Delta V = \frac{\Delta V^2}{R}$$

⇒ NOTE that for a given  $\Delta V$ , the dissipated power is decreased for larger values of R (convince yourself that this makes sense!!)

□ Because voltage drops across a resistor, we can use that to our advantage to create a useful effect when we have two resistors: a voltage divider

- Voltage drop along the path will deal with both  $R_1$  and  $R_2$  by means of their sum (we'll see why shortly)

$$\Delta V_B = V_1 + V_2$$

↑  
voltage drop across  $R_1$

↑  
voltage drop across  $R_2$

$$= IR_1 + IR_2$$


$$= I(R_1 + R_2)$$

$$\rightarrow I = \frac{\Delta V_B}{R_1 + R_2}$$

Now note that

$$\Delta V_2 = R_2 I$$

$$= \frac{R_2}{R_1 + R_2} \Delta V_B$$

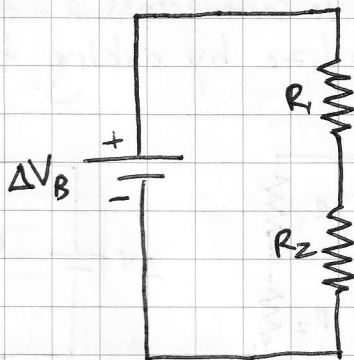

(same current goes through both resistors!)

→ Note that even though the same charges pass through each resistor, they can have different energies!




(hence the difference in  $V_1$  and  $V_2$ )

⇒ so depending upon the relative values of  $R_1$  and  $R_2$ , we can 'step down' or 'dial up' a potential (since  $0 \leq \Delta V_2 \leq \Delta V_B$ ); this is known as a **voltage divider** (it doesn't change the amount of current flowing through  $R_1$ , but does decrease the energy of that flow)

[if this seems confusing, try relating back to Giordano's water flow analogies as shown in Fig. 19.1 and Fig. 19.11]

2/1/13

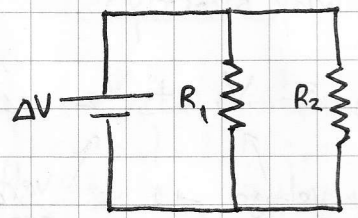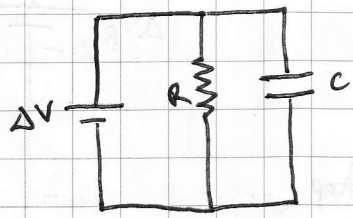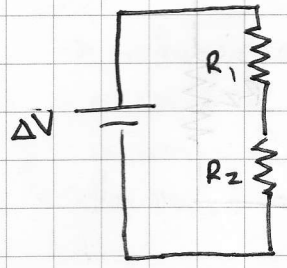□ So we've come across a few concepts that we can further crystallize by asking the following question:



→ How does the behavior of these circuits differ?

□ Considering how the behavior of a capacitor-only circuit varied depending upon their connections (i.e. series vs parallel; see 1/23 and 1/29 notes), the above question motivates a series of additional questions:

- What is the relationship between voltage and current for different 'branching' layouts in the circuit?
- How does the voltage and/or current change depending upon whether we have a resistor or capacitor (or something else) at a given place?
- How is energy stored when we have a combination of elements? Dissipated? How does this change when we re-wire things?


⇒ We can get quite a lot of insight by means of two (deceptively simple) rules: Kirchoff's Rules

□ We will state Kirchoff's Laws, then look at a set of circuits of resistors + battery to understand what they imply and how to use them

Kirchoff's Law

1) Junction Law:


$$\sum I_{in} = \sum I_{out}$$

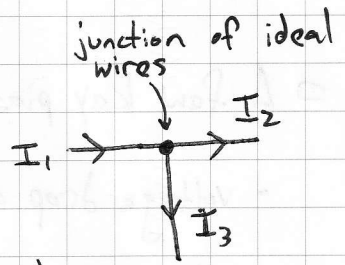

(this stems from the conservation of charge and current; put another way, what flows in must flow out w/ respect to a junction)

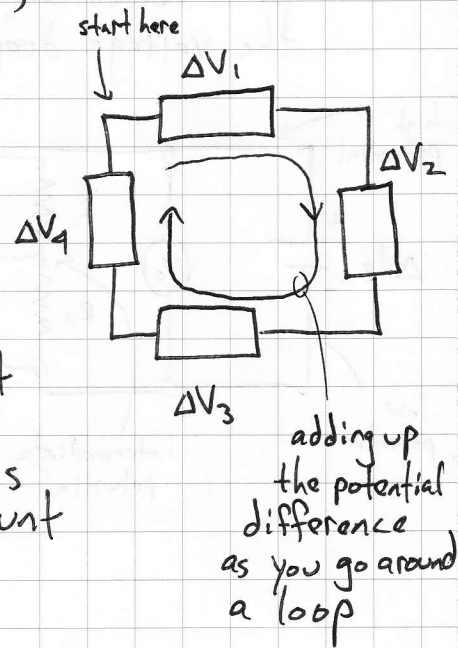2) Loop Law:

$$\Delta V_{loop} = \sum \Delta V_i = 0$$



(this is essentially a statement on the conservation of energy; a charge that moves fully around a closed loop and returns to its starting point has  $\Delta U = 0$ , i.e. it has the same amount of electrical potential energy)

Historical Aside:

- Kirchoff was a German who formulated these 'laws' while he was still a student in 1845!
- Kirchoff based his work off of Georg Ohm, and later on Maxwell realized Kirchoff's Laws can be derived from a more general set of considerations (known as Maxwell's eqns.)