


2/6/13

# Ground

□ We have been a bit loose in defining an appropriate reference (i.e. where is the potential zero?). When dealing with potential diffs. this is not an issue.

→ However when connecting different circuits together, you need a common reference

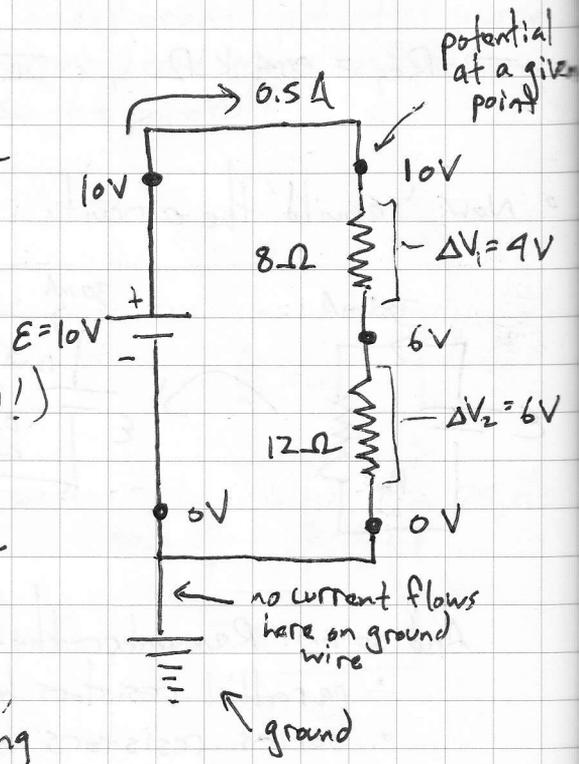□ Consider the earth as a conductor upon whose potential we define as 0 V. Suppose we connect a wire from our circuit to the earth (such that there is no closed loop to ground!)




◦ Ground wire is not part of complete circuit, so no current flows along it

◦ Since wires are equipotential, it gives connecting points along the wire the same potential (i.e. 0 V)

◦ Though the ground wire can change the potential, it does not affect the way the circuit functions (i.e. total resistance stays unchanged, voltage drop across resistor is unchanged, current through resistors is unchanged)

\* → what the ground allows us to do is specify the potential at a given point along the circuit (not just a potential difference across a given element)

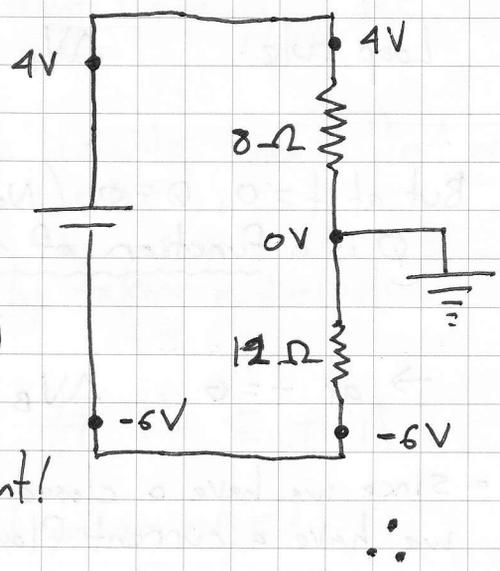
ex] what if we re-wired the circuit such that the ground was in between the two resistors?



→ the only thing that has changed is the potential (not the potential difference!) at a given point along the circuit, simply just because we changed our reference point!

RC Circuits

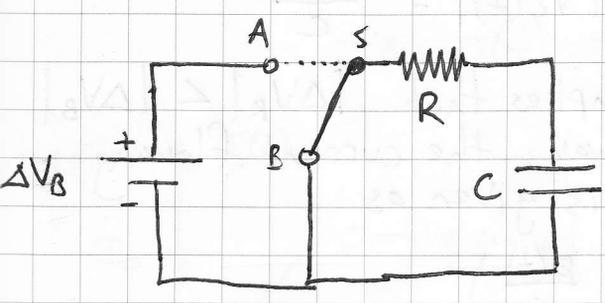→ what happens when a capacitor is added to the mix?



Switch connects either:

- S to A (battery charges C via R)
- S to B (battery disconnected → C discharged via R)

Basic Idea: When connected to battery, current flows through R and charges C. Once battery is disconnected, that energy stored in C gets 'discharged' via R.

2/6/13

- 1) Start w/ S-B connection. No charge on C (i.e.  $Q=0$ )
- 2) Connect S-A. Current starts to flow due to battery

Loop rule:  $\Delta V_B - IR - \frac{Q}{C} = 0$

$\swarrow \Delta V_R$        $\nwarrow \Delta V_C$

$\nearrow$  potential drop due to capacitor

But at  $t=0$ ,  $Q=0$  (Note that  $Q$  is a function of time, as is  $I$ )

$\rightarrow$  at  $t=0$ ,  $\Delta V_B = IR \rightarrow I(t=0) = \frac{\Delta V_B}{R}$

$= \Delta V_R$

• Since we have a closed loop, that means that at  $t=0$  we have a current flowing through C (limited by R)

- 3) For  $t > 0$ , charge  $Q(t)$  starts to build up on the capacitor plates

$$|V_C(t)| = \frac{Q(t)}{C}$$

From the loop rule, this implies that  $|\Delta V_R| < |\Delta V_B|$  for  $t > 0$ . Put another way, the current flowing (through both R and C) is given as

$$I(t) = \frac{1}{R} \left( \Delta V_B - \frac{Q(t)}{C} \right)$$

$\rightarrow$  Can we obtain a more specific expression for  $I(t)$  that doesn't depend upon  $Q(t)$ ?  
[we will need a bit of calculus]

2/6/13

4) Remember that  $I(t) \equiv \frac{dQ}{dt}$  (by definition). So re-writing things:

$$\frac{dQ}{dt} = \frac{\Delta V_B}{R} - \frac{1}{RC} Q(t) = I_0 - \frac{Q(t)}{\tau}$$

where  $I_0 = \frac{\Delta V_B}{R}$  (initial current) and  $\tau \equiv RC$  (this is called the RC time const.)

NOTE: This is an example of a (simple, linear first order ordinary differential eqn., or ODE)


→ we can get back to  $I(t)$  by taking a derivative:

$$\frac{d^2 Q}{dt^2} = -\frac{1}{\tau} \frac{dQ}{dt} \iff \frac{dI}{dt} = -\frac{1}{\tau} I(t)$$

(another ODE!)

6) This is a fairly simple/common ODE that you can more or less guess the answer based upon a result from calculus (i.e.  $\frac{d}{dx} e^x = e^x$ ) combined w/ the chain rule

$$\rightarrow I(t) = I_0 e^{-t/\tau}$$

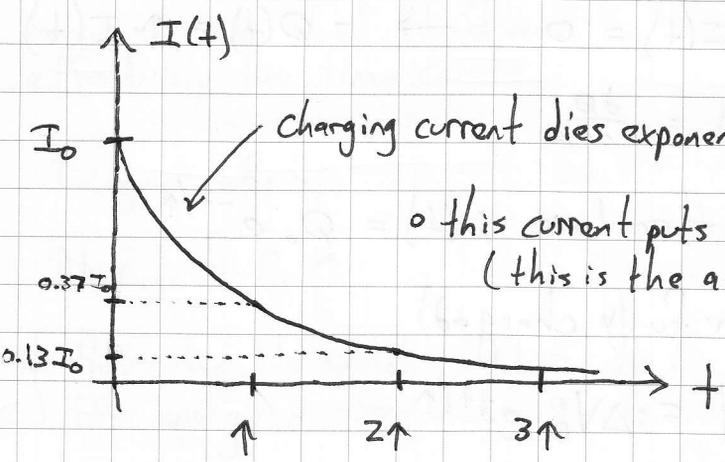

charging current dies exponentially w/ time const.  $\tau$

o this current puts charge  $Q(t)$  on the plate (this is the area under the  $I(t)$  curve)

o this charge builds up the potential  $\Delta V_C = \frac{Q(t)}{C}$


2/6/13

7) Can we determine what  $\Delta V_C(t)$  does?  $\rightarrow$  use loop law!

$$\Delta V_B + \Delta V_R + \Delta V_C = 0 \rightarrow \Delta V_C = -\Delta V_B + RI(t)$$

$$\text{so } |V_C(t)| = \left| \Delta V_B \left( -1 + \frac{RI_0}{\Delta V_B} e^{-t/\tau} \right) \right| = \Delta V_B (1 - e^{-t/\tau})$$

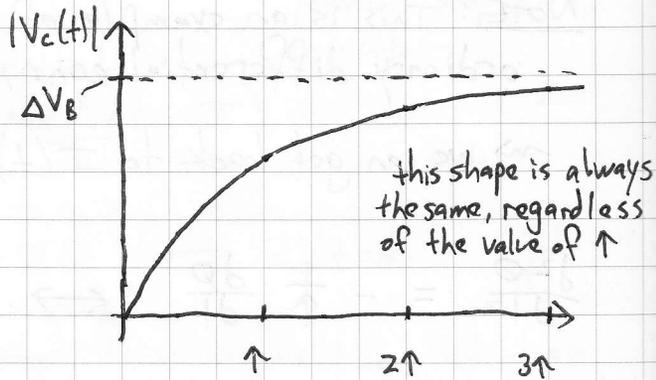$\rightarrow$  so potential diff. across capacitor is also an exponential function asymptoting to  $\Delta V_B$



8) What if we flipped the switch from S-A to S-B?

$\rightarrow$  same basic picture, but now rather than 'charge' the capacitor will 'discharge'

Loop Law:  $\Delta V_C(t) + \Delta V_R(t) = 0$   
(no battery)

$$-\frac{Q(t)}{C} - RI(t) = 0 \rightarrow -Q(t) = \tau I(t)$$


$$\text{so } -\frac{Q(t)}{\tau} = I(t) = \frac{dQ}{dt}$$

similar to before, we then have  $Q(t) = Q_0 e^{-t/\tau}$

$\bullet$   $Q_0 = C\Delta V_B$  (when fully charged)

$$\Rightarrow |V_C(t)| = \Delta V_B e^{-t/\tau}$$

ex

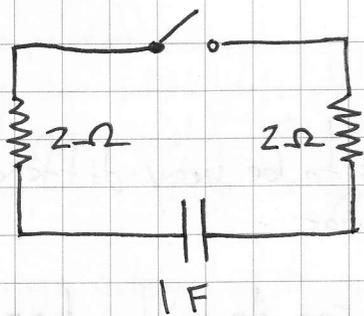

once the switch is closed, what is the time const. for the discharge of the capacitor?

→ two resistors in series ( $R_{eq} = 4\Omega$ )

$$\text{so } \tau = RC = (4\Omega)(1F) = 4s$$

Note that the resistors do not 'cancel out' such that the capacitor doesn't discharge!

NOTE  $\tau = RC$  and  $[\tau] = s$  → does this make sense?

$$[R] = \Omega = \frac{V}{A} = \frac{kg \cdot m^2 / A \cdot s^3}{C \cdot s} = \frac{J \cdot s}{C^2}$$


$$[C] = F = \frac{A \cdot s}{V} = \frac{C^2}{J}$$

$$\text{so } [R][C] = \frac{J \cdot s}{C^2} \cdot \frac{C^2}{J} = s \quad \checkmark$$

□ For the circuit to the right, the picture doesn't change much except that there are effectively two time consts.

$$\tau_{\text{charge}} = R_1 C$$

$$\tau_{\text{discharge}} = R_2 C$$

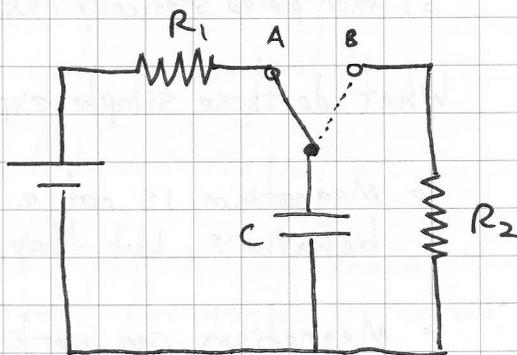

Note that when the switch is flipped to B (from A, after fully charging C) then energy dissipated by  $R_2$  is the same as the energy stored in C