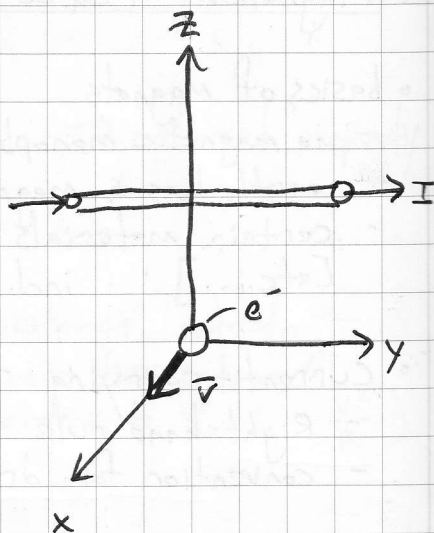


2/26/13

(Giordano P20.17)

[ex] Electron passes near a current-carrying wire laying in  $y-z$  plane. Electron moves along  $+x$ -axis. What is the force on the electron due to the wire's magnetic field?



•  $\vec{B}_{\text{wire}}$  points along  $-x$ -axis where electron is

•  $\vec{F}_m = q(\vec{v} \times \vec{B})$  where  $q = -e$

but since  $\vec{v} \times \vec{B} = 0$  (since they are parallel to one another), the force is zero

• However, once the electron moves off the  $y-z$  plane, there will be a non-zero component of  $\vec{v} \times \vec{B}$  and the electron will start feel a force

[ex] (Giordano P20.52)


length of wire  
 $F_{\text{wire}} = ILB \sin \theta$

$$\vec{F}_{\text{total}} = \sum_i \vec{F}_i$$

$$= \vec{F}_L + \vec{F}_R + \vec{F}_H$$


$$= 0 - IB \left( \frac{L}{\cos \theta} \right) \sin \theta + IB L \tan \theta$$
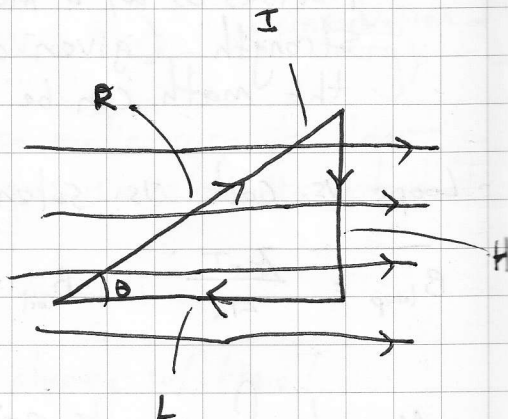
$$= 0 \quad (\text{no net force, regardless of } \theta!)$$




• Note that sign diff. arises because  $F_R$  is into the page and  $F_H$  is out of the page

ex (Giordano P19.100)

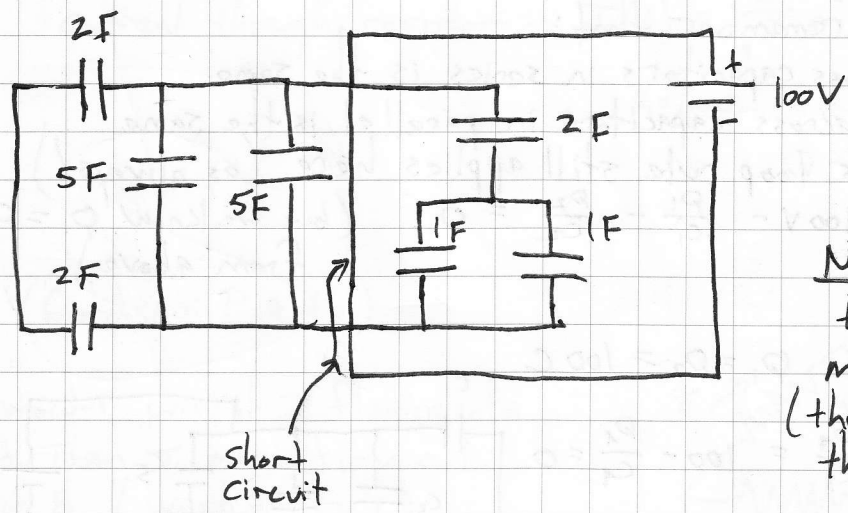


NOTE: As shown in the text, the problem makes no sense! (there is a short across the battery)

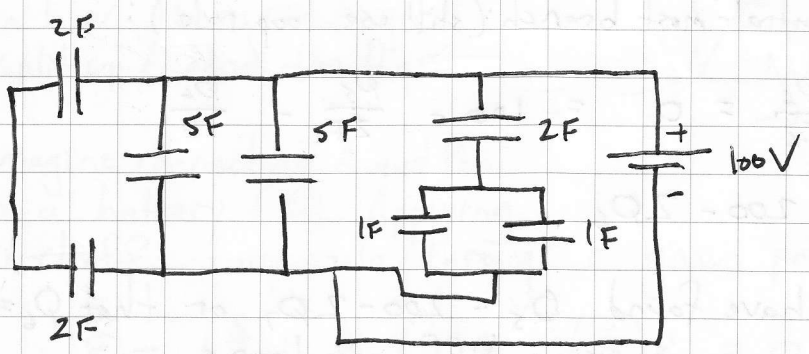
More realistic version (that doesn't kill the battery)



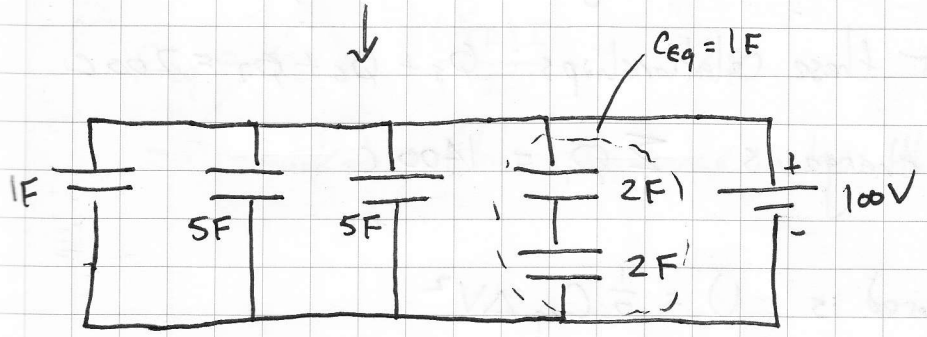Strategy  
Break down the various branches into smaller and smaller pieces



$C_{eq} = 12F$

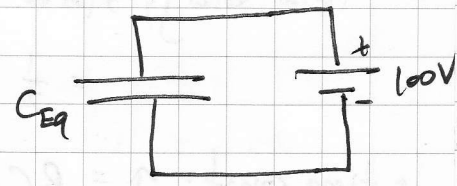

2/26/13 (cont.)

(19.100 cont)

To get the charge, remember that:


- charge across capacitors in series is the same
- potential across capacitors in parallel is the same
- Kirchoff's loop rule still applies here (as always!)

eg.  $100V - \frac{Q_1}{C_1} - \frac{Q_2}{C_2} = 0$  (but we know  $Q_1 = Q_2$  from above)

since  $C_1 = C_2 = 2F$ ,  $Q_1 = Q_2 = 100C$

similarly:  $100 - \frac{Q_3}{C_3} = 100 - \frac{Q_4}{C_4} = 0$

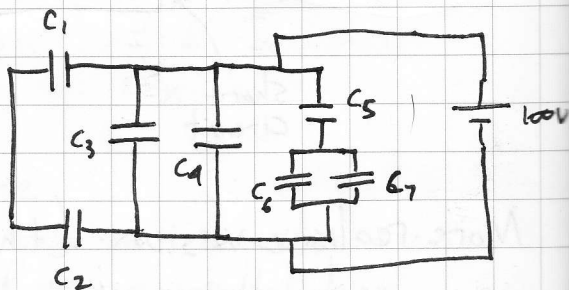$C_3 = C_4 = 5F \rightarrow Q_3 = Q_4 = 500C$



a bit tricky for the central-most branch: (still use loop rule):

$$100 - \frac{Q_5}{C_5} - \frac{Q_6}{C_6} = 0 = 100 - \frac{Q_5}{2F} - \frac{Q_6}{1F}$$

$$\rightarrow Q_5 = 200 - 2Q_6$$

we similarly could have found  $Q_5 = 200 - 2Q_7$  or that  $Q_6 = Q_7$  using different loops

adding together these relationships:  $Q_5 + Q_6 + Q_7 = 200C$

thus the total charge is  $\sum_i Q_i = 1400C$

◦ total energy stored is  $U = \frac{1}{2} C_{eq} \Delta V^2$   
 $= \frac{1}{2} (12) (100)^2 = 6 \times 10^4 J$

◦ time const:  $\tau = RC_{eq} = (100 \Omega)(12 F) = 1.2 \times 10^3 s$  (Very long!)


(19.100 cont.)

current through resistor:  $I(t) = \frac{\epsilon}{R} e^{-t/\tau} = e^{-t/1200} \text{ A}$

$\epsilon = 100 \text{ V}$   
 $R = 100 \Omega$

ex] (Giordano P19.46)

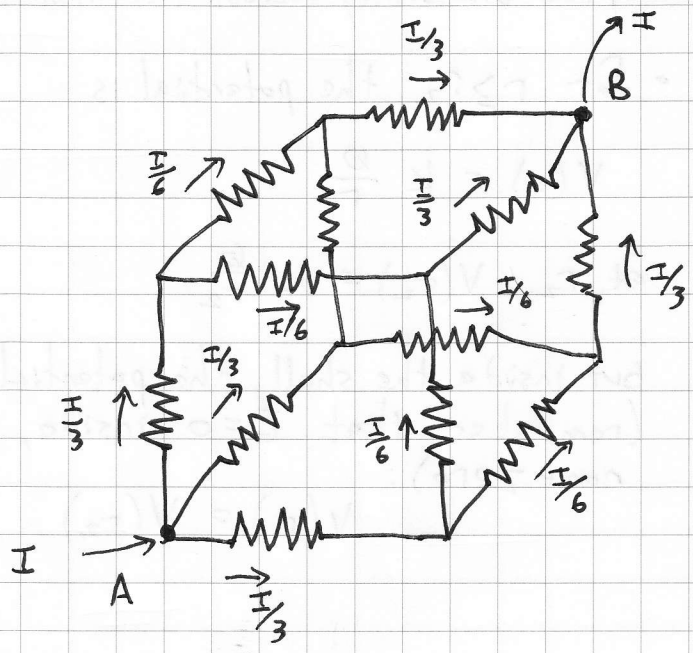- consider current  $I$  flowing into A. Then  $I$  must flow out at B (junction rule)
- since all resistors are the same, there is a symmetry in how the current gets split up/added together
- imagine connecting A and B to a battery ( $\epsilon$ ). Applying Kirchoff's loop rule through a given path:



$$\epsilon - \left(\frac{I}{3}\right)R - \left(\frac{I}{6}\right)R - \left(\frac{I}{3}\right)R = 0 \rightarrow \epsilon = I\left(\frac{5}{6}R\right)$$


$$R_{eq} = \frac{\epsilon}{I} = \frac{\left(\frac{5}{6}R\right)I}{I} = \frac{5}{6}R$$

→ remarkably this resistance is less than a single resistor!

2/26/13

ex (Giordano P18.30)

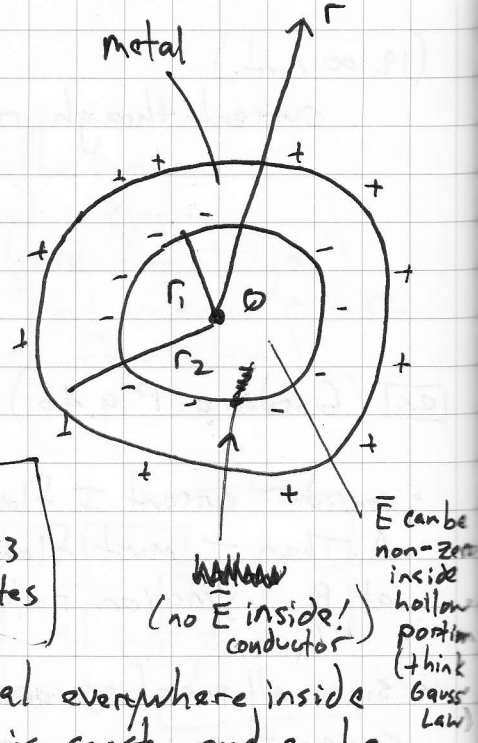- since  $\vec{E} = 0$  inside the inner shell ( $r < r_1$ ) there must be  $-\phi$  excess charge spread uniformly across the inner surface
- for  $r \geq r_2$ , the potential is



for additional ref. see 'fig. 27.33 from 1/22/13 notes

$$V(r) = k \frac{\phi}{r}$$

at  $r_2$ ,  $V(r_2) = k \frac{\phi}{r_2}$

but inside the shell, the potential is equal everywhere inside (remember that  $\vec{E} = 0$  inside, but  $V$  is const. and can be non-zero):

$$V(r_1) = V(r_2) \rightarrow V(r_1) = k \frac{\phi}{r_2}$$


ex (Giordano P17.48)

$$\vec{E} = \sum_i \vec{E}_i = \vec{E}_2 + \vec{E}_3 + \vec{E}_4$$

$$(\vec{E}_1 + \vec{E}_5 = 0)$$

$$= (\cos 45) k \frac{\phi}{r_2} (\hat{y}) + k \frac{\phi}{r_2} (-\hat{y}) + (\cos 45) k \frac{\phi}{r_2} (-\hat{y})$$
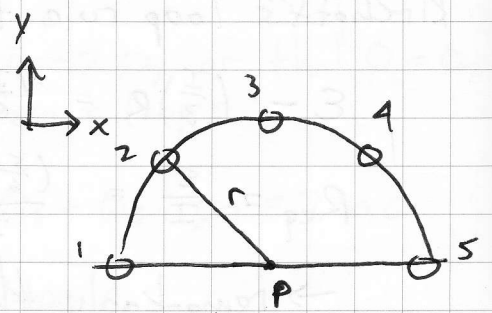
$$= (1 + \sqrt{2}) k \frac{\phi}{r_2} (-\hat{y})$$



NOTE: Vector components along  $\hat{x}$  cancel out (only left w/ components pointing along  $-\hat{y}$  (assuming  $\phi > 0$ ))