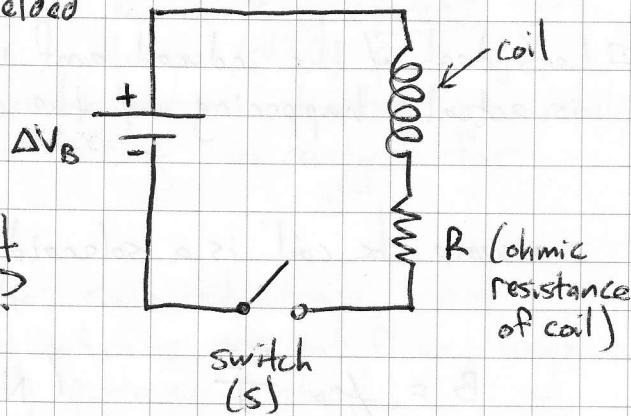


# Inductance and RL Circuits

□ Faraday's Law (combined w/ Lenz's Law) basically states that an electromotive force is generated so to resist change. or put another way that there is some sort of 'inertia' associated with magnetic fields

✓ (i.e. an N-turn solenoid)

□ Consider a coil placed into a circuit containing a battery. Assume the coil has some resistance ( $R$ ) associated with it (we can represent this as a resistor in series w/ the coil). Also assume there is no magnetic flux through the coil (e.g. it is shielded from earth's field)



- When the switch  $S$  is closed (at  $t=0$ ), what is the current flowing through the circuit?

Guess:  $I = \frac{\Delta V_B}{R}$

→ If this is true, then there'd be a magnetic flux  $\Phi_B$  instantly set up in the coil. From Faraday's Law:


$$\mathcal{E} = -\frac{d\Phi_B}{dt} \quad \rightarrow \text{instant turn-on of current mean } \frac{d\Phi_B}{dt} = \infty!$$

(not possible!!)

⇒ An emf will be induced in the coil to prevent an instant turn-on of the current

3/6/13

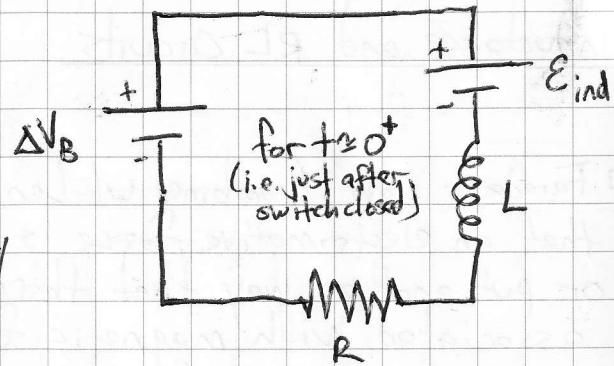- the coil acts as an inductor and tries to prevent an increase in  $\Phi_m$  (from zero) by countering the battery emf ( $\Delta V_B$ ) with an induced emf ( $E_{ind}$ )



- The induced emf is transient: as time goes on the current grows and a magnetic field is built up. As this happens, the rate of change of  $\Phi_m$  decreases and  $E_{ind}$  decreases

Let's deal w/ the induced emf in detail by considering what is actually happening w/ the coil:

- assume the 'coil' is a solenoid (length  $\gg$  radius)

$$B = \mu_0 \frac{NI}{d} \quad (N = \# \text{ of turns})$$

cross-section  
A - area of  
solenoid

- For a single turn:  $\Phi_m^{(1)} = BA = \mu_0 \frac{NI}{d} A$

- For N turns (i.e. total flux):  $\Phi_m = N\Phi_m^{(1)} = \mu_0 \frac{N^2 I}{d} A$

- Faraday's Law:  $E_{ind} = - \frac{d\Phi_m}{dt} = -\mu_0 \frac{N^2 A}{d} \frac{dI}{dt} \equiv -L \frac{dI}{dt}$

$\Rightarrow L = \frac{\mu_0 N^2 A}{d}$  (physical property of the solenoid)

$$\Rightarrow \mathcal{E}_{\text{ind}} = -L \frac{dI}{dt} \quad (\text{self-induced emf})$$

$$= \Delta V_L \quad (\text{potential 'drop' across inductor})$$

◻ We call  $L$  the inductance and ~~what parts of the circuit have inductance~~

→ some general comments on inductance:

- a physical property of a solenoid (or coil) that one can measure

- has units of Henrys (H), which is equivalent to


$$1 \text{ H} = \frac{\text{m}^2 \cdot \text{kg}}{\text{C}^2} = \frac{\text{V} \cdot \text{s}}{\text{A}} = \Omega \cdot \text{s}$$

- Turning on a current ( $dI/dt > 0$ ) means  $\mathcal{E}_{\text{ind}}$  opposes the battery. Turning off the battery ( $dI/dt < 0$ , e.g. disconnecting it) means the current can not stop immediately and  $\mathcal{E}_{\text{ind}}$  exists such that the current can continue for some time
- A simple straight wire also has some inductance, as it surrounds itself w/ a  $\vec{B}$  field when a current flows through it (their inductance  $L$  is relatively quite small though)
- The induced emf has something to do w/ energy storage: building up  $\vec{B}$  via a current implies energy storage analogous to that in an electric field ( $E$ ) of a capacitor
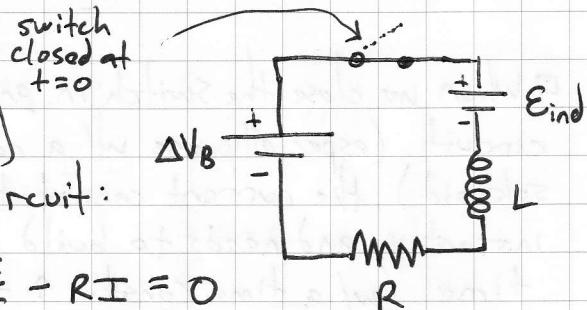
### LR Circuit

◻ Can apply Kirchoff's Law (loop rule) to determine the dynamics of the circuit:

$$\Delta V_B + \Delta V_L + \Delta V_R = \Delta V_B - L \frac{dI}{dt} - RI = 0$$



3/6/13

→ So now we have a (differential) equation that tells us about the current through the circuit and how it varies w/ time:

- we likely expect an asymptotic response (i.e. exponential)
- at  $t = 0$ , the current through the circuit should be zero (since the induced  $E_{ind}$  opposes the flow of current so to prevent the flux  $\Phi_m$  from changing)
- We can introduce a new time constant ( $\tau$ ) as follows:

$$\frac{\Delta V_B}{R} - \frac{L}{R} \frac{dI}{dt} - I = 0 \quad \rightarrow \quad I_{ss} - \uparrow \frac{dI}{dt} - I = 0$$


- $I_{ss} \equiv \frac{\Delta V_B}{R}$  (steady-state current, happens when  $t \rightarrow \infty$ )
- $\tau \equiv \frac{L}{R}$  (inductive time const.), const.

[Math Aside: this is an example of a linear, homogeneous, autonomous first order ordinary differential equation]

⇒ Solution:  $I(t) = I_{ss} (1 - e^{-t/\tau})$   $\equiv$  ODE


[Verify that this solution satisfies the ODE stemming from Kirchoff's Loop Law]

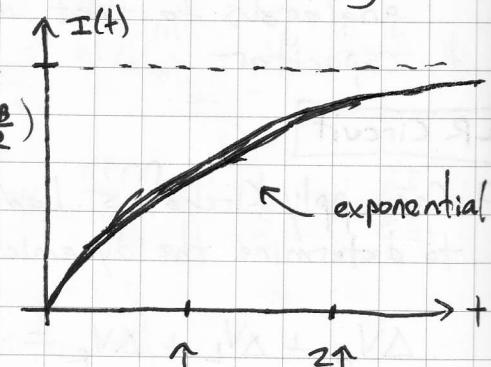- ◻ When we close the switch in any circuit (especially one w/ a coil or solenoid), the current cannot turn on instantly and needs to build up over time (w/ a time const.  $\tau = L/R$ )



- ◻ Note that the door swings both ways here in that disconnecting the battery (but keeping a closed circuit) will cause an induced current to resist the change

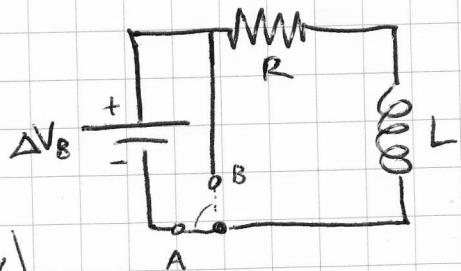- assume switch is at A for a long time. Then the current through the battery is  $I_0 = \Delta V_B / R$



- Now flip the switch to B (i.e. essentially disconnect the battery)

$$\text{Kirchhoff's Loop Rule: } \Delta V_R + \Delta V_L = 0$$

$$-RI - L \frac{dI}{dt} = 0$$

→ similar to before, but one less term!

$$\text{Solution: } I(t) = I_0 e^{-t/\tau} \quad (\tau = \frac{L}{R})$$

⇒ exponential decay from  $\Delta V_B / R$  down to zero

- ex** See circuit below. Switch initially at A for a long time, then flipped to B at  $t=0$ .

- Determine the current at  $t = 5.0 \mu\text{s}$
- At what time has the current decayed to 1% its initial value?

$$I_0 = \frac{10\text{V}}{100\Omega} = 0.1\text{A} \quad (\text{current before } t=0)$$

$$\tau = \frac{L}{R} = \frac{0.002\text{H}}{(100+100)\Omega} = 10\mu\text{s} = 10 \times 10^{-6}\text{s}$$

$$I(5 \times 10^{-6}\text{s}) = 0.1\text{A} e^{-5/10} = 0.061\text{A}$$

$$0.01I_0 = I_0 e^{-t/(10 \times 10^{-6}\text{s})} \rightarrow t = 46\mu\text{s}$$

(use natural log!)

