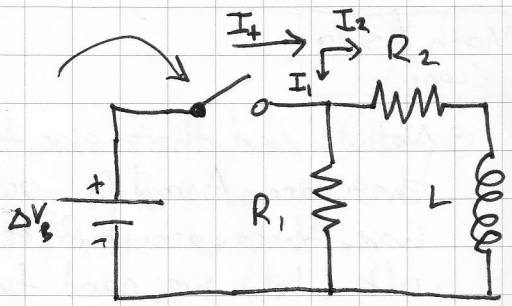


3/12/13

ex. (Giordano P.2.42)

switched closed at $t=0$



a) At $t=0$, inductor prevents current flow through R_2 branch (i.e. $\Delta V_{R_2} \neq 0$)

- $R_1 = 0.8 \text{ k}\Omega$
- $R_2 = 0.5 \text{ k}\Omega$
- $L = 4.5 \text{ mH}$
- $\Delta V_B = 3.0 \text{ V}$

$$\Delta V_{R_1} = I_1 R_1 = \Delta V_B$$

$$\rightarrow I_1 = \frac{\Delta V_B}{R_1} = \frac{3.0 \text{ V}}{800 \Omega} = 3.8 \times 10^{-3} \text{ A} = 3.8 \text{ mA}$$

b) At $t=0$, there is no potential drop across R_2 . Put another way, L is essentially in parallel w/ R_1 (i.e. they have the same potential across them)

$$|\Delta V_L(t=0)| = 3 \text{ V}$$

\rightarrow put yet another way, this is the \mathcal{E}_{ind} that opposes current flow through the R_2 branch

c) After the switch has been closed for a long time, $\mathcal{E}_{\text{ind}} (= \Delta V_L) = 0$, since the current (and thereby the mag. flux) has reached steady-state. So we just have two resistors in parallel, both w/ the same potential diff. ($\Delta V_B = 3 \text{ V}$) across them:


$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2} \approx 307.7 \Omega \quad \rightarrow \quad I_+ = \frac{3 \text{ V}}{0.31 \text{ k}\Omega} = 9.7 \text{ mA}$$

$$I_1 + I_2 = I_+, \quad I_2 = \frac{R_1}{R_1 + R_2} I_+ \approx 6.0 \text{ mA} \text{ (to right)}, \quad I_1 = 3.7 \text{ mA} \text{ (downward)}$$

d) Switched opened at $t = t_{open}$ (i.e. battery essentially disconnected)

→ inductor creates \mathcal{E}_{ind} to oppose change and induces clockwise current. at $t = t_{open}$

$|\mathcal{E}_{ind}| = 3V + \text{contrib. due to } R_1, R_2 \text{ (see e)}$

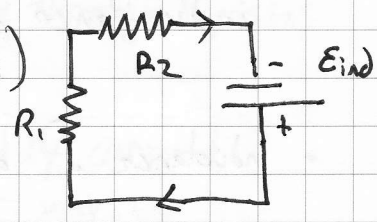

So current through R_1 is $\frac{\mathcal{E}_{ind}}{R_1} = 6.0 \text{ mA}$ and points in the opposite direction of I_1 from when the switch was closed (!)




e) Use Kirchoff's Loop Rule:

$$\Delta V_L \neq \Delta V_{R1} + \Delta V_{R2} = 0$$

$$\Delta V_L = -\Delta V_{R1} - \Delta V_{R2} = I_2 (R_1 + R_2) = (6.0 \text{ mA})(900\Omega + 500\Omega) = 7.8 \text{ V}$$

∴

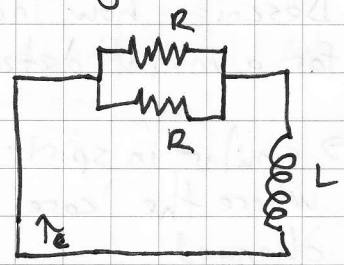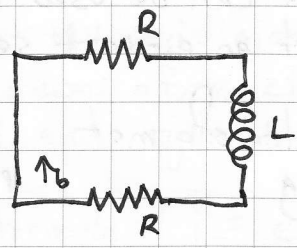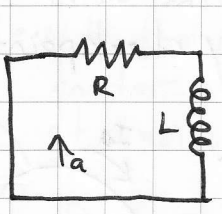ex Rank the time constants from smallest to largest:



$$\tau = \frac{L}{R} \rightarrow R_b > R_a > R_c \rightarrow \tau_c > \tau_a > \tau_b$$

∴

3/12/13

ex An inductor is made by tightly wrapping 0.30 mm diameter wire around a 4.0 mm diameter cylinder. What must the length of the cylinder be in order to get an inductance of 10 μ H?

• Inductance of a solenoid is given by $L = \frac{\mu_0 N^2 A}{l}$

→ we are looking for l

• N (the total # of turns) must be given by $N = \frac{l}{d}$
(think about it; put another way, $l = Nd$ since all turns span the length of the cylinder)
 $r =$ radius of cylinder ($= 2.0$ mm)


so $L = \frac{\mu_0 A}{l} \left(\frac{l}{d}\right)^2 = \frac{\mu_0 \pi r^2 l}{d^2} \rightarrow l = \frac{L d^2}{\mu_0 \pi r^2}$

$= \frac{(1.0 \times 10^{-5} \text{ H})(3.0 \times 10^{-4} \text{ m})^2}{(4\pi \times 10^{-7} \text{ Tm/A}) \pi (2.0 \times 10^{-3} \text{ m})^2} = 0.057 \text{ m} = 5.7 \text{ cm}$

ex Describe how inductance can be used as the basis for a metal detector at an airport security checkpoint.

→ similar in spirit to a transformer where the 'core' is being changed

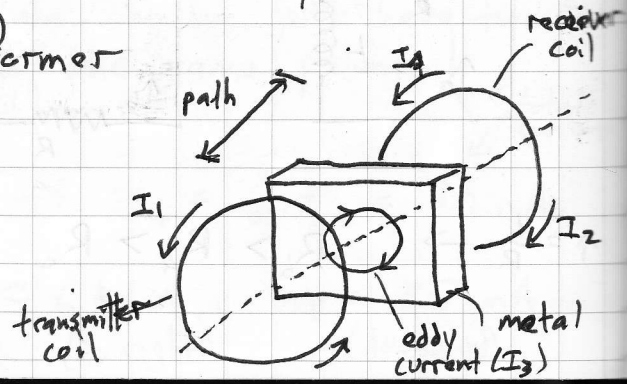
• two coils are set up, one a 'transmitter', the other a 'receiver'



- Drive the transmitter w/ an AC high frequency 'control' signal (I_1). This will induce an oppositely-oriented current in the receiver (I_2)
- The scanned object (e.g. a person walking through) passes between the two coils.
- If the object is metal, it will produce an eddy current in a plane parallel to the coils. Put another way, a current will be induced in the metal (I_3) due to the field created by the transmitting coil
- The receiver picks up the superposition of what comes from the transmitter and metal. Specifically, the eddy current (I_3) induces a current in the receiver, opposite that produced by the transmitter. This ultimately leads to a reduction in $|I_2|$.
- Circuitry detects changes in $|I_2|$, thereby raising the alarm

ex Determine i^i .

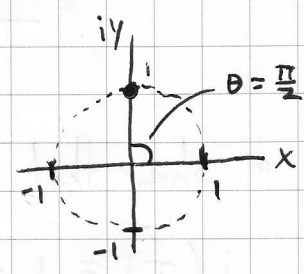• Note that $z = x + iy = i$ means $x = 0$ and $y = 1$. Put another way in terms of a circle, we are at radius $r = 1$ and angle $\theta = \frac{\pi}{2}$



• so from Euler's formula: $i = e^{i\pi/2}$

• Exponentiating exponentials: $(e^a)^b = e^{ab}$

$\rightarrow i^i = (e^{i\pi/2})^i = e^{-\pi/2} \approx 0.208$ (since $i^2 = -1$)

3/12/13

ex A solenoid has inductance $L = 50 \text{ H}$ and a resistance $R = 30 \Omega$. If connected to a 100 V battery, how long will it take to reach one half its final equilibrium value?

$$I(t) = I_{\max} (1 - e^{-t/\tau})$$

$$I_{\max} = \frac{\Delta V_B}{R}$$

$$\tau = \frac{L}{R} \approx 1.67 \text{ s}$$

$$\text{so } \frac{1}{2} I_{\max} = I_{\max} (1 - e^{-t_0/\tau})$$

$$\rightarrow 1 - e^{-t_0/\tau} = \frac{1}{2}, \quad e^{-t_0/\tau} = \frac{1}{2}, \quad -\frac{t_0}{\tau} = \ln\left(\frac{1}{2}\right)$$

$$\Rightarrow t_0 = -\tau \ln\left(\frac{1}{2}\right) = -(1.67) \ln\left(\frac{1}{2}\right) \approx 1.2 \text{ s}$$

ex Complex # arithmetic

polar form

cartesian form

$$Re^{i\theta} = x + iy$$

• express $z = 10 e^{i\pi/2}$ in cartesian form

$$\begin{cases} R = \sqrt{x^2 + y^2} \\ \theta = \tan^{-1}\left(\frac{y}{x}\right) \end{cases}$$

$$R = 10, \quad \theta = \frac{\pi}{2}$$

$$x = R \cos \theta = 10 \cos \frac{\pi}{2} = 0$$

$$y = R \sin \theta = 10 \sin \frac{\pi}{2} = 10$$

$$\begin{cases} x = R \cos \theta \\ y = R \sin \theta \end{cases}$$

$$\rightarrow z = 10 e^{i\pi/2} = 10i$$

• Show that $\frac{1}{i} = -i$

$$i \left\{ \frac{1}{i} \right\} = i \left\{ -i \right\} \Rightarrow i \cdot (-i) = -i^2 \Rightarrow -(-1) = 1 \quad \checkmark$$

(multiply both sides by i)

◦ Show that $i = e^{i\pi/2}$

3/12/13

$$i = 0 + 1 \cdot i \rightarrow x=0, y=1 \rightarrow R=1$$

$$\theta = \arctan\left(\frac{1}{0}\right) = \arctan(\infty) = \frac{\pi}{2}$$

$$\rightarrow i = Re^{i\theta} = e^{i\pi/2} \checkmark$$

Basics of complex arithmetic:

Addition: $(a+ib) + (c+id) = (a+c) + i(b+d)$

Subtraction: $(a+ib) - (c+id) = (a-b) + i(b-d)$

Multiplication: $(a+ib)(c+id) = (ac-bd) + (bc+ad)i$

Division: $\frac{(a+ib)}{(c+id)} = \frac{(a+ib)(c-id)}{(c+id)(c-id)} = \left(\frac{ac+bd}{c^2+d^2}\right) + \left(\frac{bc-ad}{c^2+d^2}\right)i$

NOTE: if $z = c+id$, then $z' = c-id$ is called the complex conjugate of z . It has the nice property that:

$$z \cdot z' = (c+id)(c-id) = c^2 - d^2 \quad (\text{which is real!})$$