
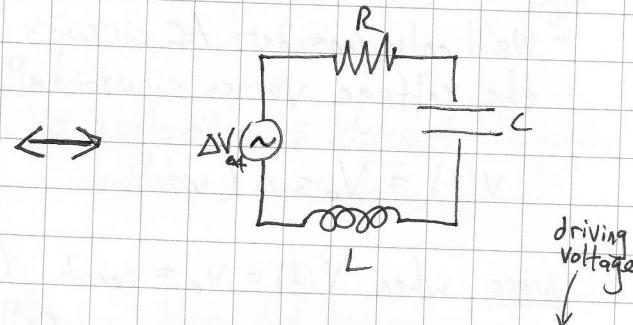


AC Circuits (Giordano ch. 22)

3/18/13

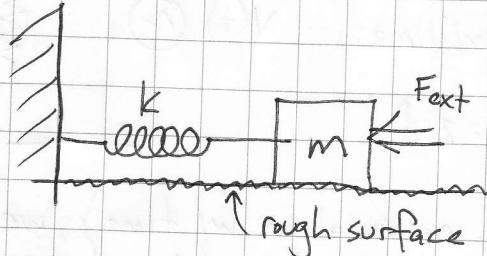□ Remarkably, these two are physically equivalent:



$$M\ddot{x} + b\dot{x} + kx = F_{ext}$$

$$L\ddot{q} + Rq + \frac{q}{C} = \Delta V_{ext}$$

- mass \leftrightarrow inductance
 - spring \leftrightarrow capacitor
 - damping \leftrightarrow resistor
- \boxed{X} storage of energy (reactance)
- \boxed{R} loss of energy (resistance)

Note: Engineers commonly use the notion of impedance, which is a complex quantity and defined as

$$Z = R + iX \rightarrow |Z| = \sqrt{R^2 + X^2}$$

where

$$X = X_L - X_C$$

$$= Z\pi f L - \frac{1}{Z\pi f C}$$

$$= \left[R^2 + \left(Z\pi f L - \frac{1}{Z\pi f C} \right)^2 \right]^{\frac{1}{2}}$$

(this is eqn. 22.41 in Giordano's book)

and f is the driving freq.

(we assume V_{ext} is sinusoidal at freq. f)

\Rightarrow this leads to a more general form of Ohm's Law: $V = IZ$


(though Giordano states this in eqn. 22.39, he avoids the complex nature of things)

3/18/13

- Let's take a step back and try to more clearly lay out the pieces dealing w/ AC circuits

- We'll only consider AC circuits where the voltage varies sinusoidally w/ time:
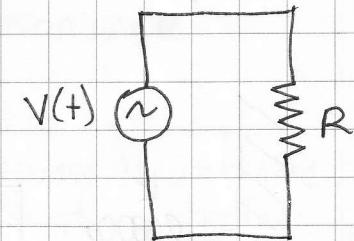
$$V(t) = V_0 \sin(\omega t) \quad \omega = 2\pi f$$



NOTE when $V(t) = V_0 = \text{const.}$ (i.e. no variation w/ time), we call the voltage DC (direct current)
 ↳ this is what we've dealt with primarily until now

- From Ohm's Law, we simply have:

$$I(t) = \frac{V_0}{R} \sin(\omega t)$$

- A useful quantity are RMS (root-mean-square) values, defined as:

$$V_{\text{rms}} = \sqrt{\frac{1}{2} V^2}$$

r - root
 m - $\frac{1}{2}$

s - squared max.

or more simply:

$$V_{\text{rms}} = \frac{V_{\text{max}}}{\sqrt{2}}$$

$$\approx 0.71 V_{\text{max}}$$

NOTE: V is the max. amplitude of displacement

→ Also applies to current as well: $I_{\text{rms}} = 0.71 I_{\text{max}}$

- To see why rms quantities are useful in the context of AC circuits, let us consider power loss through a resistor when connected to a battery:
(see fig. on last pg.)

- Battery

$$\Delta V_B = \mathcal{E} \rightarrow P_B = i_B \mathcal{E}$$

Note: lowercase = instantaneous
uppercase = average

i_B = instantaneous current through battery (not $\sqrt{-1}$ here!)

- Resistor

$$P_R = i_R V_R = i_R^2 R \quad (\text{power dissipated by resistor})$$

- Assume circuit is AC: $i_R = I_R \cos \omega t$

$$\rightarrow P_R = I_R^2 R \cos^2 \omega t$$

- Let P_R be the average power (i.e. total energy dissipated per second)

$$P_R = I_R^2 R \cos^2 \omega t \quad \left| \begin{array}{l} \text{one cycle} \\ \hline \end{array} \right.$$

$$= I_R^2 R \left[\frac{1}{2} (1 + \cos 2\omega t) \right] \quad \left| \begin{array}{l} \text{one cycle} \\ \hline \end{array} \right.$$

$$= \frac{1}{2} I_R^2 R + \frac{1}{2} I_R^2 R \cos 2\omega t \quad \left| \begin{array}{l} \text{one cycle} \\ \hline \end{array} \right.$$

$$= \frac{1}{2} I_R^2 R \quad \left| \begin{array}{l} = 0 \text{ over} \\ \text{one cycle} \end{array} \right.$$

$$\text{but } \frac{1}{2} I_R^2 = \left(\frac{I_R}{\sqrt{2}} \right)^2 = I_{\text{rms}}^2 \quad (\text{and } I_{\text{rms}} = \frac{V_{\text{rms}}}{R}) \quad P_R = \frac{1}{2} I_R^2 R$$

$$\rightarrow P_R = I_{\text{rms}} V_{\text{rms}} = I_{\text{rms}}^2 R \quad \left| \begin{array}{l} \text{average power} \\ \text{dissipated over one cycle} \end{array} \right.$$

