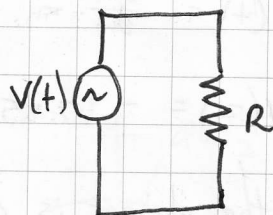


3/20/13

AC Circuits: Capacitors + Inductors

- Phasors - A useful concept (introduced in Giordano ch. 22.2) for describing AC circuits

- Consider an AC voltage source connected to a resistor:



$$V(t) = V_0 \sin(\omega t) = V_0 \sin \theta$$


(i.e. $\theta = \omega t$)

- Ohm's Law still applies here:

$$I(t) = \frac{V(t)}{R} = \frac{V_0}{R} \sin \theta = I_0 \sin \theta$$

max. current

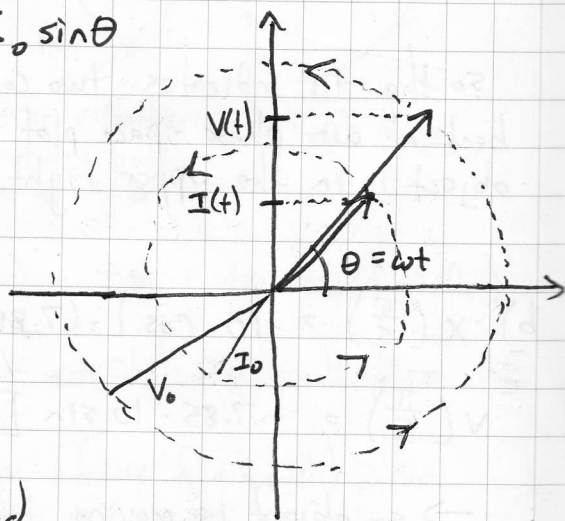
- A phasor diagram is just a way to plot the dynamics via a circle



- as time goes on, phasor rotate in counter-clockwise direction
- phasor tail fixed at origin, head ends on a circle whose radius is max. voltage or current
- The voltage or current can be determined at any given time (i.e. for a given value of θ) by projecting onto the vertical axis [if using cos, it'd be the horizontal axis projection]
- The actual axes don't matter in that they do not tell you the size of I and V, but only the timing difference between them

□ AC circuit w/ a capacitor

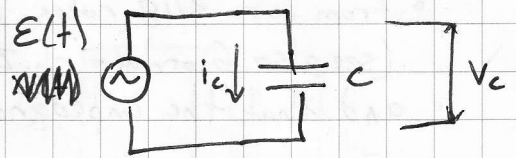◦ $\Delta V_c = V_c(t) = \frac{q}{C} = E(t)$



so the potential diff. across the capacitor is determined by the AC source $E(t)$, which in turn determines $q = q(t)$ [C is const.!]

$E(t) = E_0 \cos \omega t$
AC voltage drive


↙ change on plates varies sinusoidally!

◦ so $q(t) = C E_0 \cos(\omega t)$, but the instantaneous current through the capacitor is given by:

$i_c = \frac{dq}{dt} = -\omega C E_0 \sin(\omega t) = \omega C E_0 \cos(\omega t + \frac{\pi}{2})$

◦ Note that

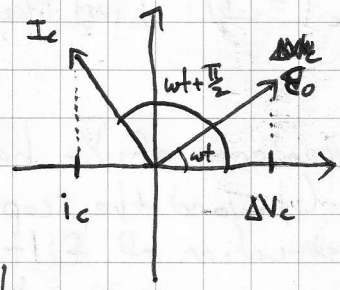$V_c(t) \propto \cos(\omega t)$
 $i_c(t) \propto \cos(\omega t + \frac{\pi}{2})$



↑ phase change of 1/4 cycle!

→ we say that the AC current through a capacitor LEADS the voltage by 1/4 cycle

← remember the projections are onto the horizontal axis here since we are using cos

→ this is directly analogous to a simple harmonic oscillator:

$x(t) = A \cos \omega t$, $v(t) = \frac{dx}{dt} = -\omega A \sin \omega t$
velocity $= -V_{max} \sin \omega t = V_{max} \cos(\omega t + \frac{\pi}{2})$

That is, the velocity 'leads' the position by 1/4 cycle (see also Giordano Figs. 22.10 and 22.13a)


2/20/13

From our 3/18 notes, we introduced the notion of impedance (see also Giordano ch. 22.7) in the context of Ohm's Law and that the impedance consisted of two parts:

- Resistance (describes how energy is added/removed from system)
- Reactance (describes how energy is stored by the system)

→ Since a capacitor stores energy (just like a spring!), we can define its reactance
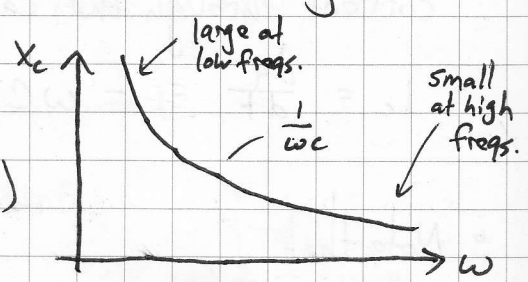
$$X_c \equiv \frac{1}{\omega C} = \frac{1}{2\pi f C}$$



Note that $[X_c] = \Omega$ (just like resist.)

This freq. dependence of X_c has many important practical implications (beyond the scope of H10 unfortunately) such for the construction of filters via RC circuits (see Giordano ex. 22.8 and Table 22.3) stemming from the RC time constant ($\tau = RC$) and oscillating nature of the driving voltage

Note that for a circuit containing only a capacitor and AC voltage source, Ohm's Law still applies (see 3/18 notes!)

$$V_c = I_c X_c \leftarrow \text{reactance}$$

↑
max. voltage across capacitor


↑
max. current through resistor (= ωCV)

Aside: Using complex #'s, we actually have $X_c = \frac{-i}{\omega C}$ such that $V = -i \cdot \frac{I_c}{\omega C}$ and multiplying by $-i$ is consistent w/ V lagging I_c by $\frac{1}{4}$ cycle!

AC circuit w/ an inductor

As we've seen before, the instantaneous voltage across an inductor is

$$V_L = L \frac{di_L}{dt}$$

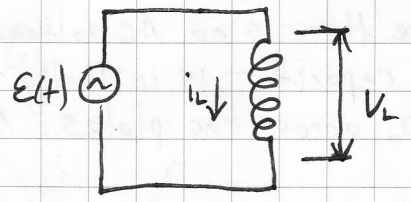

where i_L is the inst. current and V_L decreases when $\frac{di_L}{dt} > 0$ and increases when $\frac{di_L}{dt} < 0$ (Lenz's Law)

If $E(t) = E_0 \cos \omega t$, then similar to the capacitor, we'll have:

$$V_L = E_0 \cos \omega t \quad (\text{i.e. the max. volt. drops across the induct. is determined by the source})$$

Since $\frac{di_L}{dt} = \frac{V_L}{L} = \frac{E_0}{L} \cos \omega t$, we can integrate to obtain i_L :


$$i_L(t) = \frac{1}{\omega} \frac{E_0}{L} \sin \omega t = \frac{E_0}{\omega L} \cos(\omega t - \frac{\pi}{2}) = I_L \cos(\omega t - \frac{\pi}{2})$$

↑
max. current thru inductor (= $E_0/\omega L$)

So in this case the current lags the voltage by $\frac{1}{4}$ cycle (see Giordano Figs. 22.14 and 22.16a)

Similar to the capacitor, the inductor stores energy and thereby has an associated reactance:

$$X_L = \omega L$$

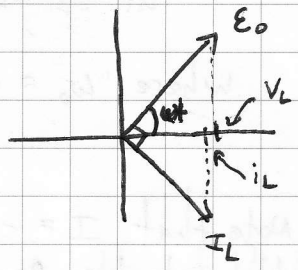

Aside: When both an inductor and capacitor are present, the total reactance is $X = X_L - X_C = \omega L - \frac{1}{\omega C}$

when a resistor is also in place, the total impedance is

$$Z = R + X_i = R + i(\omega L - \frac{1}{\omega C})$$