
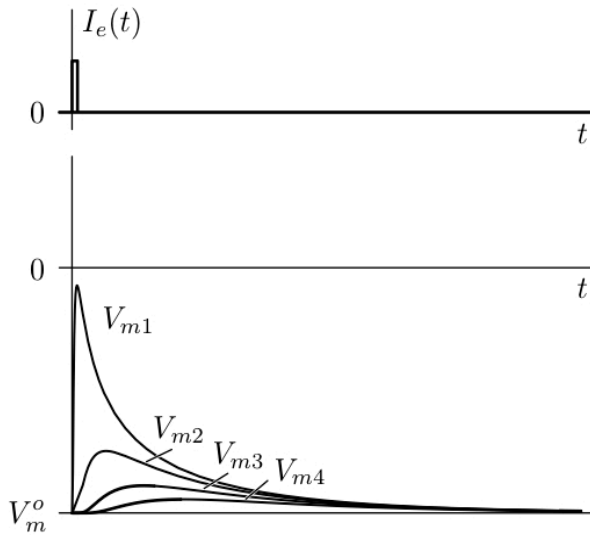


Biophysics I (BPHS 4080)



Instructors: Prof. Christopher Bergevin (cberge@yorku.ca)

Website: <http://www.yorku.ca/cberge/4080W2018.html>


Decremental conduction

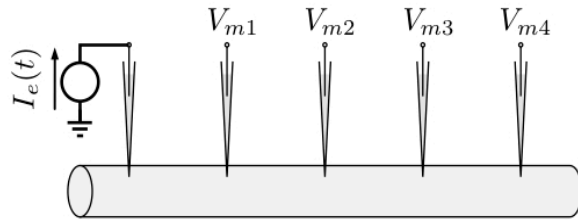

Decrement-free conduction

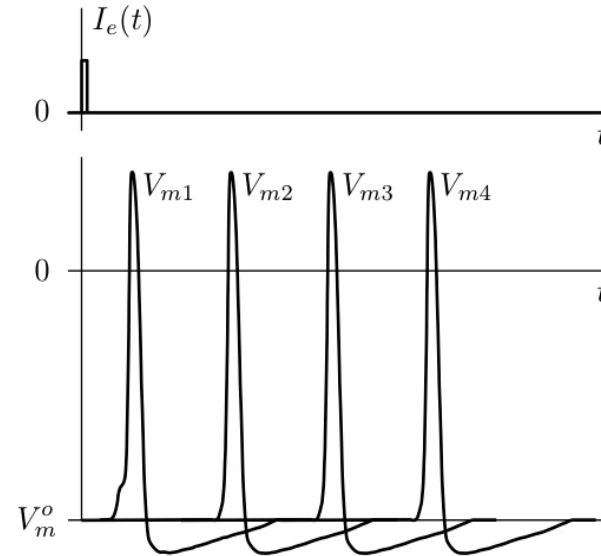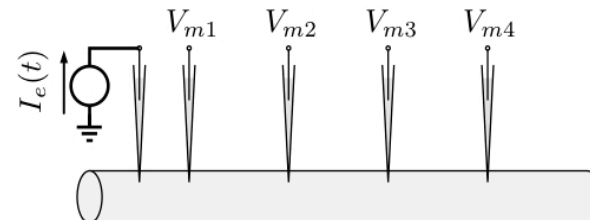

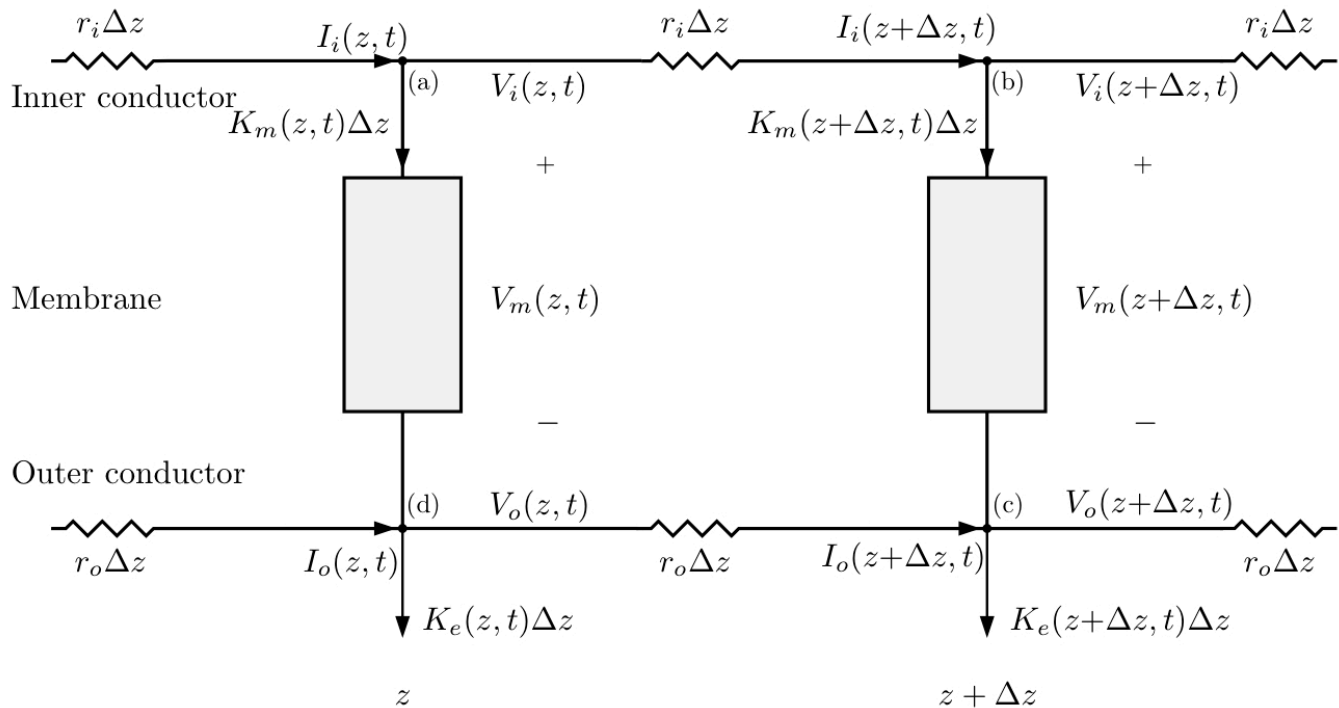Core-Conductor Model (starting point) → Model for electrically large cells





No assumptions
made about
membrane!



THE Core – Conductor Equation

$$\frac{\partial^2 V_m(z, t)}{\partial z^2} = (r_o + r_i)K_m(z, t) - r_o K_e(z, t)$$

Decremental conduction

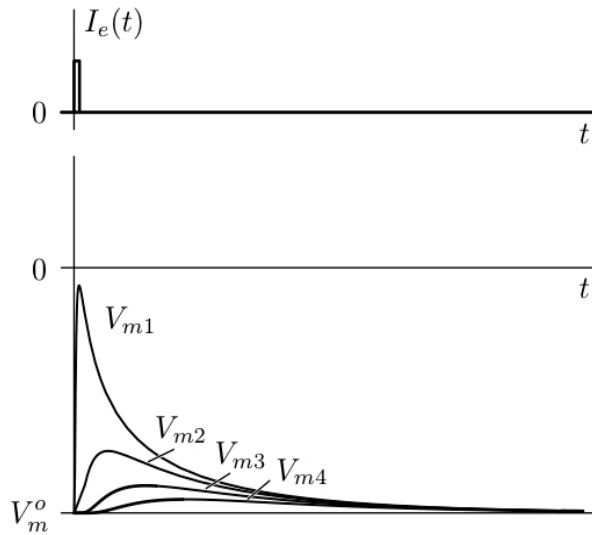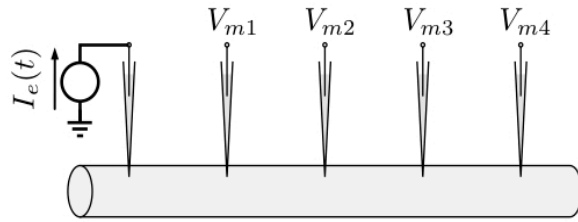

Decrement-free conduction

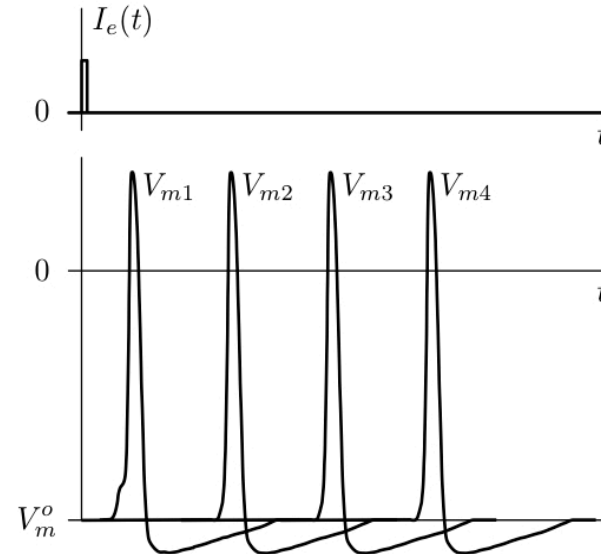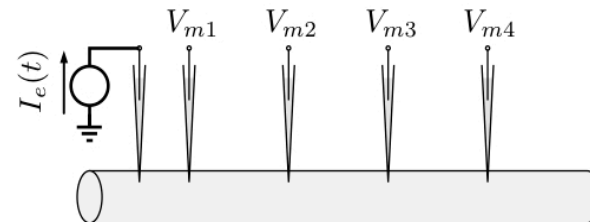

Note dynamics of response....

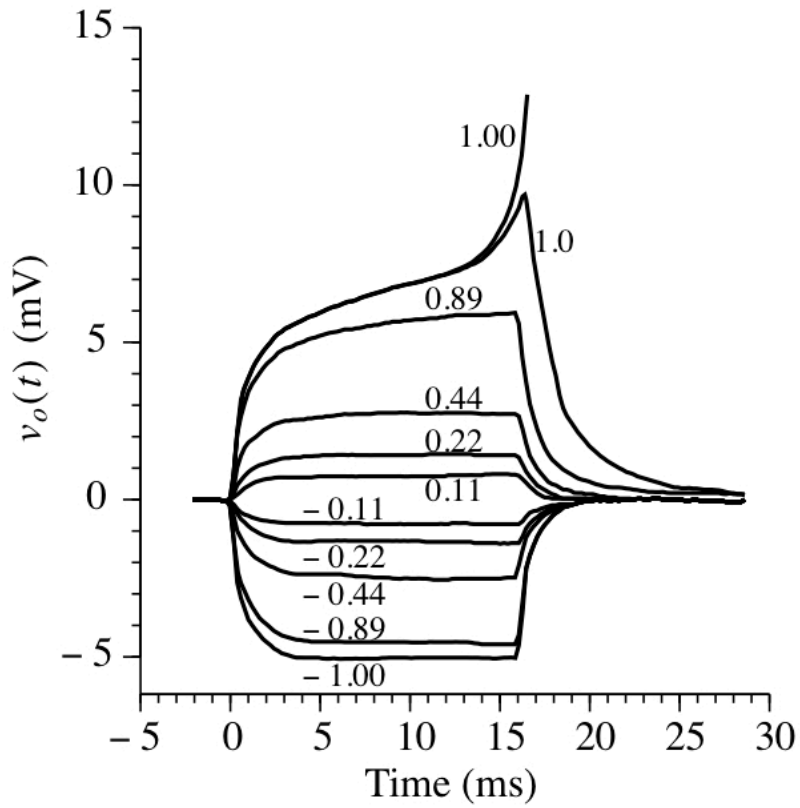


Figure 3.1

1. Linear (to a point)

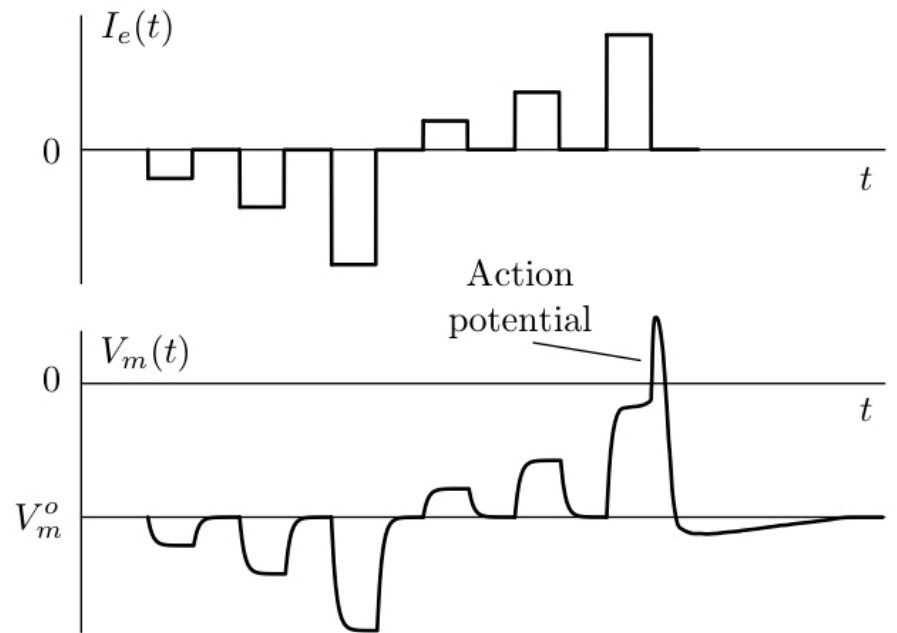
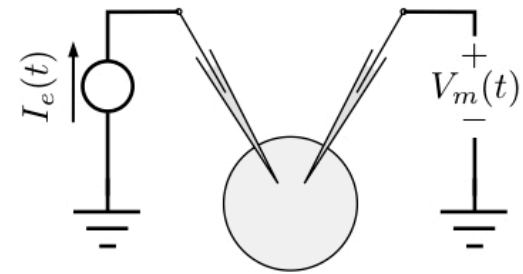


Figure 1.8

2. Delay apparent


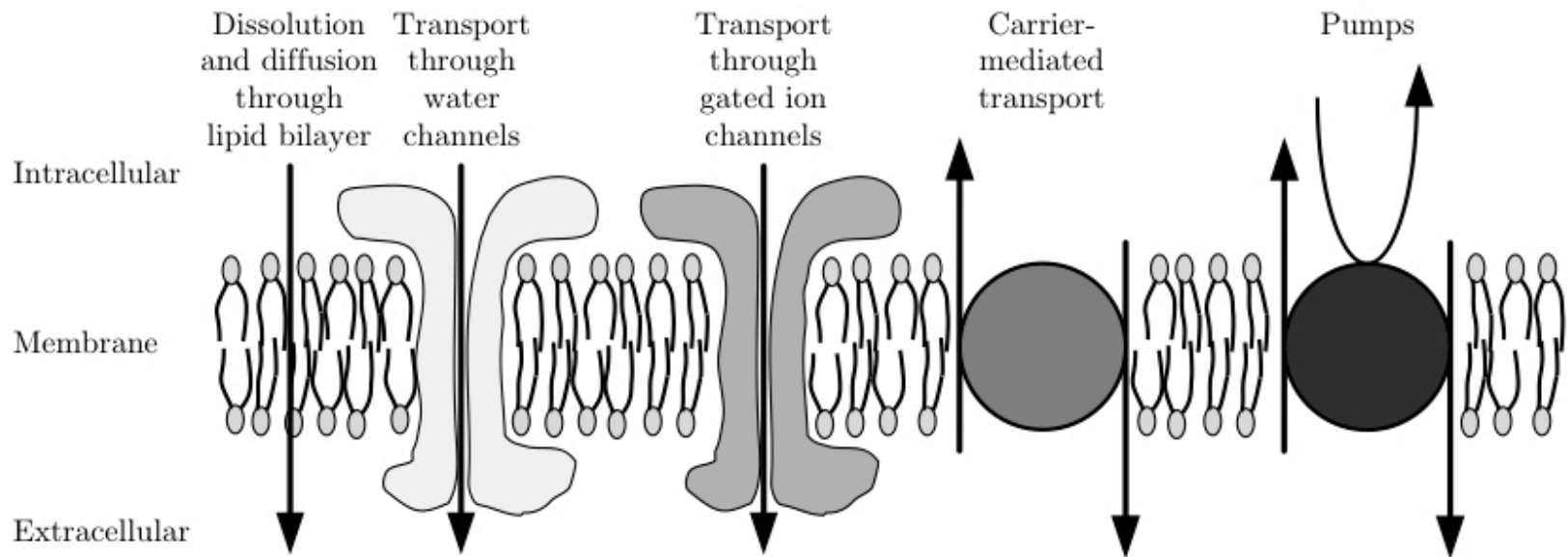


Figure 2.19


Idea: Membrane not only allows for charge transport, but also charge separation

Cell Membrane = Capacitor

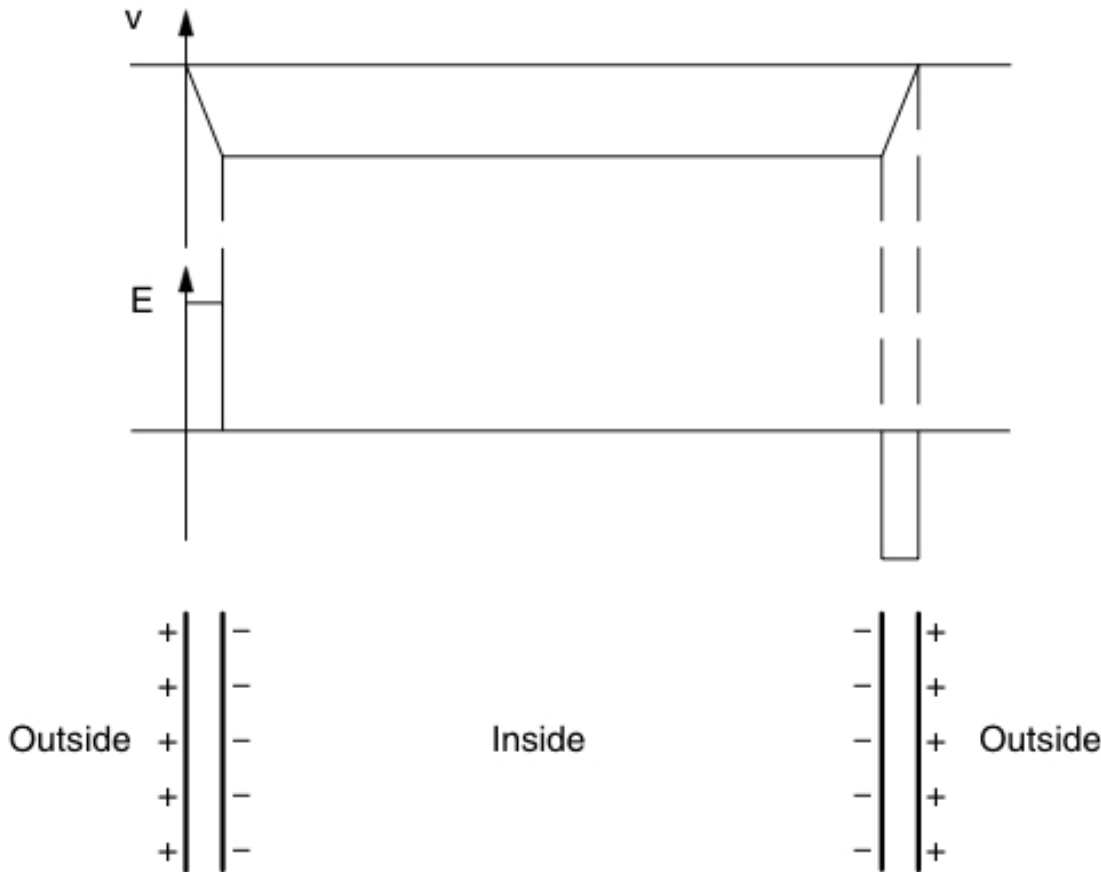


- Steady-state electrodiffusion cause charge buildup on both sides of membrane
- Charge separation acts like parallel-plate capacitor
($C \sim 1 \mu\text{F}/\text{cm}^2$)


Lipid Bilayer = Dielectric

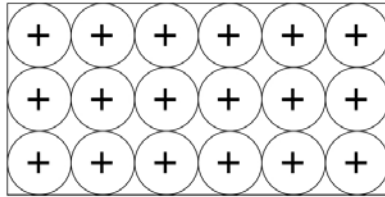


(a)

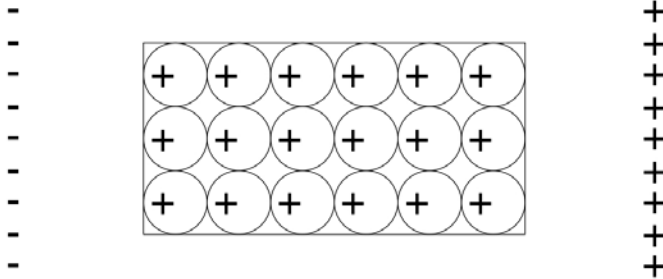

(b)

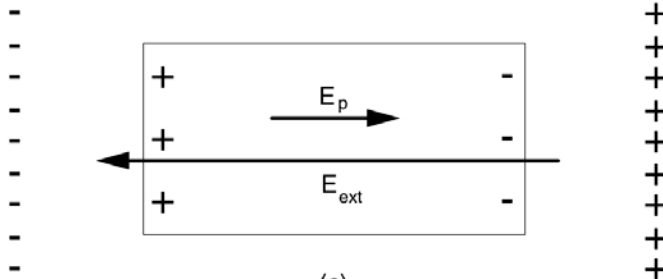

(c)




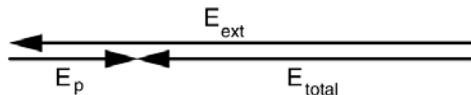


(d)

- Lipid bilayer is an insulator
(i.e., acts as a dielectric w/ const. κ)

- $\kappa \sim 3-7$, meaning more charge separation can occur (higher capacitance)

Circuit Representation

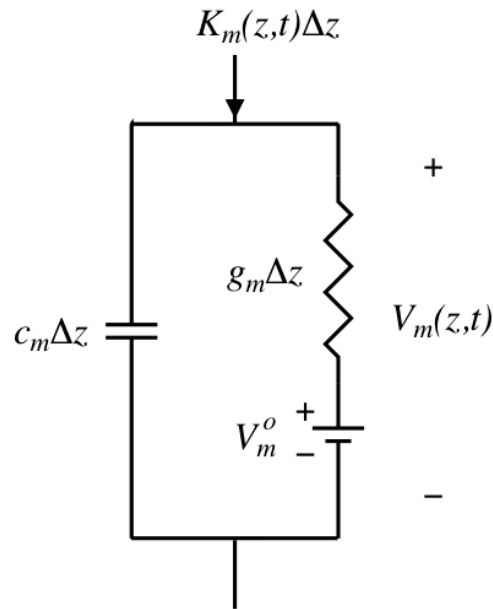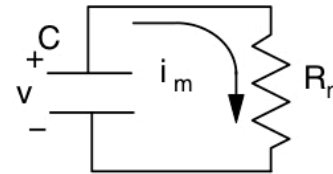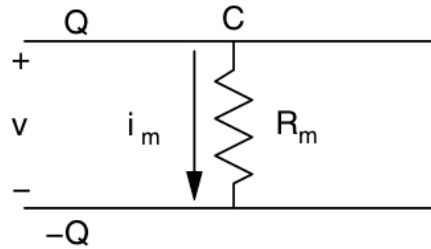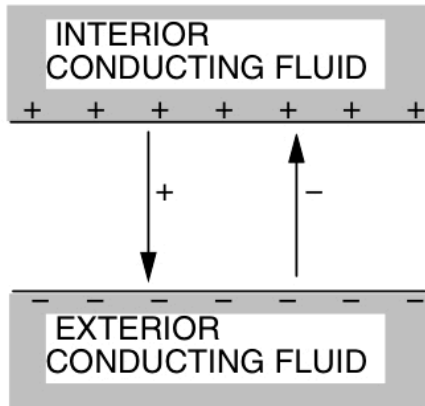


Resistor and capacitor in series
 → RC time constant

Figure 3.6

Review: Capacitance

- Charging a parallel-plate capacitor

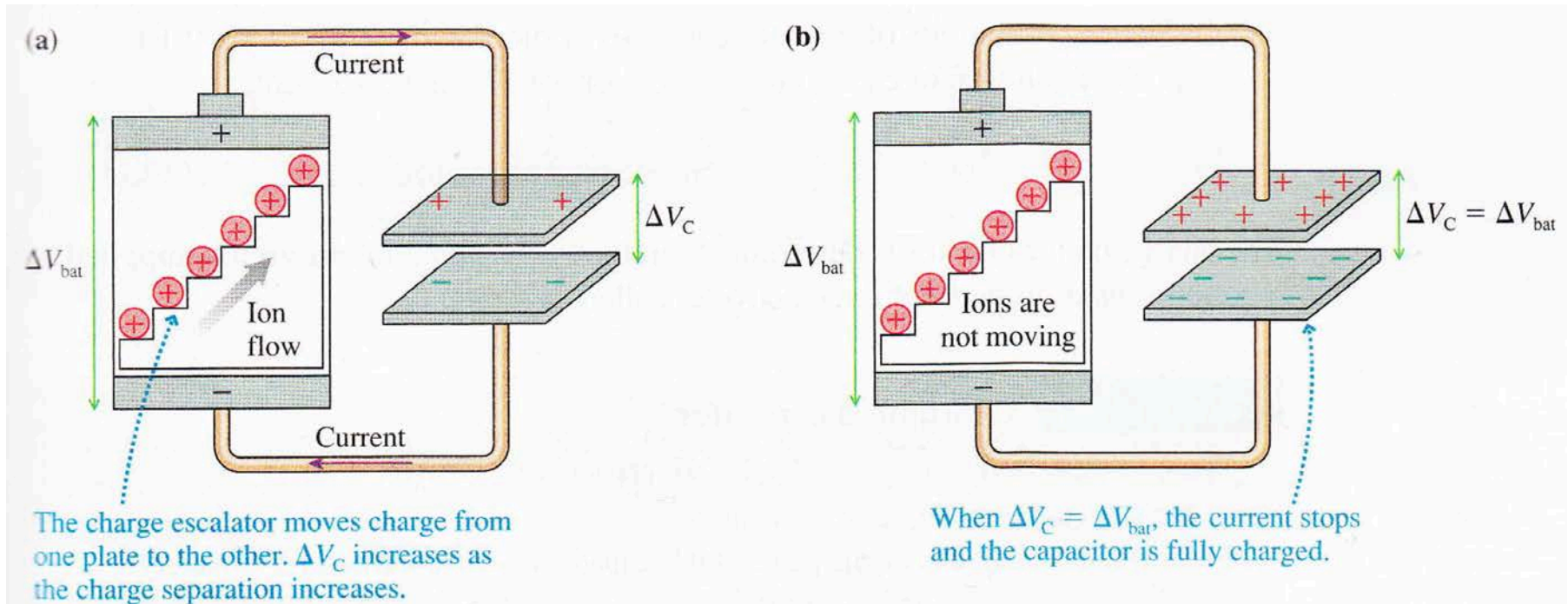

$$Q = C \Delta V_C \quad (\text{charge on a capacitor})$$

→ Stored charge is proportional to potential difference. Constant of proportionality is characterizes the “capacitance”

Review: RC Circuits

KVL (combined w/ Ohm's law):

$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$

Negative because resistor current removes charge from capacitor

$$\frac{dQ}{dt} + \frac{Q}{RC} = 0 \qquad \frac{dQ}{Q} = -\frac{1}{RC} dt$$


$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$

$$\ln Q \Big|_{Q_0}^Q = \ln Q - \ln Q_0 = \ln \left(\frac{Q}{Q_0} \right) = -\frac{t}{RC}$$

$$Q = Q_0 e^{-t/RC}$$


(a) Before the switch closes

The switch will close at $t = 0$.

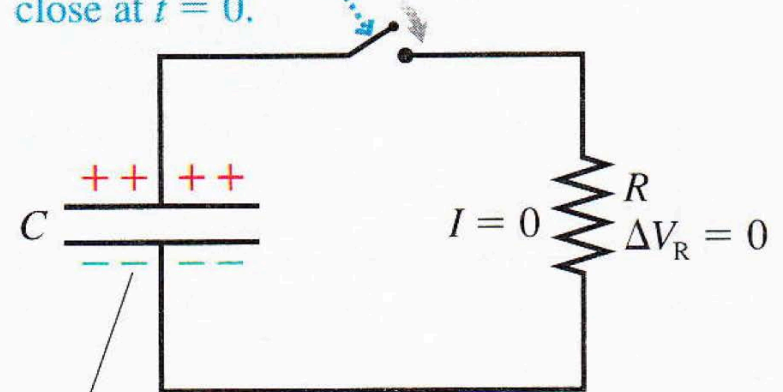

Charge Q_0
 $\Delta V_0 = Q_0/C$

(b) After the switch closes

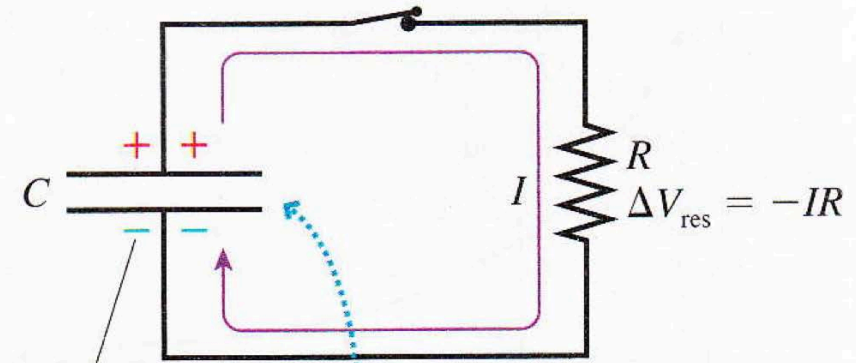

Charge Q
 $\Delta V_{\text{cap}} = Q/C$
 The current is reducing the charge on the capacitor.

Review: RC Circuits

$$Q = Q_0 e^{-t/RC}$$

$$Q = C \Delta V_C$$

$$\tau = RC$$

$$\Delta V_C = \Delta V_0 e^{-t/\tau}$$

“RC time constant”


→ Resistor dissipates energy stored in the capacitor

Current through the capacitor?

$$I = \frac{dQ}{dt}$$

$$I_C = C \frac{dV_C}{dt}$$

$$Q = C V_C$$

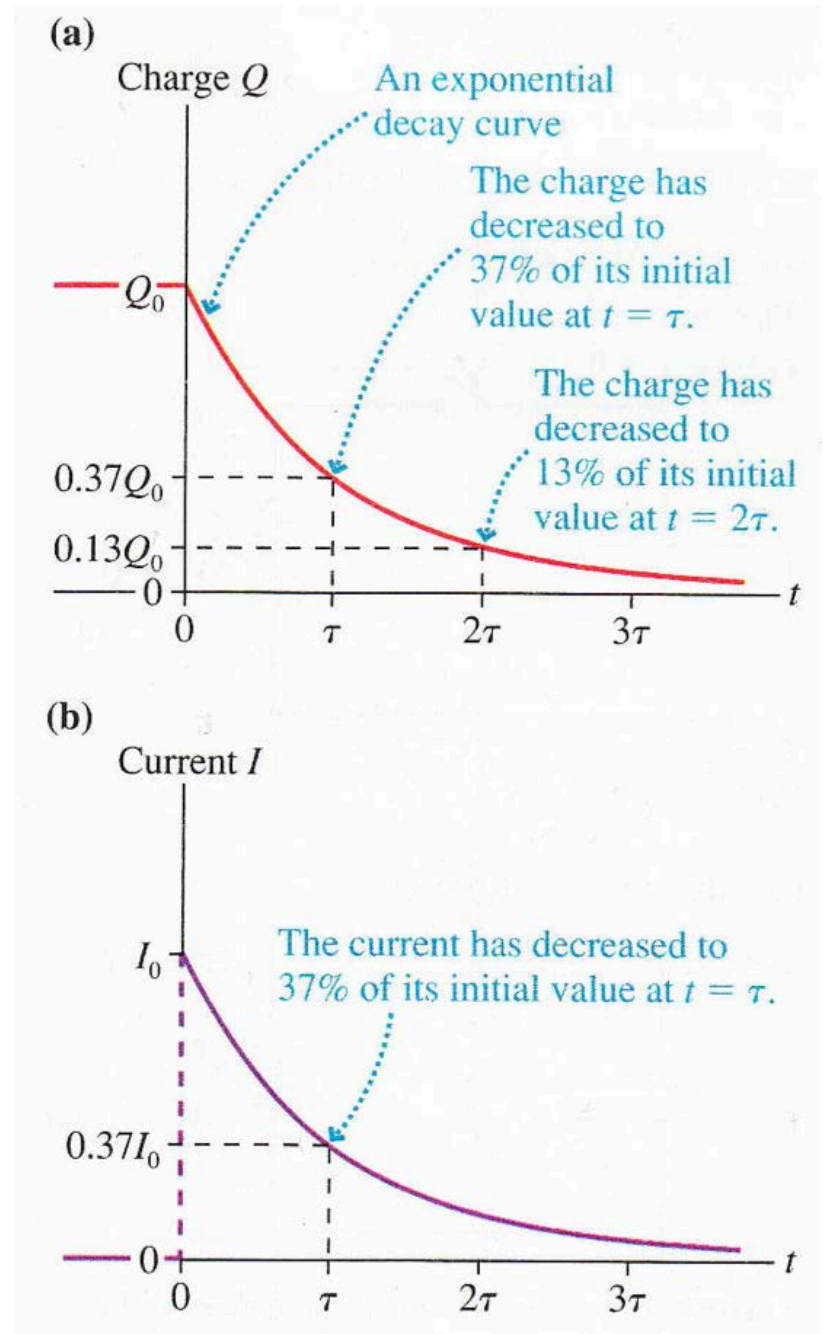

Review: RC Circuits

DC (some energy initially stored via charged capacitor) → **KCL**

$$C \frac{dV}{dt} + \frac{V}{R} = 0$$

$$V(t) = V_o e^{-\frac{t}{RC}}$$




$$\tau = RC$$

“RC time constant”


AC (sinusoidally-driven at ω , steady-state) → **KVL**

$$Z = R - \frac{i}{\omega C}$$

Think: RLC without the inductor

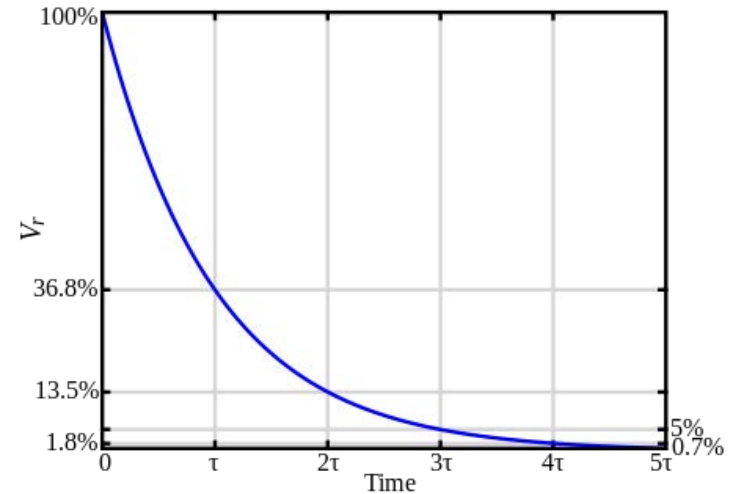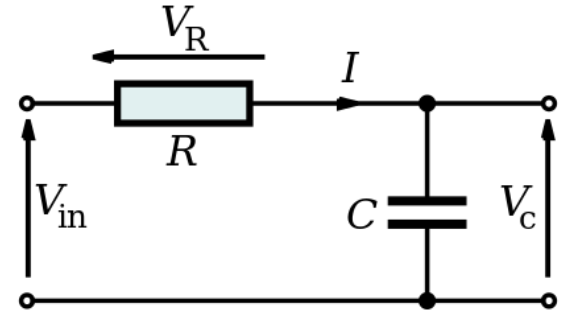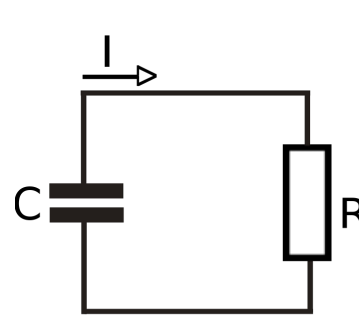





Complex impedance

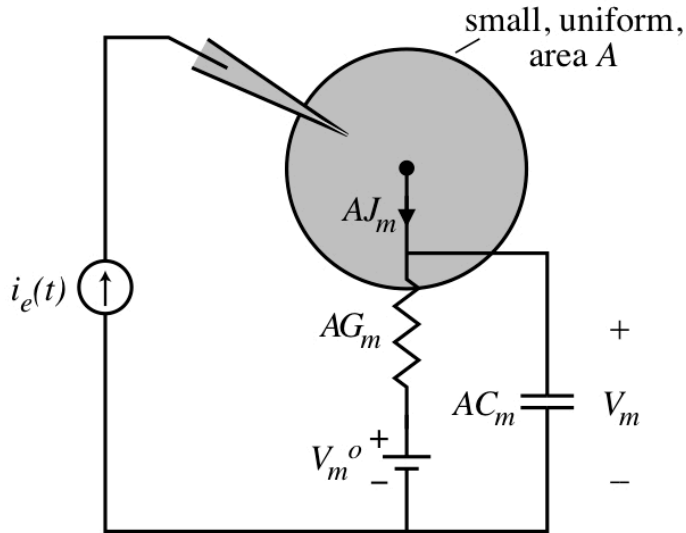

$$i_e(t) = AJ_m = AC_m \frac{dV_m}{dt} + AG_m(V_m - V_m^o)$$
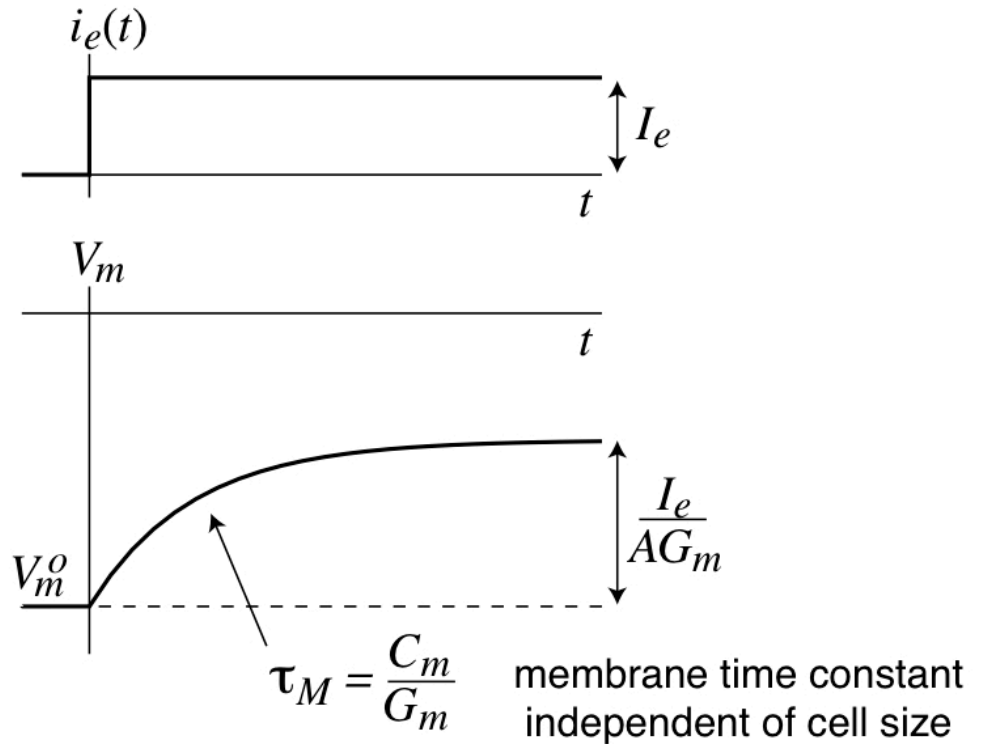
$$\frac{AC_m}{AG_m} \frac{dV_m}{dt} + V_m = V_m^o + \frac{i_e(t)}{AG_m}$$



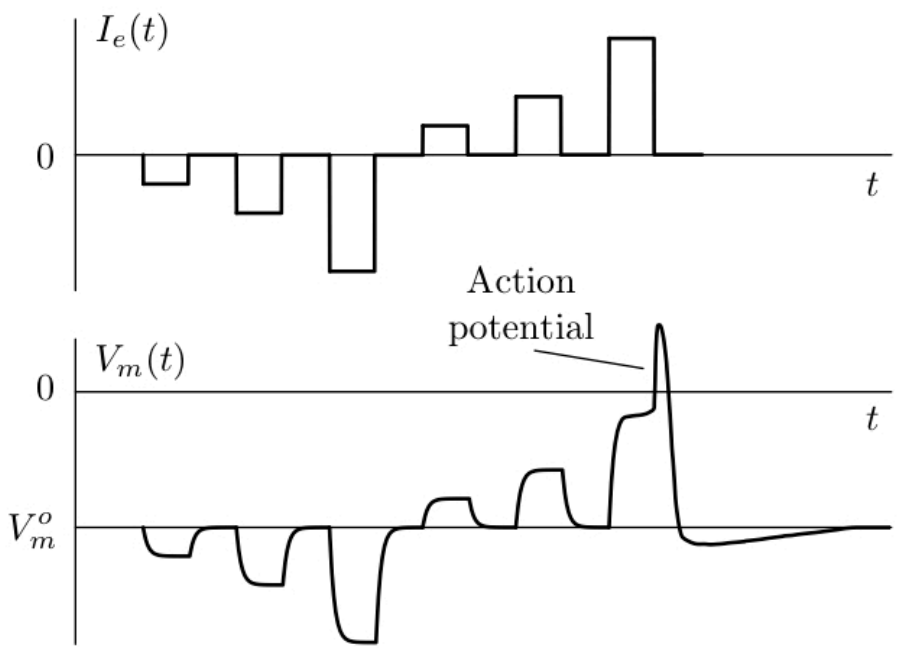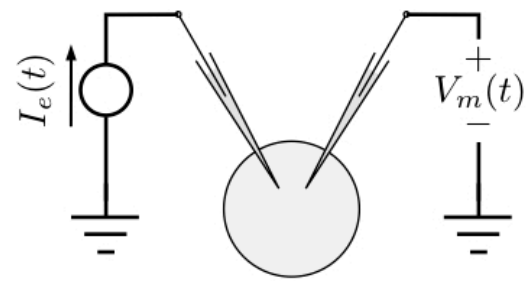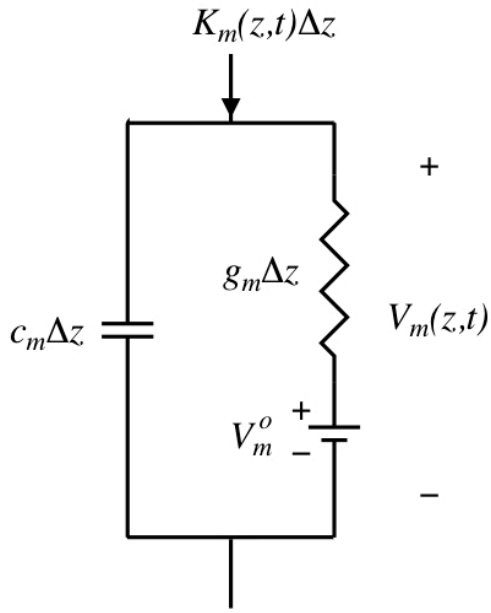

→ Delay explained
(but not action potentials yet!)

Figure 1.8

Cable Model - History

- First solved by William Thomson (aka Lord Kelvin) in ~1855
- Motivated by Atlantic submarine cable for intercontinental telegraphy

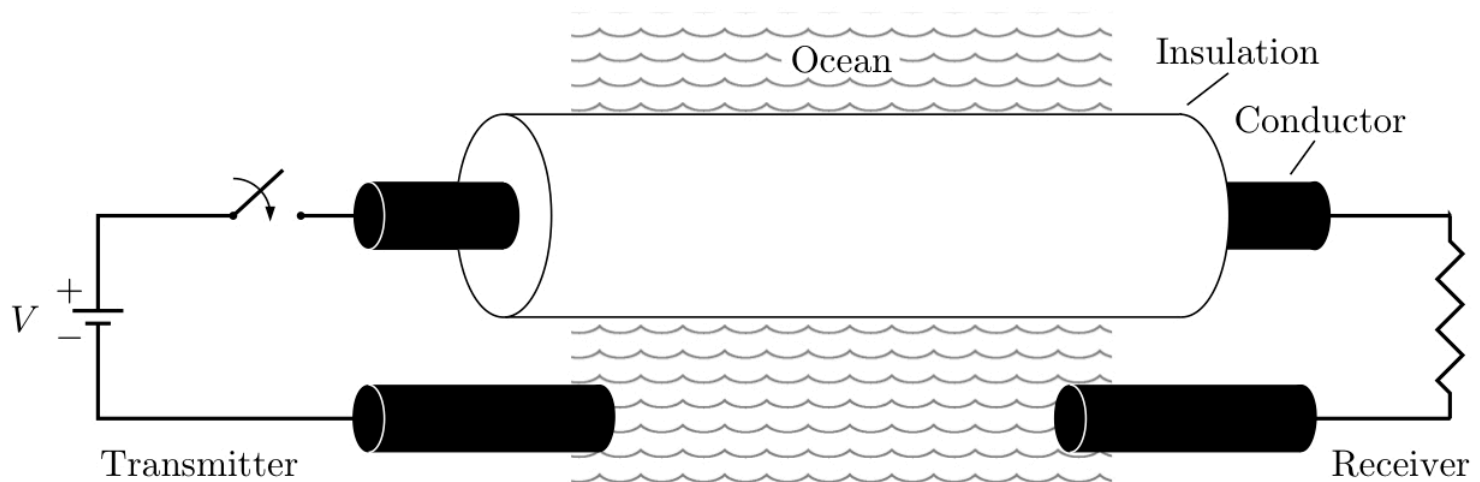


Figure 3.8

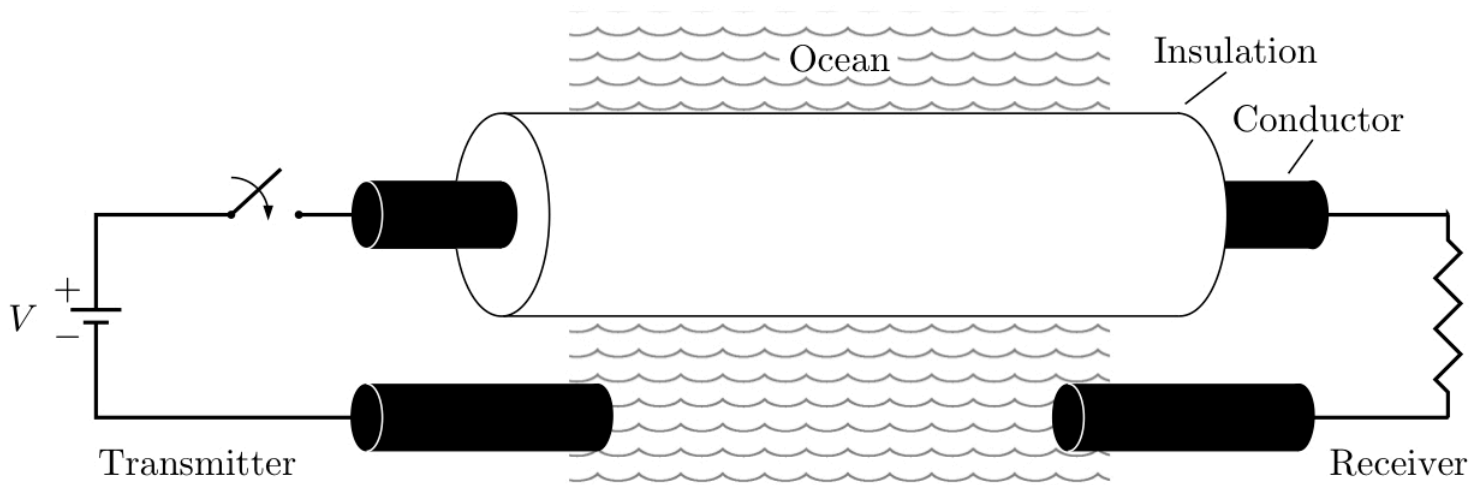


Figure 3.8

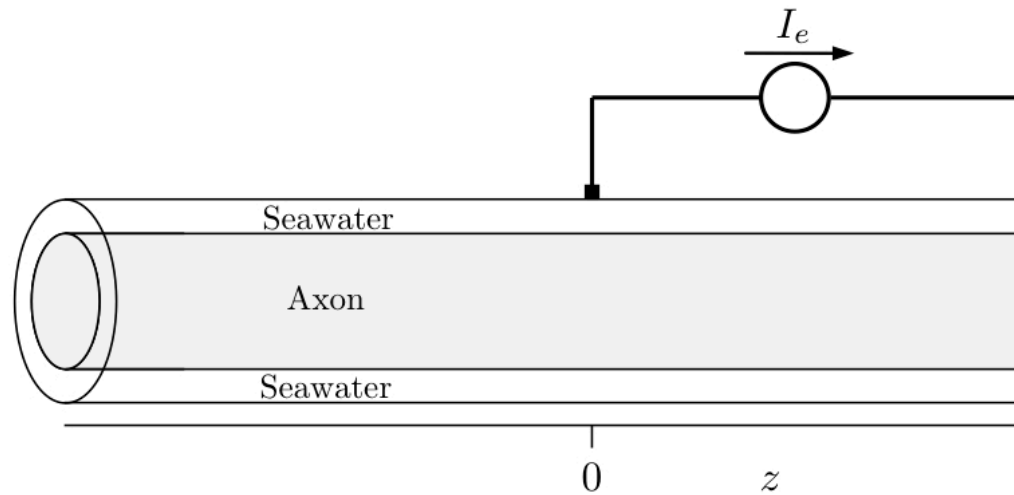


Figure 3.9

Cable Model - Overview

- Uses the Core Conductor model as underlying basis
- Assumes membrane that it can be described as a parallel capacitance and conductance
- Linear

Core Conductor Model

