

Kirchhoff's rules


C13 W10

We learned two important relations. For a capacitor

the voltage drop $\Delta V_C = \frac{Q}{C}$ and for a resistor

$$\Delta V_R = R I.$$

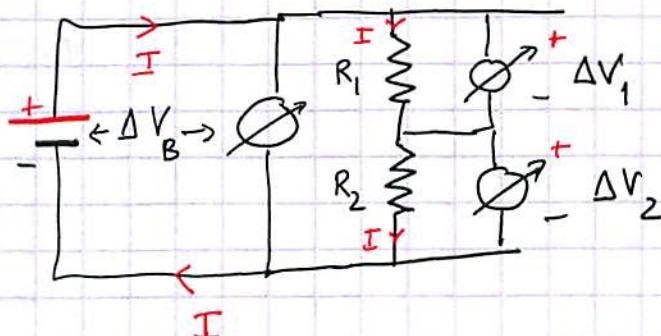for a series combination of capacitors or resistors we learned the additivity rule for voltages




$$\Delta V_B = \Delta V_1 + \Delta V_2$$

Ohm's law (sloppy version)

$$\Delta V_R = R I \quad (\text{e.g. } \Delta V_1 = R_1 I)$$

Careful version: a loop

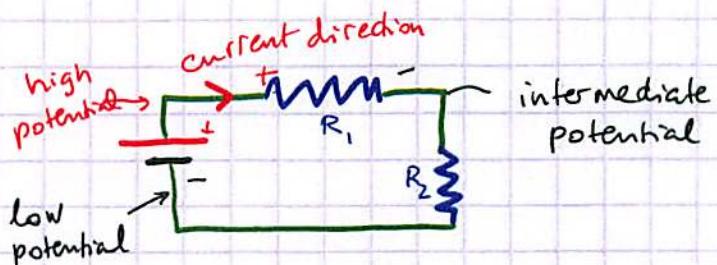

- the potential drops along the resistor: given a current direction, $\Delta V \triangleq$ from high to low
- with signs done carefully:

$$\Delta V = -RI$$

Voltages add up to zero:

$$\Delta V_B + \Delta V_1 + \Delta V_2 = 0$$

$$\Delta V_B - R_1 I - R_2 I = 0$$

$$\therefore \Delta V_B = (R_1 + R_2) I$$

Here the battery EMF ($\mathcal{E} = \Delta V_B$) raises the charges from low to high

(1) Kirchhoff Loop Rule


Dead battery?

When a battery gets old (or a rechargeable one is low)

we observe: no load $\rightarrow \Delta V_B = \mathcal{E}$ = nominal value.

apply a load + measure voltage \rightarrow it drops. Why?


Real battery:

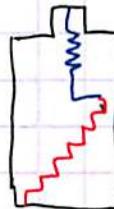

internal resistance (in series)

\mathcal{E} = EMF escalator, raises charges by
 $\mathcal{E} = \Delta V_B$

circuit:

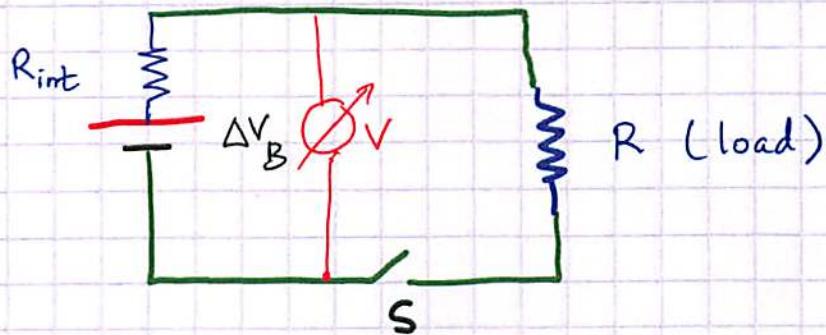

Before S is closed: Voltmeter is very good, requires almost no current to measure \rightarrow voltage drop across R_{int} is negligible $\rightarrow \Delta V_B$ is displayed!

When S is closed: a current I flows. a voltage drop occurs across R_{int} . $\Rightarrow I = \frac{\Delta V_B}{R + R_{int}}$

Voltmeter reads less than ΔV_B due to the drop across R_{int} .

Old (discharged) battery: R_{int} gets bigger!

external voltage collapses under load.

$$\text{Power} = \frac{\text{Dissipated Energy}}{\text{Unit time}}$$

Take a resistor with current I flowing \rightarrow voltage drop.

In time Δt we have charge $\Delta q = I \Delta t$ dropping in energy by $\Delta E = \Delta q \Delta V = (I \Delta t) \Delta V$ due to the potential drop by $\Delta V = RI$ (magnitudes only, no sign)

$$\text{Dissipated power } P = \frac{\Delta E}{\Delta t} = I \cdot \Delta V \quad \begin{aligned} \text{unit} &= \text{volt} \cdot \text{ampere} \\ &= \text{watt} \end{aligned}$$

$$\begin{aligned} P &= I \cdot (RI) = R I^2 \\ &= \frac{\Delta V}{R} \cdot \Delta V = \frac{\Delta V^2}{R} \end{aligned}$$

When using a resistor in a circuit \rightarrow design consideration:


what current/voltage drop combination will occur?

is the resistor "big enough" to get rid off the heat?

$\frac{1}{10}$ Watt, $\frac{1}{4}$ Watt, $\frac{1}{2}$ Watt resistors, etc.

(2) Kirchhoff junction rule

Consider a branching

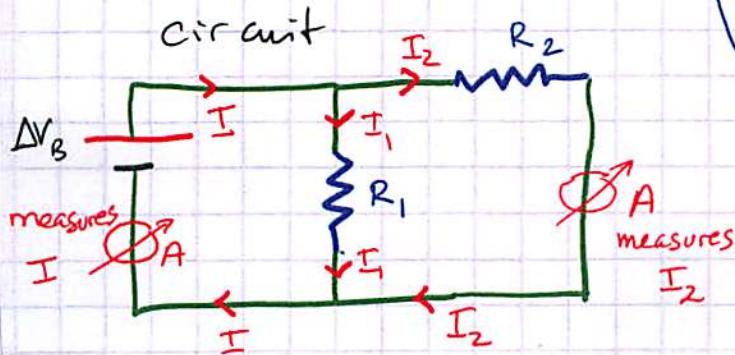

Note how current is measured:
it has to pass through the instrument.
Ideal ammeter: $R_{\text{int}} \approx 0$

Two junctions in this circuit


$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

for each junction

Parallel resistors

Take the above circuit.

What is the equivalent load?

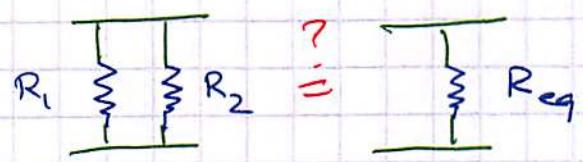

How do we solve this?

- I = I₁ + I₂ (Kirchhoff junction rule)

- $\Delta V_1 = \Delta V_2 = \Delta V_B$ (Kirchhoff loop w/o signs)

- Ohm's law 3 times: $\Delta V_B = R_{eq} I$

$$\Delta V_B = R_1 I_1 \quad \Delta V_B = R_2 I_2$$

Solve (3) for currents and use in (1):

$$\frac{\Delta V_B}{R_{eq}} = \frac{\Delta V_B}{R_1} + \frac{\Delta V_B}{R_2} \quad \therefore \text{(cancel } \Delta V_B\text{)}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

parallel resistors

→ same eqn as series capacitors

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

series resistors

→ same eqn as parallel capacitors

The idea of parallel resistors has other applications:

a radiator system pumps water through hoses with branching + hoses of different diameter

→ pipe with small cross section → bigger resistance
thicker pipe or parallel pipes → less resistance