

Magnetic field: energy content


Electric fields  $\vec{E}$  contain energy: when a capacitor with charge  $\pm Q$  on its plates is connected to a resistor, then the discharge current heats the resistor  $\rightarrow$  The electric energy associated with  $\vec{E}$  is dissipated into heat.

Can we say something similar about the  $\vec{B}$  field generated by a current passing through an inductor  $L$ ?

Turning on a current is not easy: the inductance of a coil (or even a simple wire!) generates a counter-EMF which is overcome on the time scale of  $\tau = L/R$  only. Here  $R$  is the combined resistance of the inductor (coil or wire) and the load.

What about turning off a current?

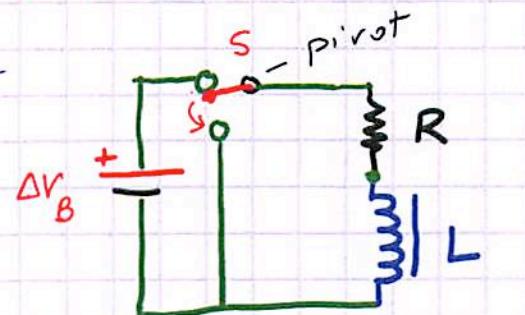Long after  $\Delta V_B$  was connected: the RL circuit is switched to a controlled discharge (as the RC was)



Idealized scenario: the switching is instantaneous (textbook discussion)

inductor  
with iron core

Kirchhoff loop law ( $S$  has closed in the discharge pos'n)

$$-R I(t) - L \frac{dI}{dt} = 0$$


$$I(t=0) = I_0 = \frac{\Delta V_B}{R}$$

$$\therefore I(t) = -\frac{L}{R} \frac{dI}{dt} = -\tau \frac{dI}{dt}$$

$$\therefore I(t) = I_0 e^{-t/\tau}$$

battery was connected for many multiples of  $\tau = L/R$  before  $S$  changed.

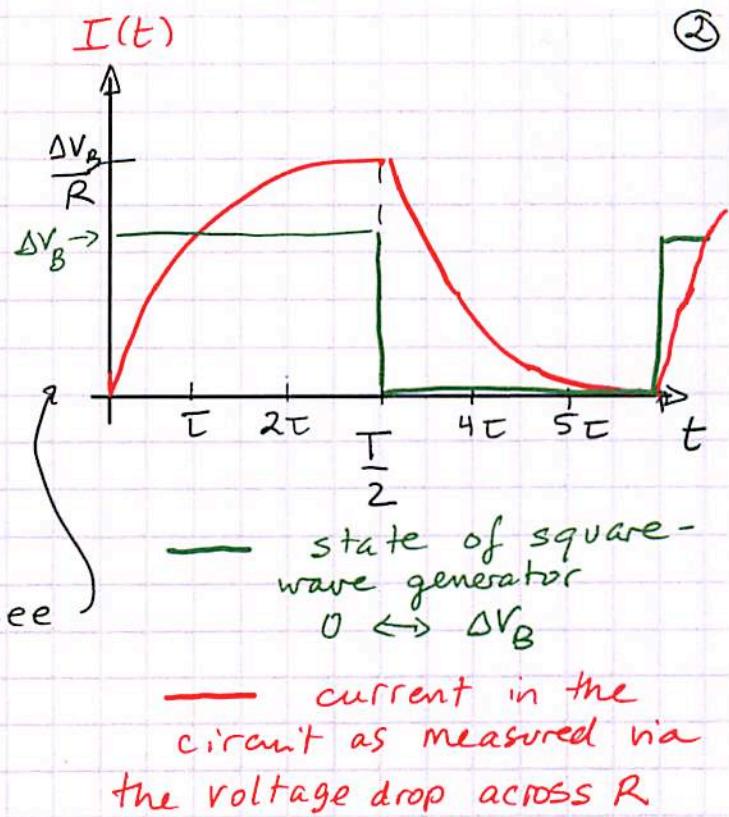Thus, if we continuously switch the battery into the circuit and then replace it with a short (a square-wave generator, except that in the low state it is not a short, but a  $50\Omega$  internal resistance), and the switching is on a time scale  $T \gg \tau = \frac{L}{R}$ , we see



This looks very benign, and follows from the equations. It raises the question: what makes the current to continue to flow after the battery was disconnected?

The  $\vec{B}$  field's inertia (according to Lenz/Faraday) is to blame. The term  $-L \frac{dI}{dt}$  represents an EMF.

$E = -\frac{d}{dt} \phi_M$  where  $\phi_M = L I$  is now providing a forward EMF (since  $\frac{dI}{dt} < 0$  for a decreasing current)


If the current were to stop suddenly, then  $\frac{dI}{dt} = -\infty$ , and a huge voltage would be generated by the inductor. Is this for real?

In fact, yes! When we use a simple battery to power an inductor, and then remove the contact by pulling the wire from a terminal  $\rightarrow$  sparks fly!

what does this mean?  $\nearrow$

Opening the contact (and not closing at  $t=0$  to make a short as discussed above) ③

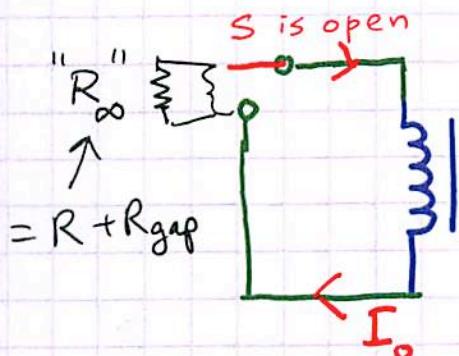creates an RL discharge circuit with  $R \rightarrow \infty$ .



Even though the circuit is broken,  $I(t)$  has to continue to flow.

The gap between the switch contacts acts like a capacitor: the contact points acquire charge  $\pm Q$ , an  $\vec{E}$

field builds up, and a discharge occurs.

Discharge: electrons ionize the air molecules  $\rightarrow$  charges can support a current  $\rightarrow R_{\infty}$  becomes finite

$Q$ : is this a tiny capacitor or a big resistor ??


Practical (electronic/electrical engineering) messages:

1) switching off currents in large inductors (motors) creates transient voltages  $E = -L \frac{dI}{dt}$  in the thousands of volts range (otherwise no sparking!) arc ing

2) switches will burn  $\rightarrow$  need protective circuits, capacitor across contact points  
↳ allows transient current to flow

3) power grid, electronic power supplies  $\rightarrow$  electrically dirty  
 $\rightarrow$  protect sensitive circuits by "voltage clamps"

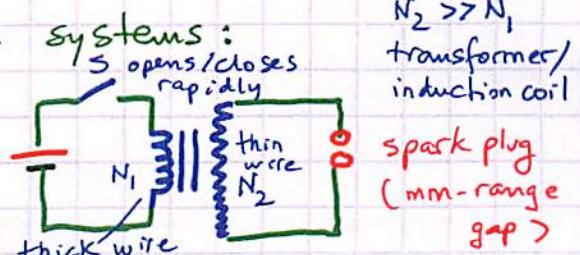
4) "pre-electronic" car ignition systems:  
use a rapidly switching primary inductor coil to generate high-voltage peaks:



# Transformers and AC circuits

Faraday's law  $\mathcal{E} = - \frac{d\phi_M}{dt} = - L \frac{dI}{dt}$  opens up interesting possibilities for non-constant electric currents.

In a transformer

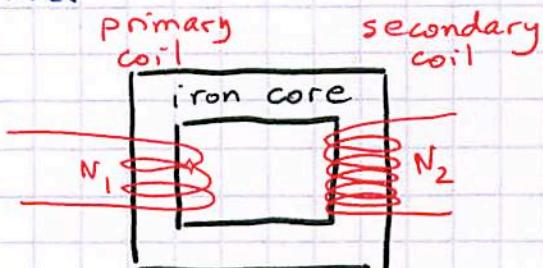

We feed the primary coil with a sinusoidal (or some other periodic) current and generate a time-varying magnetic flux  $\phi_M(t)$  which is guided by the iron core into the secondary coil. Each of the  $N_2$  secondary coil turns now generates  $\mathcal{E} = - \frac{d\phi_M}{dt}$ ; when added in series one realizes that: (ignoring the core )

at primary coil:  $\Delta V_{AC1} = - \frac{d\phi_M}{dt}$

*each turn is driven by  $\frac{1}{N_1} \Delta V_{AC}$ !*

*$N_1$  turns produce a time-varying magnetic flux  $\phi_M(t)$*

at secondary coil in each of the  $N_2$  turns:

$$\frac{d\phi_M}{dt} \Rightarrow \mathcal{E} \quad \therefore \text{in series: } N_2 \mathcal{E} \text{ is produced in total}$$

$$\Delta V_{AC2} = N_2 \frac{d\phi_M}{dt} = N_2 \frac{\Delta V_{AC1}}{N_1} \quad \therefore \Delta V_{AC2} = \frac{N_2}{N_1} \Delta V_{AC1}$$

- 1) We can step up/down time-varying voltages by adjusting the number of turns in the primary and secondary coils
- 2) Ohmic resistance in the primary causes some heating loss
- 3) Under load: more heat is produced as the current load increases

Energy (density) associated with  $\vec{B}$  (extra)

For an  $\vec{E}$  field in a capacitor:  $PE = \frac{1}{2} C \Delta V^2$ ;  $E = \frac{\Delta V}{d}$

Q: how is PE stored in a  $\vec{B}$  field?

A: We derived the "charge" cycle for an RL circuit ( $B \sim I$ )

$$I(t) = \frac{\Delta V_B}{R} (1 - e^{-t/\tau}) \quad \tau = \frac{L}{R}, \frac{\Delta V_B}{R} = I_{\max}$$

The voltage drop across the inductor  $\Delta V_L = -L \frac{dI}{dt}$

$$\Delta V_L(t) = -L \frac{\Delta V_B}{R} \left( +\frac{1}{\tau} e^{-t/\tau} \right) = -\underbrace{\Delta V_B e^{-t/\tau}}_{\substack{\text{initially } -\Delta V_B \\ \text{eventually } \rightarrow 0!}}$$

The power associated with loading the inductor:

$$P_L = |\Delta V_L| \cdot I = \frac{\Delta V_B^2}{R} \left( \underbrace{e^{-t/\tau} - e^{-2t/\tau}}_{\geq 0!} \right) \rightarrow \begin{aligned} \partial t=0 &= 0 \\ \partial t \rightarrow \infty &= 0 \end{aligned}$$

We need: PE for  $t \rightarrow \infty$  when  $I = I_{\max} = \frac{\Delta V_B}{R}$   
and  $B = B_{\max}$

$$P_L = \frac{\Delta PE}{\Delta t} \quad \therefore PE = \int_0^\infty P_L(t) dt$$

$$\int_0^\infty e^{-t/\tau} dt = -\tau e^{-t/\tau} \Big|_0^\infty = \tau; \int_0^\infty e^{-2t/\tau} dt = \frac{\tau}{2}$$

$$\therefore PE_L = \frac{\Delta V_B^2}{R} \left( \tau - \frac{\tau}{2} \right) = \frac{1}{2} \frac{\Delta V_B^2}{R} \left( \frac{L}{R} \right) = \frac{1}{2} L \frac{\Delta V_B^2}{R^2} = \frac{L}{2} I_{\max}^2$$

Thus, we found the counter-part to the energy stored  
in a capacitor:

$$PE_L = \frac{1}{2} L I^2 \quad \substack{\text{steady-state} \\ \text{current}}$$

Given that the magnetic field strength  $B \sim I$ ,

we have:  $PE_L \sim B^2$  in analogy to  $PE_C \sim E^2$

In detail:  $PE_L = \frac{1}{2} L \left( \frac{B d}{\mu_0 N} \right)^2 = \frac{1}{2} \underbrace{\left( \frac{\mu_0 N^2 A}{d} \right)}_{L_{\text{solenoid}}} \frac{d^2}{\mu_0^2 N^2} B^2 = \frac{B^2}{2\mu_0} \underbrace{(Ad)}_{\substack{\text{solenoid} \\ \text{volume}}}$

$$B_{\text{solenoid}} = \frac{\mu_0 N I}{d}$$