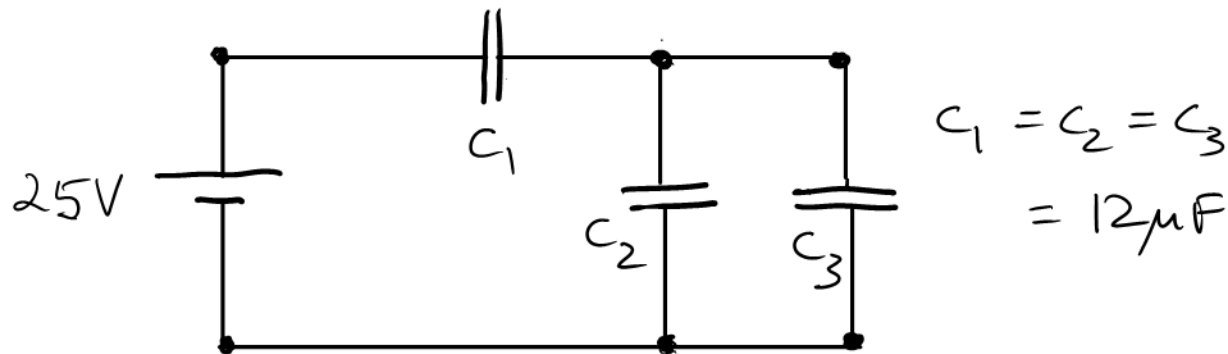


PhysicsTutor<sup>mh</sup>

Capacitor network

# Problem:


- What is the potential drop across the first capacitor  $C_1$ ?



Relevant ideas:

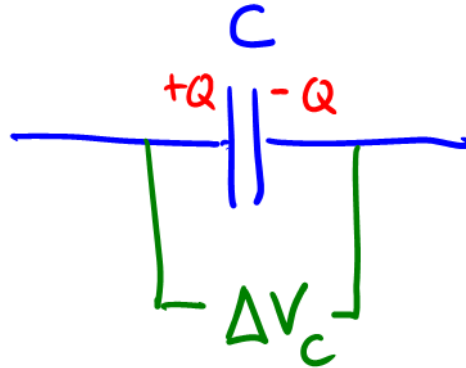
# Relevant ideas:

- Voltage-charge relationship:  $\Delta V_C = Q/C$  .



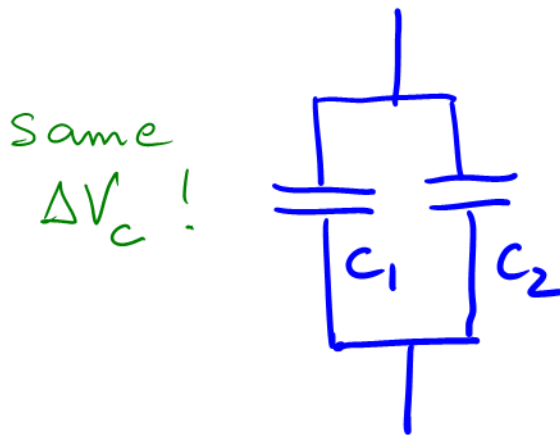
# Relevant ideas:

- Voltage-charge relationship:  $\Delta V_C = Q/C$ .
- Equivalent capacitance for series and parallel capacitor combinations.



$$C_{eq} = C_1 + C_2$$

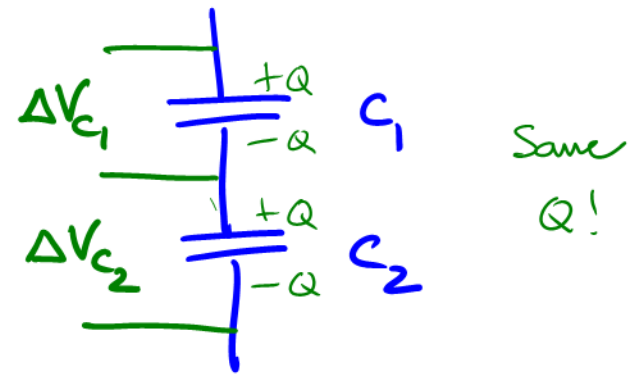

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$


$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

# Relevant ideas:

- Voltage-charge relationship:  $\Delta V_C = Q/C$ .
- Equivalent capacitance for series and parallel capacitor combinations.
- Series capacitors are charged to the same  $Q$ , since the same current passes through them.

time scale  
for charge  
current:

$$\tau = R_{int} \cdot C_{eq}.$$

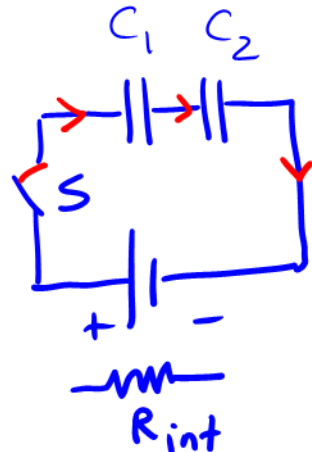

switch closes:

current flows for a short  
time to displace charge  $Q$

→ charge displacement  
is the same for  $C_1$  &  $C_2$

# Equations associated with ideas:

$$C_{23}^{eq} = C_2 + C_3$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{23}^{eq}}$$

$$\Delta V_C = \frac{Q}{C}$$

$$\Delta V_B + \Delta V_1 + \Delta V_{23}^{eq} = 0$$

# Strategy




# Strategy

- Replace the parallel pair by a single capacitor with the capacitances added.
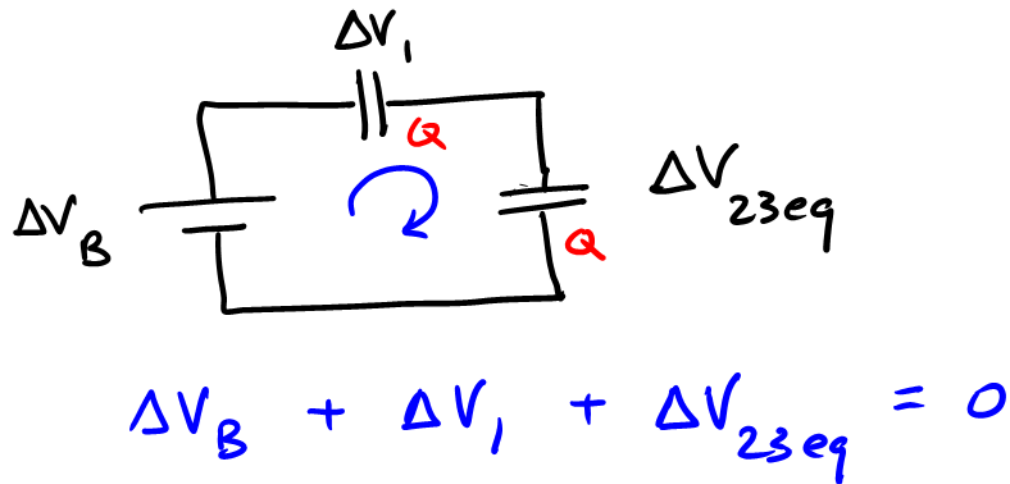
# Strategy

- Replace the parallel pair by a single capacitor with the capacitances added.
- The series capacitor circuit splits the battery to different voltage drops.



# Strategy

- Replace the parallel pair by a single capacitor with the capacitances added.
- The series capacitor circuit splits the battery to different voltage drops.
- The charge is the same in both series-connected capacitors, this allows to determine the voltage split.

# Solution

# Solution

- $C_{23}^{e_1} = (12 + 12) \mu F = 24 \mu F$

---


# Solution

- $C_{23}^{eq} = (12 + 12) \mu F = 24 \mu F$

---

- $C_{eq} = \frac{C_{23}^{eq} \cdot C_1}{C_{23}^{eq} + C_1} = \frac{24 \cdot 12}{24 + 12} \mu F = 8.0 \mu F$

---

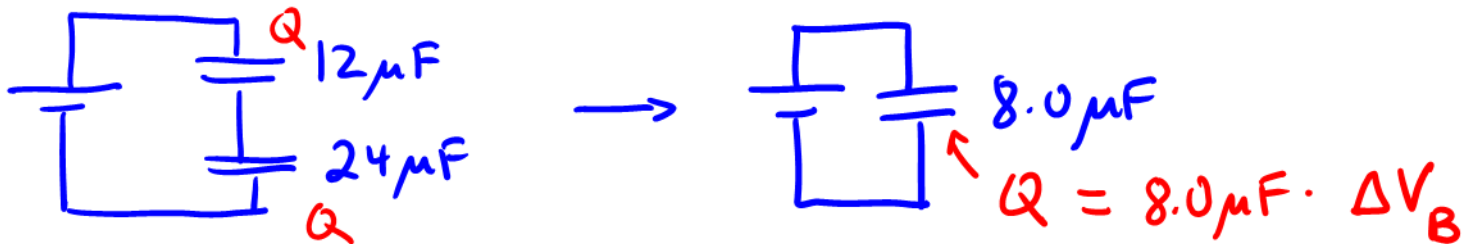

# Solution

- $C_{23}^{eq} = (12 + 12) \mu F = 24 \mu F$


---

- $C_{eq} = \frac{C_{23}^{eq} \cdot C_1}{C_{23}^{eq} + C_1} = \frac{24 \cdot 12}{24 + 12} \mu F = 8.0 \mu F$

---

- $Q = C_{eq} \Delta V_B = 8.0 \times 10^{-6} \cdot 25 \text{ FV} = 2.0 \times 10^{-4} \text{ C}$

---

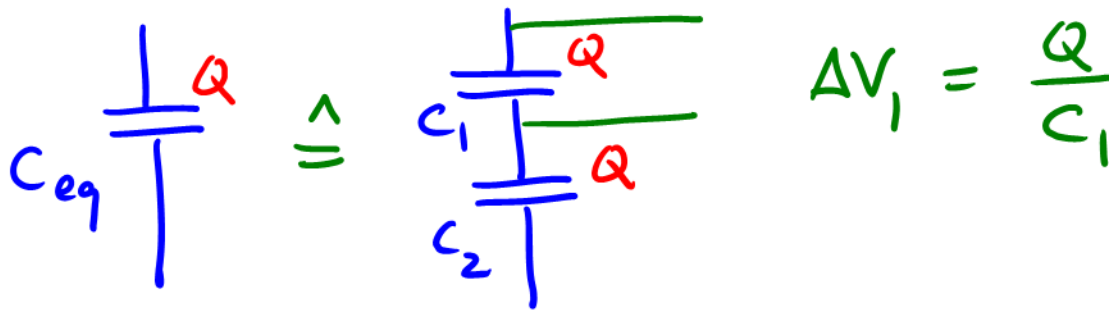

# Solution

- $C_{23}^{eq} = (12 + 12) \mu F = 24 \mu F$

---

- $C_{eq} = \frac{C_{23}^{eq} \cdot C_1}{C_{23}^{eq} + C_1} = \frac{24 \cdot 12}{24 + 12} \mu F = 8.0 \mu F$

---

- $Q = C_{eq} \Delta V_B = 8.0 \times 10^{-6} \cdot 25 \text{ FV} = 2.0 \times 10^{-4} \text{ C}$

---

- $\Delta V_1 = \frac{Q}{C_1} = \frac{2.0 \times 10^{-4} \text{ C}}{12 \times 10^{-6} \text{ F}} = 16.7 \text{ V} = 17.0 \text{ V}$

---

cross check:  $\Delta V_2 = \frac{Q}{C_2} = \frac{2 \times 10^{-4} \text{ C}}{24 \mu F} = 8.33 \text{ V}$

$= (25 - 16.67) \text{ V}$

