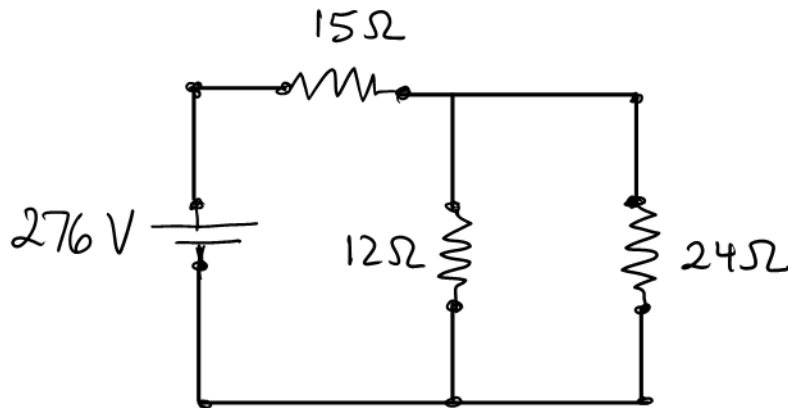


PhysicsTutor ^{mh}

Resistor Circuit

Problem:


- How much current flows through the battery in the given circuit?
- What is the current in the $12\ \Omega$ resistor?



Relevant ideas:

Relevant ideas:

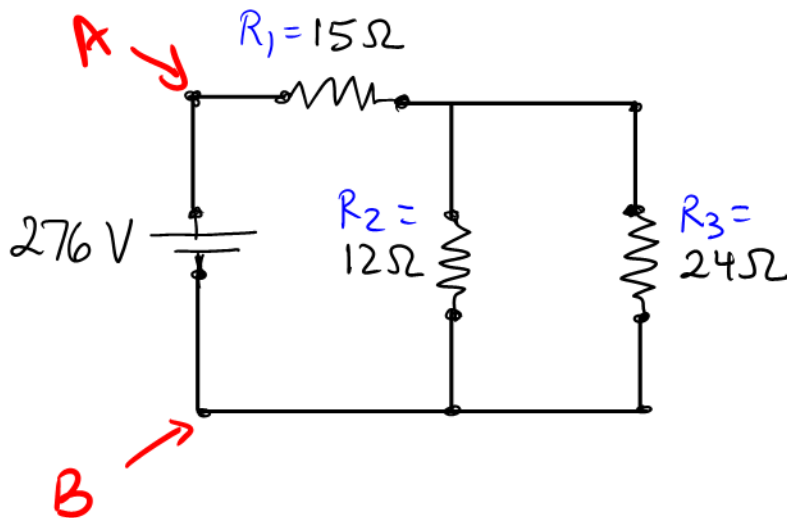- Equivalent resistance for the entire circuit.





$$R_{AB} = R_{eq}$$

R_{23}^{eq} : R_2 / R_3
are parallel

R_{AB} : R_1 and R_{23}^{eq}
are in series

Relevant ideas:

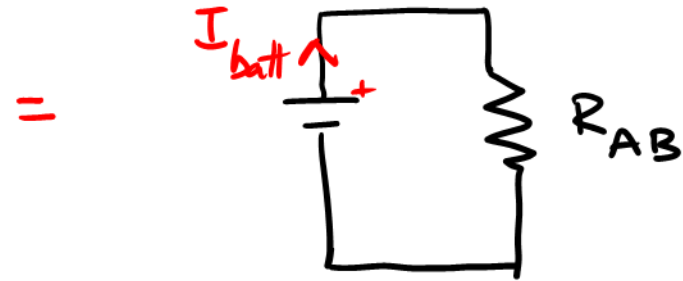
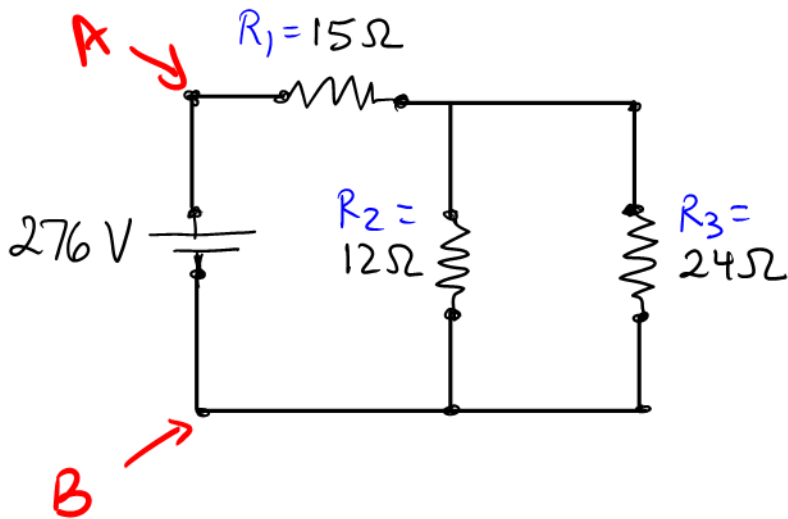
- Equivalent resistance for the entire circuit.
- Use Ohm's law for the equivalent resistance.



$$\Delta V_B = R_{AB} \cdot I_{\text{batt}}$$

Relevant ideas:

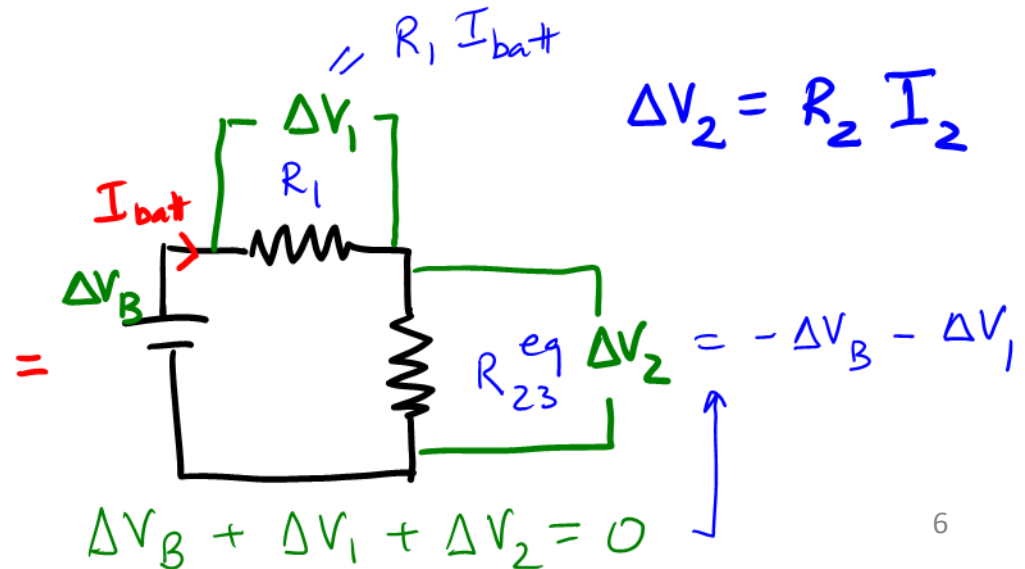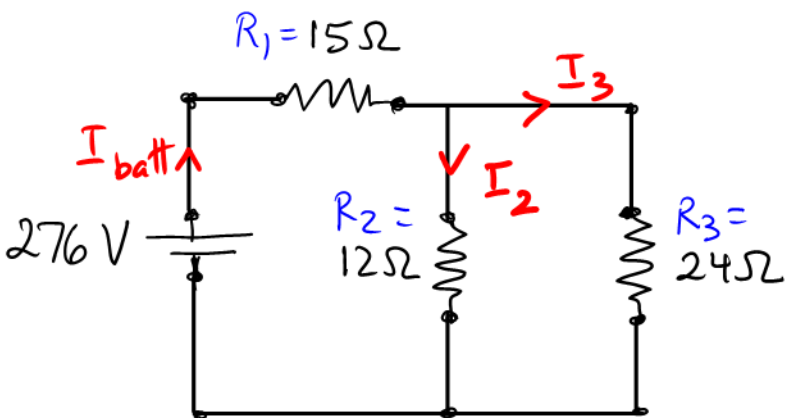- Equivalent resistance for the entire circuit.
- Use Ohm's law for the equivalent resistance.
- Kirchhoff junction and loop rules:
- Voltage drop across 12Ω resistor?
- Again Ohm's law.



Equations associated with ideas:

series - R :



$$R_{eq} = R_1 + R_2$$

parallel - R :



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\therefore R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


Ohm: $\Delta V_i = R_i I_i$

Kirchhoff loop :



$$\Delta V_B + \Delta V_1 + \Delta V_2 = 0$$

Kirchhoff junction :

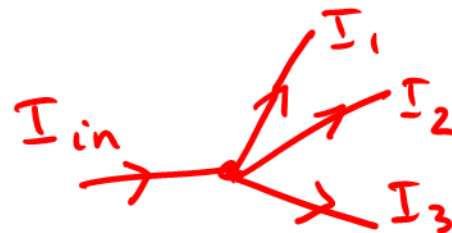

$$I_{in} = I_1 + I_2 + I_3$$

Strategy

Strategy

- Parallel-resistor pair (12Ω and 24Ω) – get their equivalent resistance.

Strategy

- Parallel-resistor pair (12Ω and 24Ω) – get their equivalent resistance.
- $15\ \Omega$ resistor is in series with the parallel pair.

Strategy

- Parallel-resistor pair (12Ω and 24Ω) – get their equivalent resistance.
- $15\ \Omega$ resistor is in series with the parallel pair.
- Battery current splits after the $15\ \Omega$ resistor.

Strategy

- Parallel-resistor pair (12Ω and 24Ω) – get their equivalent resistance.
- 15Ω resistor is in series with the parallel pair.
- Battery current splits after the 15Ω resistor.
- Voltage drops across ($12/24\Omega$) resistor pair and across (15Ω) resistor add up to ΔV_B . Calculate them from Ohm's law, then get the current through (12Ω) resistor from Ohm.

Solution

Solution

- $R_{23}^{eq} = \frac{R_2 R_3}{R_2 + R_3} = \frac{12 \cdot 24}{12 + 24} \Omega = 8.0 \Omega$

Solution

- $R_{23}^{eq} = \frac{R_2 R_3}{R_2 + R_3} = \frac{12 \cdot 24}{12 + 24} \Omega = 8.0 \Omega$

- $R_{AB} = R_1 + R_{23}^{eq} = 15 + 8.0 \Omega = 23 \Omega$; $I_B = \frac{276V}{23\Omega} = 12 A$

Solution

- $R_{23}^{eq} = \frac{R_2 R_3}{R_2 + R_3} = \frac{12 \cdot 24}{12 + 24} \Omega = 8.0 \Omega$

- $R_{AB} = R_1 + R_{23}^{eq} = 15 + 8.0 \Omega = 23 \Omega ; I_B = \frac{276V}{23\Omega} = 12 A$

- $|\Delta V_1| = R_1 I_B = 180 V \therefore |\Delta V_2| = \Delta V_B - |\Delta V_1| = 96 V$

Solution

- $R_{23}^{eq} = \frac{R_2 R_3}{R_2 + R_3} = \frac{12 \cdot 24}{12 + 24} \Omega = 8.0 \Omega$

- $R_{AB} = R_1 + R_{23}^{eq} = 15 + 8.0 \Omega = 23 \Omega$; $I_B = \frac{276V}{23\Omega} = 12 A$

- $|\Delta V_1| = R_1 I_B = 180 V \therefore |\Delta V_2| = \Delta V_B - |\Delta V_1| = 96 V$

- $I_2 = \frac{96V}{12\Omega} = 8.0 A$

cross check: $I_3 = (12 - 8.0) A = 4.0 A$ by junction rule

$$\Delta V_3 = \Delta V_2 = 96 V$$

$$R_3 \cdot I_3 = 24 \Omega \cdot 4.0 = 96 V$$

✓