


# PhysicsTutor<sup>mh</sup>

Crazy circuit

Giambattista 18.68
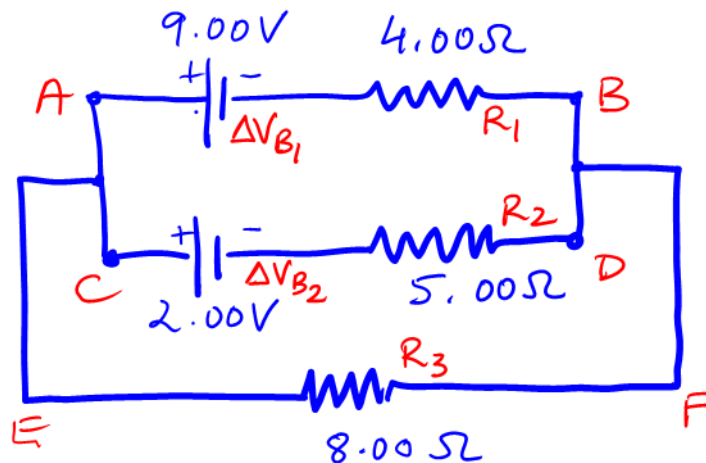
# Problem:

- At what rate is electric energy converted into heat in the  $4.00\ \Omega$  and  $5.00\ \Omega$  resistors in the diagram?



Relevant ideas:

# Relevant ideas:

- Power = Energy/Time. Rate of energy conversion = power dissipated.

heat = energy transfer

mechanical power: how much work has a force done per unit time.

electric motor: converts electric energy into mechanical at some rate  $\rightarrow$  power.

resistor: converts electrical energy into heat at some rate  $\rightarrow$  power dissipated.

# Relevant ideas:

- Power = Energy/Time. Rate of energy conversion = power dissipated.
- Power = Voltage times Current. (1 W = 1 V A)

$$P_i = \Delta V_i I_i = \frac{\Delta V_i^2}{R_i} = R_i I_i^2$$


↑  
we need the  
currents "only"

# Relevant ideas:

- Power = Energy/Time. Rate of energy conversion = power dissipated.
- Power = Voltage times Current. (1 W = 1 V A)
- We need the AB and CD currents (which are the battery currents), also need the relevant resistor voltage drops.

needed:  $P_1 = R_1 I_1^2$ ,  $P_2 = R_2 I_2^2$

$I_1 + I_2 = I_3$  junction

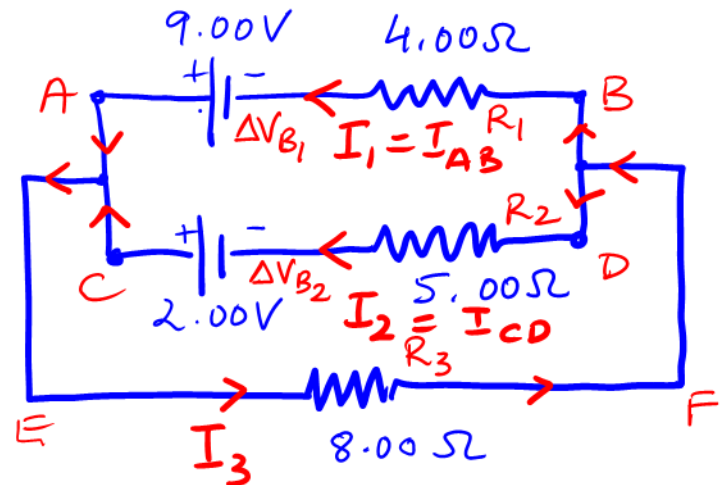

# Relevant ideas:


- Power = Energy/Time. Rate of energy conversion = power dissipated.
- Power = Voltage times Current. ( $1 \text{ W} = 1 \text{ V A}$ )
- We need the AB and CD currents (which are the battery currents), also need the relevant resistor voltage drops.
- Kirchhoff's rules are needed to sort out what's going on (multiple loops, also junctions).

# Equations associated with ideas:

$$P_1 = R_1 I_1^2$$

$$P_2 = R_2 I_2^2$$
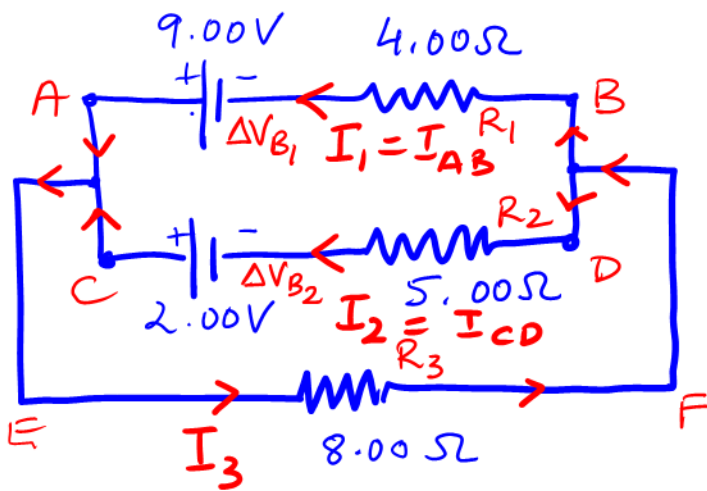
$$I_3 = I_1 + I_2 \quad \textcircled{1}$$



Ohm carefully

$$\Delta V = -RI \quad (\text{drop})$$

Loop AEFB, start at battery:  
used  $\textcircled{1}$

$$9 - 8(I_1 + I_2) - 4I_1 = 0$$

Loop CEF D, start at battery:  
used  $\textcircled{2}$

$$2 - 8(I_1 + I_2) - 5I_2 = 0$$

2 eq's 2 unknowns  $\rightarrow$  problem solved

3<sup>rd</sup> loop (consistency check) ACDB:

$$9 - 2 + 5I_2 - 4I_1 = 0$$



# Strategy


# Strategy

- Define currents in the three branches and relate them using the junction rule.

$$I_3 = I_1 + I_2$$
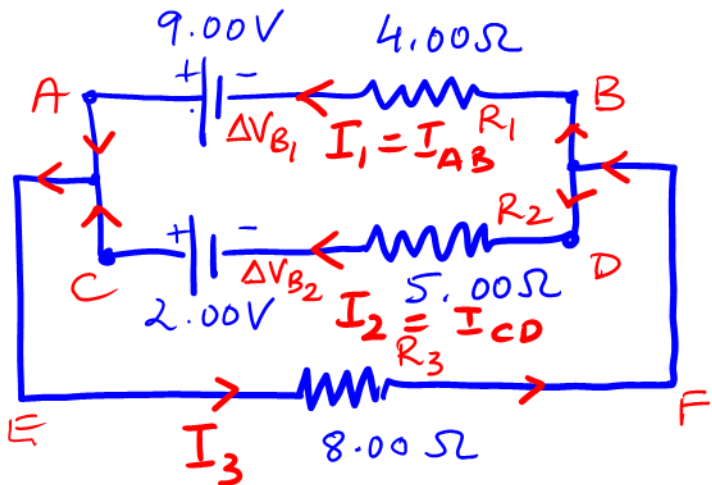
# Strategy

- Define currents in the three branches and relate them using the junction rule.
- Formulate several loop rule relations, but watch out for redundancies.



Loop AEFB, start at battery:  
used ①

$$9 - 8(I_1 + I_2) - 4I_1 = 0$$

Loop CEFD, start at battery:  
used ①

$$2 - 8(I_1 + I_2) - 5I_2 = 0$$

3<sup>rd</sup> loop (consistency check) ACDB:

$$9 - 2 + 5I_2 - 4I_1 = 0$$

# Strategy

- Define currents in the three branches and relate them using the junction rule.
- Formulate several loop rule relations, but watch out for redundancies.
- Two unknown currents and two unknown voltages are to be determined; we need four conditions. *→ using Ohm's law twice we reduced the problem to finding  $I_1$  and  $I_2$ . Then we used  $I_3 = I_1 + I_2$  and two of the three obvious loops.*

# Solution

# Solution

- $$\begin{array}{l} 9 - 8(I_1 + I_2) - 4I_1 = 0 \\ 2 - 8(I_1 + I_2) - 5I_2 = 0 \end{array} \left. \vphantom{\begin{array}{l} 9 - 8(I_1 + I_2) - 4I_1 = 0 \\ 2 - 8(I_1 + I_2) - 5I_2 = 0 \end{array}} \right\} \begin{array}{l} 12I_1 = 9 - 8I_2 \quad | :3 \\ 8I_1 = 2 - 13I_2 \quad | :2 \end{array}$$

---

# Solution

- $$\left. \begin{array}{l} 9 - 8(I_1 + I_2) - 4I_1 = 0 \\ 2 - 8(I_1 + I_2) - 5I_2 = 0 \end{array} \right\} \begin{array}{l} 12I_1 = 9 - 8I_2 \quad | :3 \\ 8I_1 = 2 - 13I_2 \quad | :2 \end{array}$$

---

- $$\frac{9 - 8I_2}{3} = \frac{2 - 13I_2}{2} \quad \therefore \quad I_2 = -\frac{12}{23} \text{ A} = -0.522 \text{ A}$$

---

# Solution

- $$\left. \begin{aligned} 9 - 8(I_1 + I_2) - 4I_1 &= 0 \\ 2 - 8(I_1 + I_2) - 5I_2 &= 0 \end{aligned} \right\} \begin{aligned} 12I_1 &= 9 - 8I_2 \quad | :3 \\ 8I_1 &= 2 - 13I_2 \quad | :2 \end{aligned}$$

---

- $$\frac{9 - 8I_2}{3} = \frac{2 - 13I_2}{2} \quad \therefore \quad I_2 = -\frac{12}{23} \text{ A} = -0.522 \text{ A}$$

---

- $$I_1 = \frac{2 - 13I_2}{8} \quad \therefore \quad I_1 = \frac{101}{92} \text{ A} = 1.10 \text{ A}$$

---



# Solution

$$\bullet \left. \begin{array}{l} 9 - 8(I_1 + I_2) - 4I_1 = 0 \\ 2 - 8(I_1 + I_2) - 5I_2 = 0 \end{array} \right\} \begin{array}{l} 12I_1 = 9 - 8I_2 \quad | :3 \\ 8I_1 = 2 - 13I_2 \quad | :2 \end{array}$$

---

$$\bullet \frac{9 - 8I_2}{3} = \frac{2 - 13I_2}{2} \quad \therefore I_2 = -\frac{12}{23} \text{ A} = -0.522 \text{ A}^*$$

---

$$\bullet I_1 = \frac{2 - 13I_2}{8} \quad \therefore I_1 = \frac{101}{92} \text{ A} = 1.10 \text{ A}$$

---

$$\bullet P_1 = R_1 I_1^2 = 4.82 \text{ W} \quad P_2 = R_2 I_2^2 = 1.36 \text{ W}$$

---

The not-so-good news  $\rightarrow$  battery 2 experiences  
a reverse current  $\rightarrow$  very undesirable operation  
 $\rightarrow$  "crazy" circuit