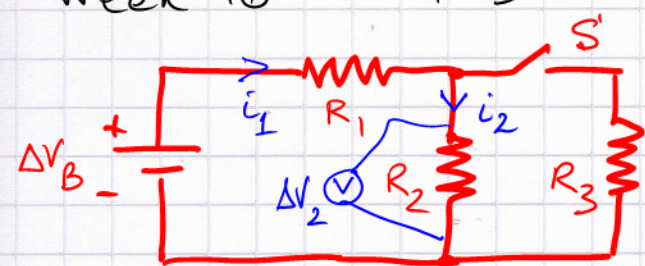


Week 16

19.23



$$R_1 = R_2 = R_3 = R$$

S closes $\rightarrow$

changes in $\begin{matrix} \nearrow i_1 & \textcircled{A} \\ \rightarrow \Delta V_2 & \textcircled{B} \\ \searrow i_2 & \textcircled{C} \end{matrix}$

Solution

With S open : $i_1 = i_2$ controlled by $R_{12} = R_1 + R_2$

$$\therefore R_{12} = 2R$$

$$\therefore i_1 = i_2 = \frac{\Delta V_B}{2R}$$

$$\therefore i_1^{\text{before}} = i_2^{\text{before}} = \frac{\Delta V_B}{2R} \quad \left(= \frac{\Sigma}{2R} \right)$$

S closes $\therefore R_1$ in series with R_{23}^{eq}

$$R_{23}^{\text{eq}} : \text{parallel} \therefore \frac{1}{R_{23}^{\text{eq}}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{R} + \frac{1}{R} = \frac{2}{R}$$

$$\therefore R_{23}^{\text{eq}} = \frac{R}{2} \therefore R_{\text{tot}} = R + \frac{R}{2} = \frac{3}{2} R$$

$$\therefore i_1 = i_{\text{tot}} = \frac{\Delta V_B}{R_{\text{tot}}} = \frac{\Delta V_B}{\frac{3}{2} R}$$

$$\frac{i_1^{\text{after}}}{i_1^{\text{before}}} = \frac{\frac{2}{3} \Delta V_B / R}{\frac{1}{2} \Delta V_B / R} = \frac{4}{3} \therefore \text{current } i_1 \text{ increases by a factor of } \frac{4}{3} \quad \textcircled{A}$$


$$\textcircled{B} : \Delta V_2^{\text{before}} = \frac{1}{2} \Delta V_B \quad (\text{voltage divides with } R_1 = R_2)$$

$$\Delta V_2^{\text{after}} : \text{voltage divides } R_1 \text{ \& } R_{23}^{\text{eq}} = \frac{R}{2} \therefore \Delta V_2^{\text{after}} = \frac{1}{3} \Delta V_B$$

$$\text{ratio} : \frac{1}{3} : \frac{1}{2} = \frac{2}{3} \quad \Delta V_2^{\text{after}} = \frac{2}{3} \Delta V_2^{\text{before}}$$


$$\textcircled{C} : i_2^{\text{after}} = \frac{1}{2} i_1^{\text{after}} = \frac{1}{2} \cdot \frac{4}{3} i_1^{\text{before}} = \frac{2}{3} i_1^{\text{before}} = \frac{2}{3} i_2^{\text{before}}$$

19.33

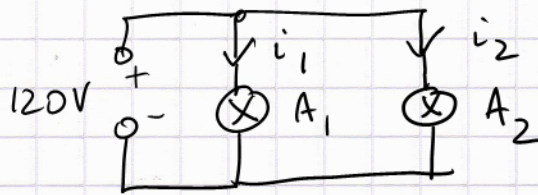

$$i_1 = 2.0 \text{ A}$$

$$i_2 = 3.5 \text{ A}$$

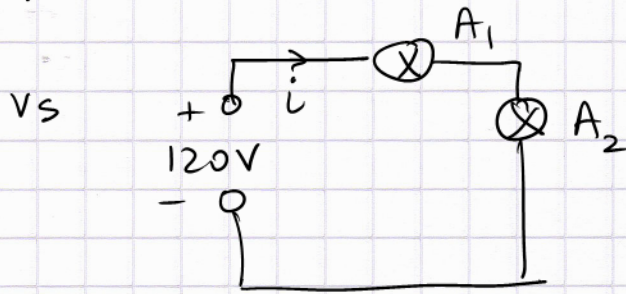

Solution

Ohm's law: $R_1 = \frac{120 \text{ V}}{2.0 \text{ A}} = 60 \Omega$, $R_2 = \frac{120 \text{ V}}{3.5 \text{ A}} = \frac{240}{7.0} \Omega$


series connection: $R_{eq} = R_1 + R_2 = \left(60 + \frac{240}{7.0}\right) \Omega$

$$i = \Delta V / R_{eq} = \frac{120 \text{ V}}{\frac{420 + 240}{7.0} \Omega} = \frac{7.0 \cdot 6}{21 + 12} \text{ A}$$

$$= \frac{42}{33} \text{ A} = 1.3 \text{ A}$$

→ less current than was passing through either appliance when connected properly (in parallel)

19.38

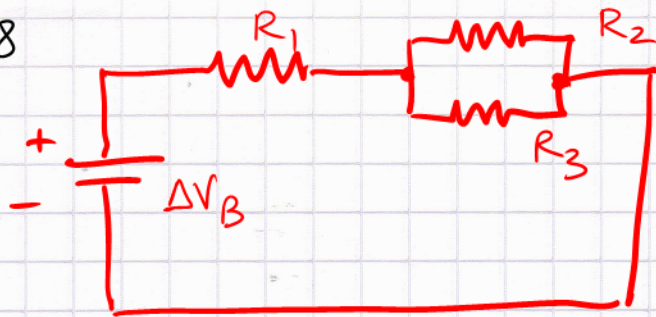

$$R_{23}^{eq} = \frac{R_2 R_3}{R_2 + R_3}$$

$$R_{tot}^{eq} = R_1 + R_{23}^{eq}$$

$$= \frac{R_1(R_2 + R_3) + R_2 R_3}{R_2 + R_3}$$

$$R_{tot}^{eq} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 + R_3}$$

$$i = \frac{\Delta V_B}{R_{tot}^{eq}} = \frac{\Delta V_B (R_2 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

values: $R_1 = 2.4 \text{ k}\Omega$; $R_2 = 1.4 \text{ k}\Omega$, $R_3 = 4.5 \text{ k}\Omega$

$$\Delta V_B = 1.5 \text{ V}$$


$$R_{23}^{eq} = 1.1 \text{ k}\Omega$$

$$R_{tot}^{eq} = (1.1 + 2.4) \text{ k}\Omega = 3.5 \text{ k}\Omega$$

$$i_1 = \frac{1.5 \text{ V}}{3.5 \text{ k}\Omega} = 0.43 \text{ mA}$$

This is also the current through the battery!

19.40

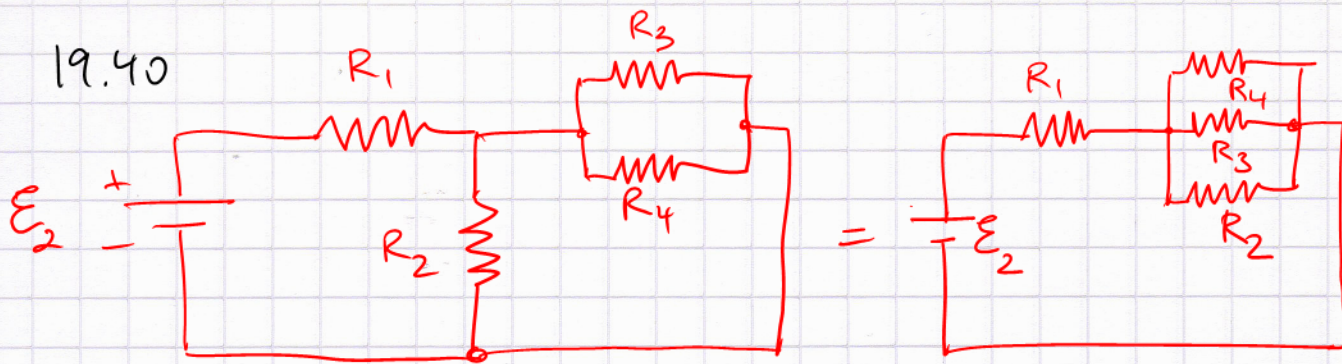

$$\therefore R_{\text{tot}}^{\text{eq}} = R_1 + R_{234}^{\text{eq}}$$

$$\frac{1}{R_{234}^{\text{eq}}} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \quad i = \frac{\Delta V_B}{R_{\text{tot}}^{\text{eq}}}$$


$$\frac{1}{R_{234}^{\text{eq}}} = \left(\frac{1}{1.4} + \frac{1}{4.5} + \frac{1}{6.0} \right) \frac{1}{\text{k}\Omega}$$

$$R_{234}^{\text{eq}} = 0.906 \text{ k}\Omega \rightarrow 900 \Omega$$

$$R_{\text{tot}}^{\text{eq}} = 2.4 \text{ k}\Omega + 0.9 \text{ k}\Omega = 3.3 \text{ k}\Omega$$

$$i_1 = i_{\text{batt}} = \frac{3.0 \text{ V}}{3.3 \text{ k}\Omega} = 0.91 \text{ mA}$$

19.58

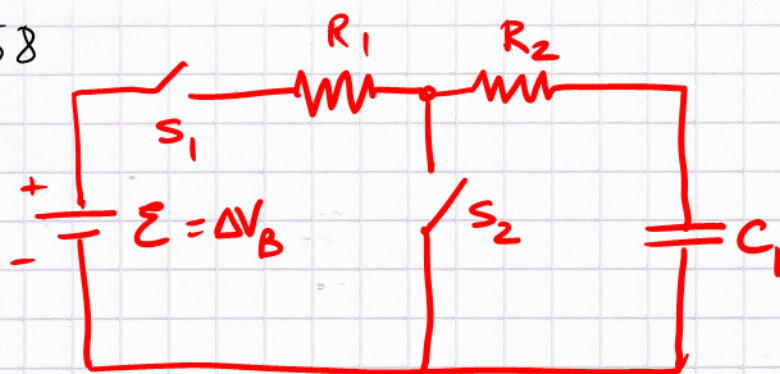close S_1

→ what is i_{batt} ?
just after S_1 closes

Solution

with S_2 open we have $R_{12}^{\text{eq}} = R_1 + R_2$ in series with C_1 , i.e., an RC circuit.

With C_1 uncharged at this instant, $\Delta V_C = 0$ ($= Q/C_1$, with $Q = 0$).

Thus R_{12}^{eq} limits the current: $i_{\text{batt}} = \frac{\Delta V_B}{R_{12}^{\text{eq}}}$

$$R_{12}^{\text{eq}} = (1.5 + 2.4) \text{ k}\Omega = 3.9 \text{ k}\Omega$$

$$\Delta V_B = 5.5 \text{ V} \quad \therefore \quad i_{\text{batt}} = \frac{5.5}{3.9} \text{ mA} = 1.4 \text{ mA}$$

NB: This current changes rapidly:


$$i(t) = \frac{\Delta V_B}{R_{\text{eq}}} e^{-t/\tau}$$

where $\tau = R_{\text{eq}} C$

is the time constant

after τ seconds $i(\tau) \approx \frac{1}{3} i(0)$ ($1/2.7 \dots$)

19.59

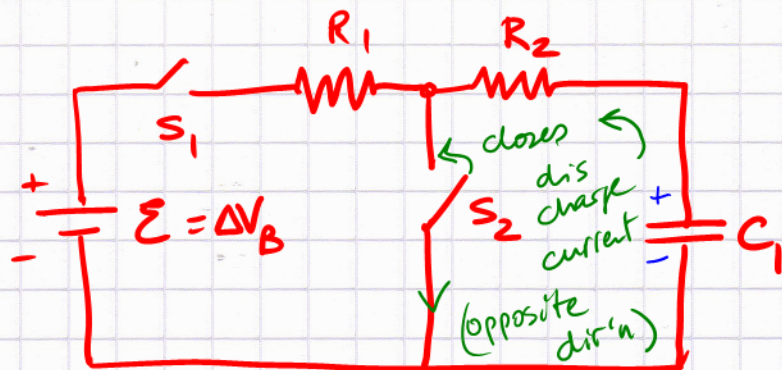

S_1 was closed
for a long time

- Now simultaneously S_1 is opened and S_2 is closed
- what is the current through S_2 just when it closed?
 - show a graph of $i_2(t)$ • $i_2(t \rightarrow \infty) = ?$

Solution.

S_1 was closed for long $\therefore \Delta V_{C_1} = \Delta V_B$; $i_1 = 0$

all charge separation has taken place, C_1 is

charged to $Q = C_1 \Delta V_B$

since there is no current, by Ohm's law there
is no voltage drop across R_1 or $R_2 \therefore \Delta V_{C_1} = \Delta V_B$!


- simultaneously opening S_1 & closing S_2 :

a) battery is disconnected

b) C_1 starts discharging through R_2 : $i_2(0) = -\frac{\Delta V_B}{R_2}$

R_2 limits the discharge
current

$$|\Delta V_{R_2}| = |\Delta V_{C_1}| \quad (\text{Kirchhoff } \infty) \quad \left| \begin{array}{l} -2.3 \text{ mA} \\ 5.5 \text{ V} \\ 3.9 \text{ k}\Omega \end{array} \right.$$

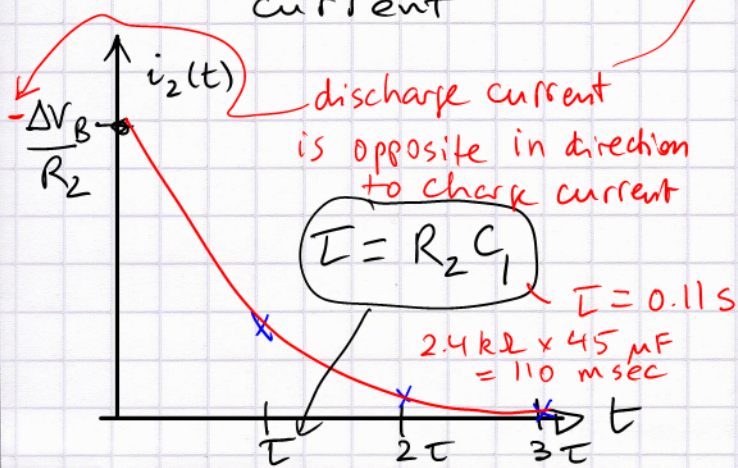

Long time (multiples of τ)

$\rightarrow$ current is zero

(C_1 plates are discharged)