

Week 20

21.50

single circular loop, $R = 2.0 \text{ cm}$, rotates $f = 60 \text{ Hz}$
in $\vec{B}$ field ($B = 1.5 \text{ T}$, constant, uniform)

Maximum EMF = ?

Solution.

This is a case where $\Phi_M = B \cdot A \cdot \cos \varphi$ is changing
in time since $\varphi = \omega t = 2\pi f t$; $B_0 = 1.5 \text{ T}$, $A = \pi R^2$

$$\therefore \Phi_M(t) = B_0 A \cos(2\pi f t)$$

Now, Faraday: $EMF = - \frac{d\Phi_M}{dt} \therefore |EMF| = \left| \frac{d\Phi_M}{dt} \right|$

Maxima occur when $\sin \varphi = \pm 1 \therefore \varphi = (n + \frac{1}{2})\pi$
 $n = 0, 1, 2, \dots$

why? $\left| \frac{d\Phi_M}{dt} \right| = |2\pi f B_0 A \sin(2\pi f t)|$

$$\therefore EMF_{\max} = 2\pi f B_0 A$$

$$= 6.28 \cdot 60 \cdot 1.5 \cdot 3.14 \cdot (2.0 \times 10^{-2})^2 \text{ V}$$

$$= 7.10 \times 10^3 \times 10^{-4} \text{ V}$$

$$= 0.71 \text{ V} = 710 \text{ mV}$$

NB: solution manual doesn't use calculus and gets
a hand-wavy estimate of 0.92 V (sine wave $\rightarrow$ triangle wave)

21.58 Current loop sits in $B(t)$ magnetic field, perpendicular to the loop




graph the EMF induced

Solution

Faraday:
$$EMF = - \frac{d\phi_M}{dt} = - \frac{d}{dt} (B(t) A) \quad \left\{ \begin{array}{l} \cos \varphi = 1 \\ \text{since} \\ \varphi = \pi/2 \end{array} \right.$$

$$= -A \frac{dB}{dt}$$

EMF [V]

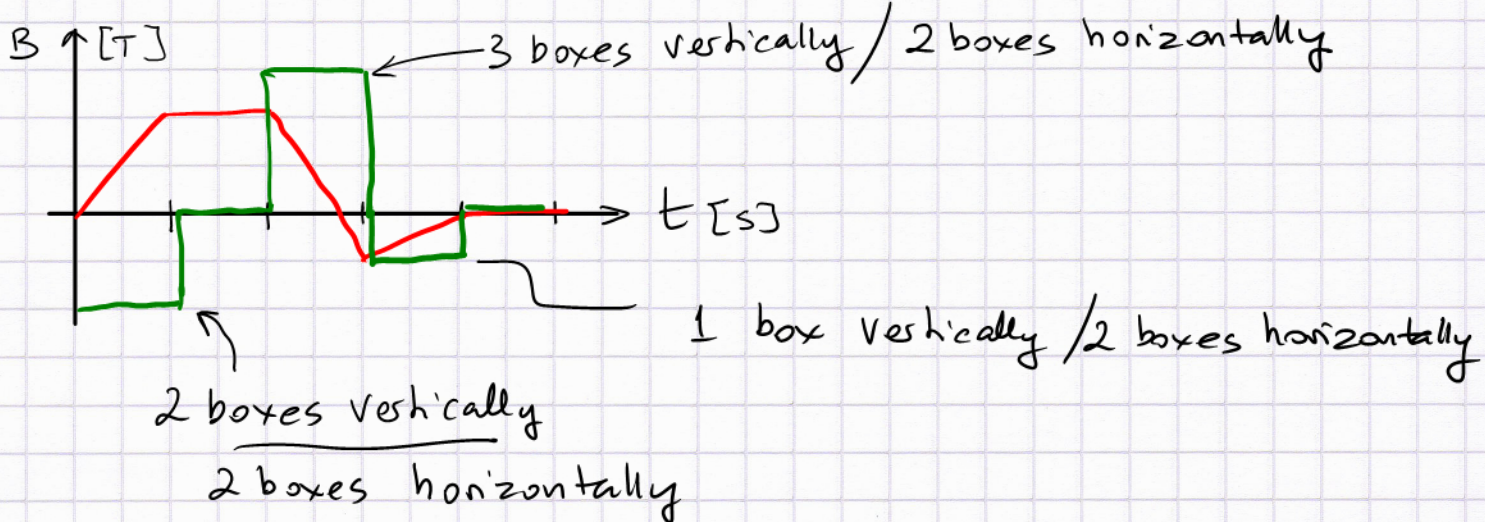


21.62

S was open a long time, $R_1 = R_2 = 50 \Omega$

$$L_1 = L_2 = L_3 = 40 \text{ mH}$$

$$\Delta V = 12 \text{ V}$$

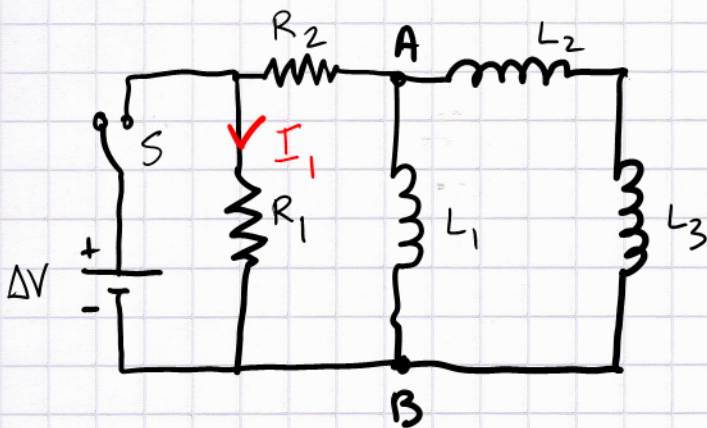

$$a) L_{eq}^{AB} = ?$$

b) at $t=0$ close S

$$I_1 = ?$$

$$c) I_1(t \rightarrow \infty) = ?$$

Solution.

L_{eq}^{AB} comes from L_1 in parallel with L_2 & L_3 in series

Two coils in series: adding the turns; means

$$L \equiv \frac{\mu_0 N^2 A}{l}$$

l = length; $\frac{N}{l} = \text{const}$

$$L = \left(\frac{\mu_0 N}{l} A \right) \cdot N$$

const.

$$\therefore L_{23}^{eq} = L_2 + L_3$$

Also by Kirchhoff: $\Delta V_{L_{eq}} = \Delta V_{L_2} + \Delta V_{L_3}$

$$= L_2 \frac{dI}{dt} + L_3 \frac{dI}{dt} = (L_2 + L_3) \frac{dI}{dt}$$

Parallel inductors: current splits, is not the same,

but voltage drop is the same

$$\Delta V_{AB} = L_{eq}^{AB} \frac{dI_2}{dt} = L_1 \frac{dI_{L_1}}{dt} = L_{23}^{eq} \frac{dI_{L_{23}}}{dt}$$

total current I_2
derivative

$$\text{where } I_2 = I_{L_1} + I_{L_{23}}$$

$$\therefore L_{eq}^{AB} \left(\frac{dI_{L_1}}{dt} + \frac{dI_{L_{23}}}{dt} \right) = \Delta V_{AB}$$

$$\therefore L_{eq}^{AB} \left(\frac{\cancel{\Delta V_{AB}}}{L_1} + \frac{\cancel{\Delta V_{AB}}}{L_{23}} \right) = \cancel{\Delta V_{AB}} \quad 1$$

$$\therefore \frac{1}{L_{eq}^{AB}} = \frac{1}{L_1} + \frac{1}{L_{23}} \quad (\text{like parallel resistors})$$

$$L_{eq}^{AB} = \frac{L_1 L_{23}}{L_1 + L_{23}}$$

$$(a) \quad L_{eq}^{AB} = \frac{40 \cdot 80}{40 + 80} \text{ mH} \\ = \frac{320}{12} \text{ mH} = 26.7 \text{ mH}$$

b) L_{eq}^{AB} will pass no current @ $t=0$ due to counter-EMF

$$\therefore I_1(0) = \frac{\Delta V_B}{R_1} = \frac{12V}{50\Omega} = \frac{24}{100} \text{ A} = 0.24 \text{ A}$$

c) In steady state the current in the loop made up by the battery, R_2 , and L_{eq}^{AB} is given by Ohm's law

$$I_2^{ss} = \frac{\Delta V_B}{R_2} = \frac{12}{50} \text{ A} = 0.24 \text{ A}$$


The current through R_1 doesn't change:

the single resistor R_1 is parallel to R_2 , which is followed in series by L_{eq}^{AB} .

Both branches pass equal amounts of current in steady state, since R_1 and R_2 are the same.

Note: opening S' will result in $I_1 \rightarrow -I_1$, since L_{eq}^{AB} will continue to pass I_2 , but the battery is now disconnected.

22.43

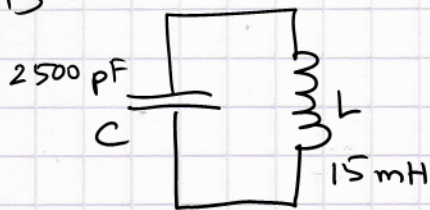

At $t = 0$ we have $q = 0$ on C ,
and $I = 45 \text{ mA}$

a) energy stored in inductor @ $t = 0$?

b) @ $t = t_1$ we have $I(t_1) = 0$.

How big is q on the plates @ t_1 ?

c) what is t_1 ?

d) $I(3t_1 = ?)$, $q(3t_1) = ?$

Solution.

$$a) PE_L = \frac{1}{2} I^2 = \frac{15}{2} \times 10^{-3} \times 45^2 \times 10^{-6} \text{ J} = 15.2 \mu\text{J}$$

b) when $I = 0$ we have no B field, all energy is in the capacitor's E field

$$PE_C = \frac{C}{2} \Delta V^2 \quad \text{where } \Delta V = \frac{q}{C} \therefore PE_C = \frac{1}{2C} q^2$$

$$\therefore q^2 = 2C PE_L = 2 \times 2.5 \times 10^{-12} \times 15.2 \times 10^{-6} \text{ C}^2$$

$$= 75.9 \times 10^{-15} \text{ C}^2 = 7.59 \times 10^{-14} \text{ C}^2$$

↑
Coulomb

$$q = 2.76 \times 10^{-7} \text{ C} = 280 \text{ nC}$$

$$c) t_1 = ? \quad \text{charge } q(t) = q_0 \sin(\omega t) \quad \text{where } \omega = \frac{1}{\sqrt{LC}}$$

$$\omega t_1 = \pi/2 \quad \therefore t_1 = \frac{3.14}{2 \cdot 1.63 \times 10^5} \text{ s} = 1.63 \times 10^{-5} \text{ s}$$

$$= 9.6 \mu\text{s}$$

d) $t_2 = 3t_1$ corresponds to $\omega t_2 = 3\frac{\pi}{2}$; this should be max. charge / zero current again, but charge is reversed

$$q_2 = 280 \text{ nC, opposite.} \quad I_3 = I(t_2) = 0$$

22.46 same circuit.

$$q(t_3) = 50 \text{ nC}, \quad PE_L = PE_C$$

What is $I(t_3)$?

Solution.

$$\text{a) } t = t_3 : \quad \frac{1}{2} L I^2 = \frac{1}{2} C \Delta V^2 = \frac{q^2}{2C}$$

$$I = I(t_3)$$

$$q = q(t_3)$$

$$I(t_3)^2 = \frac{2}{L} \frac{q^2}{2C} = \frac{q^2}{LC} = \omega^2 q^2$$

$$\therefore I(t_3) = \omega q = 1.63 \times 10^5 \times 50 \frac{\text{nC}}{\text{s}} = 8.15 \text{ mA}$$

we can check that $PE_C = PE_L = 0.50 \mu\text{J}$
at this time.

22.66

120V $\rightarrow$ 12V transformer

$$N_{\text{out}} = 4000$$

What is N_{in} ?

We need

$$\frac{N_{\text{out}}}{N_{\text{in}}} = \frac{1}{10} \therefore N_{\text{in}} = 40,000$$

connected in reverse:

$$120\text{V} \rightarrow 1200\text{V}$$

Since now

the effective $N_{\text{in}} = 4000$ and $N_{\text{out}} = 40,000$

i.e., it steps up AC by a 10:1 ratio now.