
PHYSICS 1012

Total – 94 marks

Solutions to Problem Set 2

was due February 13, 2022

“I have no reason to believe that the human intellect is able to weave a system of physics out of its own resources without experimental labour. Whenever the attempt has been made it has resulted in an unnatural and self-contradictory mass of rubbish.”

– **James Clerk Maxwell**

As always, in the following you need to show how you got an answer – i.e., show your work. If you don't you will get 0 marks for the problem. The text questions are given in the format “Chapter.Problem”. For example, the 10.2 in question 1 refers to Text Chapter 10, Problem 2.

1. (3 marks) 10.2

- Initially $i_i = V_0/(r + R) = V_0/2r$. Then, after corrosion $r' = 3r$ and $i_a = V_0/(r' + R) = V_0/4r$ so $i_a = i_i/2$ (i.e., the current delivered is halved).

2. (6 marks) 10.22

- (a) $i = V_0/(r + R) = (12 \text{ V})/(0.06 \Omega) = 200 \text{ A}(!)$
- (b) $\Delta V = iR = (200 \text{ A})(.05 \Omega) = 10 \text{ V}$
- (c) $P = i^2 R = (200 \text{ A})^2(0.05 \Omega) = 2000 \text{ W} = 2 \text{ kW}$
- (d) Now $i = V_0/(r + r_c + R) = (12 \text{ V})/(0.15 \Omega) = 80 \text{ A}$
 $\Delta V = iR = (80 \text{ A})(.05 \Omega) = 4 \text{ V}$
 $P = i^2 R = (80 \text{ A})^2(0.05 \Omega) = 320 \text{ W}$

3. (2 marks) 10.8

- No. Kirchoff's Current Law says that $i_1 + i_2 + i_3 = 0$ so at least one of them (though it can't be all) has to be negative (i.e., going in the opposite direction to that shown).

4. (6 marks) 10.42

- loop 1: $i_1 R_1 + i_2 R_2 - V_1 = 0$
loop 2: $-i_2 R_2 - i_3 R_3 + i_4 R_4 + V_2 = 0$
loop 3: $i_5 R_5 - V_2 = 0$

5. (6 marks) 10.72

- (a) Voltage division follows

$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$

- (b) R_1 and R_2 are “in parallel” so the pair can be replaced by the equivalent resistance

$$R = \frac{R_2 R_L}{R_2 + R_L} \quad \left(\text{i.e., } \frac{1}{R} = \frac{1}{R_2} + \frac{1}{R_L} \right)$$

so

$$V_{out} = V_{in} \frac{R}{R_1 + R} = V_{in} \frac{\frac{R_2 R_L}{R_2 + R_L}}{R_1 + \frac{R_2 R_L}{R_2 + R_L}} = V_{in} \left(\frac{R_2 R_L}{R_1 R_2 + R_1 R_L + R_2 R_L} \right)$$

6. (6 marks) 10.78 [Note that the answer to 10.72(a) may come in handy]

(a) $\Delta V = i_1 R_1 = (50 \text{ mA})(40 \Omega) = 2 \text{ V}$

(b)

$$\Delta V_2 = \Delta V_1 \frac{R_2}{R_2 + R_3} = (2 \text{ V}) \frac{(5\Omega)}{(5\Omega + 15\Omega)} = \frac{1}{2} \text{ V}$$

7. (6 marks) 10.36

- First note that all of the resistors are in series so, for the purposes of calculating current, they can be replaced by the equivalent resistance $R = R_1 + R_2 + R_3 + R_4 + R_5 = 60 \text{ k}\Omega$. Similarly, the two batteries can be replaced with 1 battery having a voltage of $\Delta V = 24 - 12 = 12 \text{ V}$ (with the polarity of the 24 V battery). So $i = \Delta V / R = (12 \text{ V}) / (60 \text{ k}\Omega) = (1/5) \text{ mA}$.

(a) $\Delta V_i = i R_i$ so $\Delta V_1 = i R_1 = (0.2 \text{ mA})(10 \text{ k}\Omega) = 2 \text{ V} = \Delta V_3 = \Delta V_4 = \Delta V_5$.
 $\Delta V_2 = i R_2 = (0.2 \text{ mA})(20 \text{ k}\Omega) = 4 \text{ V}$

(b) $P_{\text{supplied}} = \Delta V i = (12 \text{ V})(0.2 \text{ mA}) = 2.4 \text{ mW}$ while $P_{\text{dissipated}} = i^2 R = (0.2 \text{ mA})^2 (60 \text{ k}\Omega) = (60/25) \text{ mW} = 2.4 \text{ mW}$

8. (6 marks) 10.38 [Note that it is literally the same circuit as 10.37(b)]

- Apply KCL and KVL to get $\Delta V_1 = 18 \text{ V}$, $i_2 = 1 \text{ A}$, and $i_3 = 3 \text{ A}$

9. (6 marks) 10.40

- Apply KCL and KVL to get $i_1 = 3/2 \text{ A}$, $i_2 = 2 \text{ A}$, and $i_3 = 1/2 \text{ A}$

10. (6 marks) 10.84

- First note that R_1 , r_1 and R_5 are in series, as are r_2 and R_2 as well as R_3 , r_3 and R_4 . Similarly, ε_3 and ε_4 are in series although with opposite polarities leading to a single battery with $\varepsilon = 30 \text{ V}$. Then apply KCL and KVL to find $i_1 = -0.34 \text{ A}$, $i_2 = 0.36$, and $i_3 = 0.02 \text{ A}$

11. (2 marks) 8.20

- $Q = C \Delta V = (8 \times 10^{-12} \text{ F})(5.5 \text{ V}) = 4.4 \times 10^{-11} \text{ C}$

12. (2 marks) 8.22

- $Q = C\Delta V$ so

$$\Delta V = \frac{Q}{C} = \frac{(1.6 \times 10^{-4} \text{ C})}{(8 \times 10^{-9} \text{ F})} = \frac{1}{5} \times 10^5 \text{ V} = 20 \text{ kV}$$

13. (2 marks) 8.26

- $C = \epsilon_0 A/d$ so

$$d = \frac{\epsilon_0 A}{C} = \frac{(8.85 \text{ pF/m})(0.01 \text{ m}^2)}{(60 \text{ pF})} = 1.48 \text{ mm}$$

14. (4 marks) A parallel-plate, air-filled capacitor having area 35 cm^2 and spacing of 1.5 mm is charged to a potential difference of 500 V . Find (a) the capacitance, (b) the magnitude of the charge on each plate, (c) the stored energy, and (d) the electric field between the plates.

(a) the capacitance

- $C = \epsilon_0 A/d = (8.85 \text{ pF/m})(3.5 \times 10^{-3} \text{ m}^2)/(1.5 \times 10^{-3} \text{ m}) = 20.7 \text{ pF}$

(b) the magnitude of the charge on each plate

- $q = C\Delta V = (2.07 \times 10^{-11} \text{ F})(500 \text{ V}) = 1.03 \times 10^{-8} \text{ C} = 10.3 \text{ nC}$

(c) the stored energy

- $U = C\Delta V^2/2 = (2.07 \times 10^{-11} \text{ F})(500 \text{ V})^2/2 = 2.58 \text{ } \mu\text{J}$

(d) the electric field between the plates.

- $|\vec{E}| = \Delta V/d = (500 \text{ V})/(1.5 \times 10^{-3} \text{ m}) = (1/3) \times 10^6 \text{ V/m} = 333.3 \text{ kN/C}$

15. (6 marks) A parallel-plate capacitor has plates of area A and separation d and is charged to a potential difference of ΔV_0 . The charging battery is then disconnected (so the capacitor is electrically isolated) and the plates are pulled apart until their separation is $3d$. Derive expressions in terms of A , d , and ΔV_0 for (a) the new potential difference, (b) the initial and final stored energy, and (c) the work required to separate the plates.

- For the parallel plate capacitor $C = \epsilon_0 A/d$. With $d' = 3d$ then $C' = \epsilon_0 A/d' = \epsilon_0 A/3d = C/3$

(a) the new potential difference

- $\Delta V' = q/C' = 3q/C = 3\Delta V$

(b) the initial and final stored energy

- $U = C\Delta V^2/2 = \epsilon_0 A\Delta V^2/2d$ and $U' = C'(\Delta V')^2/2 = (C/3)(3\Delta V)^2/2 = 3U = 3\epsilon_0 A\Delta V^2/2d$

(c) the work required to separate the plates

- The work required is $U' - U = 2U = \epsilon_0 A\Delta V^2/d$

16. (6 marks) 8.54

(a)

$$|\vec{E}| = 2 \left(\frac{\sigma}{2\epsilon_0} \right) = \frac{\sigma}{\epsilon_0} = \frac{(0.5 \times 10^{-3} \text{ C/m}^2)}{(8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2)} = 5.6 \times 10^7 \text{ V/m}$$

(b) $\Delta V = Et = (5.6 \times 10^7 \text{ V/m})(5.0 \times 10^{-9} \text{ m}) = 0.28 \text{ V}$

(c) $u = U/V = (1/2)\epsilon_0 E^2$ where V is volume. Assume the cell volume given is enclosed by the outer cell wall so

$$V_{outer} = \frac{4}{3}\pi R_{outer}^3 \implies R_{outer} = \left(\frac{3V}{4\pi} \right)^{1/3} = \left(\frac{3(10^{-16} \text{ m}^3)}{(4\pi)} \right)^{1/3} = 2.879 \times 10^{-6} \text{ m}$$

By definition $R_{inner} = R_{outer} - t = 2.874 \times 10^{-6} \text{ m}$ so

$$V_{inner} = \frac{4}{3}\pi R_{inner}^3 = \frac{4}{3}\pi (2.874 \times 10^{-6} \text{ m})^3 = 9.94 \times 10^{-17} \text{ m}^3$$

We would then have $V_{walls} = V_{outer} - V_{inner} = 6 \times 10^{-19} \text{ m}^3$ and so

$$\begin{aligned} U &= Vu \\ &= V \left(\frac{1}{2} \epsilon_0 E^2 \right) \\ &= \frac{1}{2} (6 \times 10^{-19} \text{ m}^3) (8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2) (5.6 \times 10^7 \text{ N/C})^2 \\ &= 8.3 \times 10^{-15} \text{ J} = 8.3 \text{ fJ} \end{aligned}$$

17. (2 marks) 10.17

- (Answer from text) “The time constant can be shortened by using a smaller resistor and/or a smaller capacitor. Care should be taken when reducing the resistance because the initial current will increase as the resistance decreases.”

18. (2 marks) 10.50

- $f = 72 \text{ min}^{-1} = (6/5) \text{ Hz}$ so $T = (5/6) \text{ s}$. Now

$$\tau = RC = T = \frac{5}{6} \text{ s} \implies R = \frac{T}{C} = \frac{5}{6(2.5 \times 10^{-8})} = \frac{1}{3} \times 10^8 \Omega = 33.3 \text{ M}\Omega$$

19. (3 marks) 10.54

(a) $\tau = RC = 10.0 \text{ ms}$ and $C = 8.00 \mu\text{F}$ so

$$R = \frac{\tau}{C} = \frac{10^{-2} \text{ s}}{8 \times 10^{-6} \text{ F}} = .125 \times 10^4 \Omega = 1.25 \text{ k}\Omega$$

(b) $V = V_0 e^{-t/\tau}$ so

$$\frac{-t}{\tau} = \ln \left(\frac{V}{V_0} \right) \implies t = \tau \ln \left(\frac{V_0}{V} \right) = (10^{-2} \text{ s}) \ln \left(\frac{12 \text{ V}}{0.6 \text{ V}} \right) = 3.0 \times 10^{-2} \text{ s} = 30.0 \text{ ms}$$

20. (12 marks) 10.94

- Assume the capacitor is initially uncharged and call the time when the switch closes $t = t_0 = 0$ so the potential drop across the capacitor will be $\Delta V_C(0) = 0$ V.

- (a) We have that $\Delta V_C = \Delta V_{R_1}$ so $\Delta V_C(0) = 0$ V means that $\Delta V_{R_1}(0) = 0$ V and all of the battery voltage is across R_2 . Therefore,

$$i_2(0) = \frac{V_1}{R_2} = \frac{24 \text{ V}}{30 \text{ k}\Omega} = \frac{4}{5} \text{ mA}$$

- (b) When the switch has been closed for a long time then the capacitor is fully charged and no current flows to it. Therefore all the current flows through R_1 and R_2 in series and so

$$i_2 = \frac{V_1}{R_1 + R_2} = \frac{24 \text{ V}}{40 \text{ k}\Omega} = \frac{3}{5} \text{ mA}$$

- (c) Once the switch is opened then no current flows through the $R_2 + V_1$ branch and so the capacitor will discharge through R_1 with the time constant $\tau = R_1 C = (10 \text{ k}\Omega)(10 \text{ }\mu\text{F}) = 0.1 \text{ s}$.

- (d) While discharging the current goes like $i(t) = i_0 e^{-t/\tau}$. So, when $i = i_0/2$

$$\frac{i}{i_0} = \frac{1}{2} = e^{-t/\tau} \quad \implies \quad t = \tau \ln 2 = (0.1 \text{ s}) \ln 2 = 0.069 \text{ s} = 69.3 \text{ ms}$$