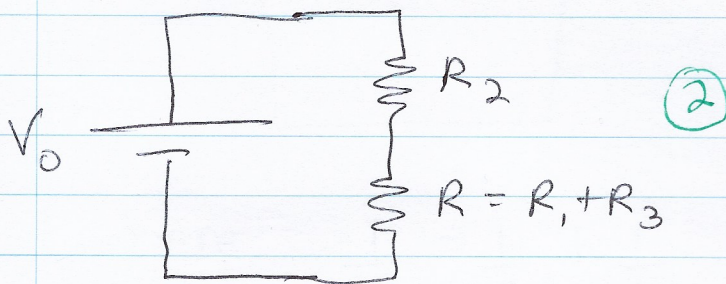


$$\text{So } \Delta V_{R_2} = \Delta V_{BD} = -i R_2 = \frac{V_0 R_2}{R_1 + R_2 + R_3} \quad (1)$$

$$\text{So } \Delta V_{R_2} = \frac{(12 \text{ V})(5 \text{ k}\Omega)}{(4 \text{ k}\Omega + 5 \text{ k}\Omega + 6 \text{ k}\Omega)} = \frac{12 \text{ V}}{3} = 4 \text{ V} \quad (1)$$


or (2) Add R_1 and R_3 in series to have



and use Voltage Division

$$\Delta V_{R_2} = V_0 \frac{R_2}{R + R_2} = V_0 \frac{R_2}{R_1 + R_2 + R_3} = 4 \text{ V} \quad (1)$$

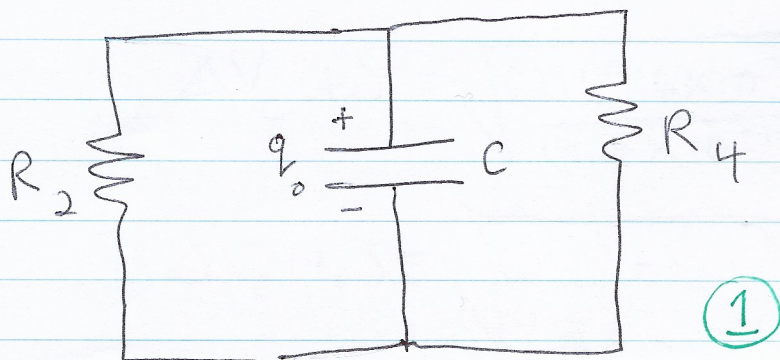(b) The idea was that this circuit was supposed to be treated like this.
 at $t = t_0$, where t_0 is the instant the S_2 is closed and S_1 is opened.



$$C = 48 \text{ pF} = 4.8 \times 10^{-11} \text{ F}$$

$$C = 36 \text{ pF} = 3.6 \times 10^{-11} \text{ F}$$