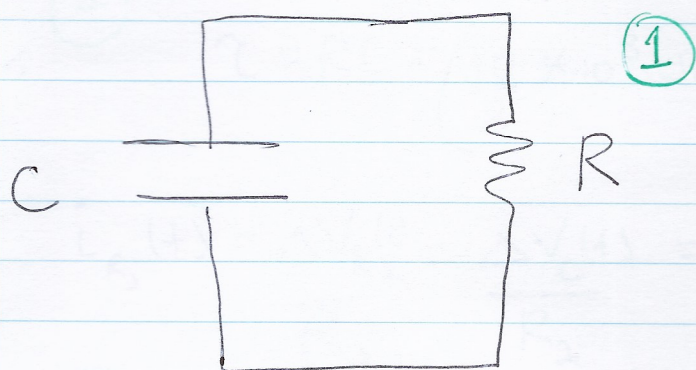


R_2 and R_4 are in parallel so to calculate ΔV_{R_2} I can replace the circuit with this:



and $\Delta V_{R_2} = \Delta V_R = \Delta V_C$

where $\frac{1}{R} = \frac{1}{R_2} + \frac{1}{R_4} \rightarrow R = \frac{R_2 R_4}{R_2 + R_4} = \frac{(5 \text{ k}\Omega)(10 \text{ k}\Omega)}{5 \text{ k}\Omega + 10 \text{ k}\Omega}$

①

$= \frac{10}{3} \text{ k}\Omega$

Now, the capacitor originally had stored $U_0 = 9.6 \text{ nJ}$ of stored energy

so $U_0 = \frac{1}{2} \frac{q_0^2}{C} = \frac{1}{2} C \Delta V_C(t_0)^2$ ①

so $\Delta V_C(t_0) = \sqrt{\frac{2U_0}{C}}$ ~~$\sqrt{\frac{(2)(9.6 \times 10^{-9} \text{ J})}{(3.6 \times 10^{-11} \text{ F})}} \neq 20 \text{ V}$~~

① $\Delta V_C(t_0) = \sqrt{\frac{(2)(9.6 \times 10^{-9} \text{ J})}{(4.8 \times 10^{-11} \text{ F})}} = \sqrt{400} \text{ V} = \cancel{20.0 \text{ V}} 20.0 \text{ V}$

① $\Delta V_C(t_0) = \sqrt{\frac{(2)(9.6 \times 10^{-9} \text{ J})}{(3.6 \times 10^{-11} \text{ F})}} = \frac{40}{\sqrt{3}} \text{ V} = 23.1 \text{ V}$