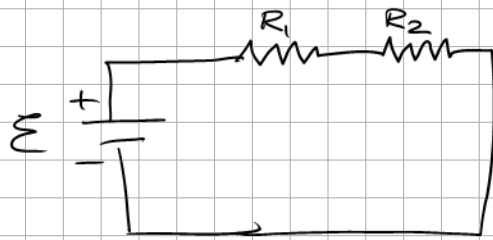


19.33 (2e)



$$R_1 = 1500 \Omega$$

$$R_2 = 3500 \Omega$$

$$\mathcal{E} = 12 \text{ V}$$

Q: power dissipated in R_2 ?

strategy: $P = \Delta V \cdot I$

\therefore need ΔV and I

I from Ohm's law for equivalent circuit:

$R_1, R_2 =$ series resistors $\therefore R_{eq} = R_1 + R_2$

$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{\mathcal{E}}{R_1 + R_2} = \frac{12}{4800} \text{ A}$$

$$I = 2.5 \text{ mA}$$

ΔV from voltage divider idea

Kirchhoff loop rule: $\underbrace{\mathcal{E} - R_1 I}_{\Delta V_1} - \underbrace{R_2 I}_{\Delta V_2} = 0$

$$12 - 1500 \cdot 2.5 \times 10^{-3} + \Delta V_2 = 0 \quad \text{need } \Delta V_2!$$

$$\Delta V_2 = -12 + 3.75 = -8.25 \text{ V}$$

$$\underline{\underline{P_2 = |\Delta V_2| \cdot I = 8.25 \cdot 2.5 \times 10^{-3} = 20.6 \text{ mW} \\ = 21 \text{ mW}}}$$

Note: R_1 also dissipates power! It is less,

since $|\Delta V_1| = 3.75 \text{ V} \therefore P_1 = 9.4 \text{ mW}$

19.38 (2e)

same circuit

$$I = 0.15 \text{ A}$$

$$R_1 = 1500 \Omega$$

$$R_2 = 2500 \Omega$$



Loop rule: $\mathcal{E} - R_1 I - R_2 I = 0$

$$\mathcal{E} = (1500 + 2500) \cdot I$$

$$= 4000 \cdot 0.15 \text{ A}$$


$$\mathcal{E} = 600 \text{ V}$$

Alternative solution: $R_{\text{eq}} = R_1 + R_2 = 4000 \Omega$

$$|\Delta V_{\text{Req}}| = \mathcal{E}$$

$$\mathcal{E} = R_{\text{eq}} I \dots$$

19.40

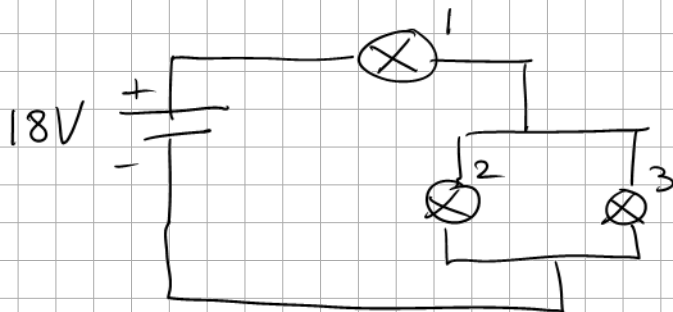


1, 2, 3 =
identical bulbs
= resistors

$$R_i = 200 \Omega \quad (i=1, 2, 3)$$

Find I_1 and I_2

Conceptual:

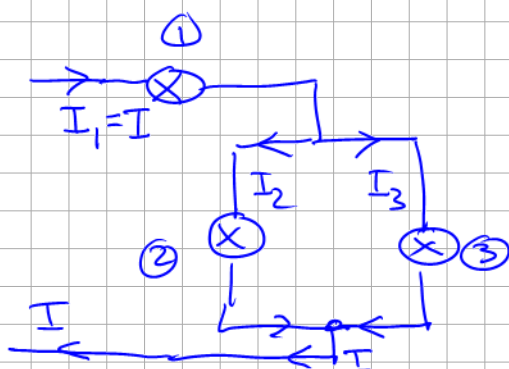

Since $R_2 = R_3$
and they are
parallel \rightarrow
same voltage drop

$$\therefore I_2 = I_3 = \frac{I}{2}$$

$$R_{23}^{eq} = \frac{R_2 R_3}{R_2 + R_3} = \frac{R}{2} = 100 \Omega$$


$$R_{tot}^{eq} = R_1 + \frac{R}{2} = \frac{3}{2} R = 300 \Omega$$

$$I = \frac{\mathcal{E}}{R} = \frac{18}{300} = 0.06 \text{ A}$$

$$I_1 = 0.06 \text{ A}$$

$$I_2 = I_3 = 0.03 \text{ A}$$

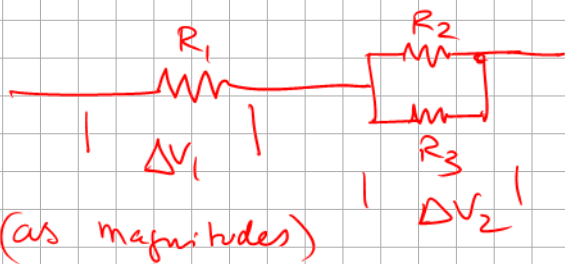Also: how bright? \rightarrow power = $\Delta V \cdot I$



(as magnitudes)

$$\Delta V_1 + \Delta V_2 = \mathcal{E}$$

$$R I + \frac{R}{2} I = \mathcal{E}$$



voltage divider!
 $12 \text{ V} + 6 \text{ V} = 18 \text{ V}$

$$P_1 = 12 \text{ V} \cdot 0.06 \text{ A}$$

$$P_2 = 6 \text{ V} \cdot 0.03 \text{ A} \leftarrow \text{4 times less power!}$$

Week 16 (1st ed.) has 19.40 = 19.52 in 2^e

19.58 (2e) Real battery check

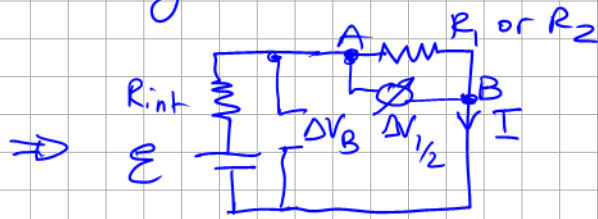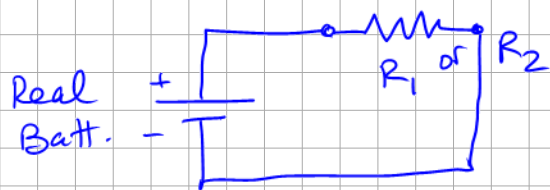

$$\left. \begin{array}{l} R_1 = 750 \Omega \quad \Delta V_{AB} = 6.5 \text{ V} \\ R_2 = 2500 \Omega \quad \Delta V_{AB} = 9.5 \text{ V} \end{array} \right\} I_{1/2} = \frac{\Delta V_{AB, 1/2}}{R_{1/2}} \rightarrow \textcircled{3}, \textcircled{4}$$

Find R_{int} and $V_0 = \mathcal{E}$

Kirchhoff loop: $\mathcal{E} - R_{int} I - \Delta V_{AB} = 0 \rightarrow \textcircled{1}, \textcircled{2}$

two times \rightarrow two unknowns (\mathcal{E}, R_{int})
can be solved for

$$\begin{array}{l} \rightarrow \textcircled{1} \quad \mathcal{E} - R_{int} I_1 - \Delta V_{AB,1} = 0 \quad I_1 = \frac{\Delta V_{AB,1}}{R_1} \quad \textcircled{3} \\ \textcircled{2} \quad \mathcal{E} - R_{int} I_2 - \Delta V_{AB,2} = 0 \quad I_2 = \frac{\Delta V_{AB,2}}{R_2} \quad \textcircled{4} \end{array}$$

$$\left. \begin{array}{l} \textcircled{1}: \quad \mathcal{E} - R_{int} \frac{\Delta V_{AB,1}}{R_1} - \Delta V_{AB,1} = 0 \\ \textcircled{2}: \quad \mathcal{E} - R_{int} \frac{\Delta V_{AB,2}}{R_2} - \Delta V_{AB,2} = 0 \end{array} \right\} \text{and call } \begin{array}{l} V_1 = \Delta V_{AB,1} \\ V_2 = \Delta V_{AB,2} \end{array}$$

$$\textcircled{5} \quad -R_{int} \left(\frac{V_1}{R_1} - \frac{V_2}{R_2} \right) - V_1 + V_2 = 0$$

$$R_{int} \frac{R_2 V_1 - R_1 V_2}{R_1 R_2} + V_1 - V_2 = 0$$

$$R_{int} = \frac{(V_2 - V_1) R_1 R_2}{R_2 V_1 - R_1 V_2} \rightarrow \frac{(9.5 - 6.5) 750 \cdot 2500}{2500 \cdot 6.5 - 750 \cdot 9.5} = 616 \Omega$$

insert into $\textcircled{1}$ $\mathcal{E} = +V_1 + R_{int} \frac{V_1}{R_1} = +6.5 + \frac{616 \cdot 6.5}{750} = 11.8 \text{ V}$

$\therefore R_{int} = 620 \Omega \quad \mathcal{E} = 12 \text{ V}$

\leftarrow "leaky" battery (meant for very low currents)