LAST NAME:

STUDENT NR:

PHYS 1010 6.0: CLASS TEST 5 $\,$

Time: 50 minutes; Calculators & formulae provided at the end = only aid; Total = 20 points.

1) [5] Analyze this experiment: in the circuit shown the switch has been in position A for a long time, while capacitors C_2 and C_3 were uncharged. At time t = 0 the switch is flipped to position B, and remains there for a long time. What is the charge on each of the three capacitors at the end of the experiment? Compare your answer to what charge was held by C_1 at t = 0, just before the switch was flipped.

$$R_{1} = 50 \Omega \quad C_{1} = 20 \mu F$$

$$R_{2} = 100 \Omega \quad C_{2} = 10 \mu F$$

$$C_{3} = 5 \mu F$$

$$Q = C \quad \Delta V = 20 \times 10^{6} \cdot 9.0 = 180 \mu C - 1$$

$$R_{1} \rightarrow R_{1} \rightarrow R_{2} = 0; \quad \Delta V_{2} = 9V$$

$$Q = C \quad \Delta V = 20 \times 10^{6} \cdot 9.0 = 180 \mu C - 1$$

$$R_{1} \rightarrow Q_{1}', \quad Q_{2} = Q_{3} \quad (same \ current); \quad Q_{1}' = Q_{1} - Q_{2}$$

$$C_{23} = \frac{C_{2}C_{3}}{c_{2}+c_{3}} = \frac{5D}{15} = 3.33 \mu F$$

$$R_{1}' = \frac{AV}{c_{3}} \quad (same \ current); \quad Q_{1}' = Q_{1} - Q_{2}$$

$$R_{2}' = \frac{C_{2}C_{3}}{c_{2}+c_{3}} = \frac{5D}{15} = 3.33 \mu F$$

$$R_{1}' = \frac{AV}{c_{3}} \quad (same \ current); \quad Q_{1}' = Q_{1} - Q_{2}$$

$$R_{2}' = \frac{C_{2}C_{3}}{c_{2}+c_{3}} = \frac{C_{2}C_{3}}{15} = 3.33 \mu F$$

$$R_{1}' = \frac{AV}{c_{3}} \quad (same \ current); \quad Q_{1}' = Q_{1} - Q_{2}$$

$$R_{2}' = \frac{C_{2}C_{3}}{c_{2}+c_{3}} = \frac{Q_{1}-Q_{1}'}{C_{2}} \quad (same \ current); \quad Q_{1}' = Q_{1} - Q_{2}$$

$$R_{2}' = \frac{AV}{c_{2}} \quad (same \ current); \quad Q_{1}' = Q_{1} - Q_{2}$$

$$R_{2}' = \frac{AV}{c_{2}} \quad (same \ current); \quad Q_{1}' = Q_{1} - Q_{2}$$

$$R_{2}' = \frac{AV}{c_{2}} \quad (same \ current); \quad R_{2}' = Q_{1} - Q_{2}$$

$$R_{2}' = \frac{AV}{c_{2}} \quad (same \ current); \quad R_{2}' = R_{2} - R_$$

on C, while C2 and C3 hold 26.
$$\mu$$
C respectively
Note Q1 = Q1 + Q2 + Q3 !!!

2) [5] In the circuit shown the switch has been in position A for a long time. (a) what is the voltage drop across resistor R_1 ? (b) what is the voltage drop across R_2 ? (c) How much charge is stored in the capacitor? (d) The switch is now (time t = 0) flipped to position B: graph the magnitude of the voltage drop across R_1 as a function of time. Calculate the time constant, and label your axes properly.

$$R_{1} = 1.0 \text{ KD}$$

$$R_{2} = 0.5 \text{ KD}$$

$$C = 4.7 \text{ pF}$$

$$a. \quad \Delta V_{R_{1}} = 0 \text{ (I)} \quad b. \quad \Delta V_{R_{2}} = \Delta V_{R_{1}} (\text{ kick holf boop rule})$$

$$= 0 \text{ (I)}$$

$$c. \quad \Delta V_{C} = \Delta V_{B} \quad \therefore \quad Q = C \Delta V = 4.7 \text{ pF} - 9 \text{ V} = 42.3 \text{ pc}$$

$$\Delta V_{R} = R_{1} T_{1}(A) = R_{2} T_{2}(A)$$

$$T = R_{eq} C$$

$$R_{eq} = \frac{R_{1} R_{2}}{R_{1} + R_{2}} = \frac{0.5}{1.5} \text{ kD}$$

$$T = 330 \text{ SD}$$

$$T = 350 \text{ SD}$$

$$T = 350 \text{ SD}$$

$$T = 350 \text{ SD}$$

С

3) [5] Three very long current-carrying wires are shown in the figure, as well as locations A,B,C,D, which are all in the x - y plane spanned by \hat{i} and \hat{j} . (a) Calculate \vec{B} (magnitude and direction in component form) at locations A, B, C, D. (b) What can you say about the field strength far away from the wires (|y| very large, or |z| very large)?

$$\vec{B}_{net} = \sum_{i=1}^{3} \vec{E}_i$$

$$\vec{I}_i = I_2 = I_3 = I_3$$

4) [5] The figure shows a copper rod of length X = 75 cm suspended by two springs to balance its weight (the springs are attached using plastic hooks). Both springs are characterized by a constant of k = 20 N/m respectively, and the rod was determined to have a mass of 500 g. A uniform magnetic field of B = 1.5 T acts over the entire length of the rod with an orientation into the page (as shown). Now you connect flexible low-mass electric contacts at points P_1 and P_2 , and drive a current through the rod by connecting P_1 to the negative terminal, and P_2 to the positive terminal of a powerful battery. Your current meter states that 50 Amps are flowing through the battery. (a) is the rod moving up or down when you turn on the current? Explain! (b) Calculate by how much the rod is displaced.

5.0

FORMULA SHEET

 $v(t_{\rm f}) = v(t_{\rm i}) + \int_{t_{\rm i}}^{t_{\rm f}} a(t) dt$ $s(t_{\rm f}) = s(t_{\rm i}) + \int_{t_{\rm i}}^{t_{\rm f}} v(t) dt$ $v_{\rm f} = v_{\rm i} + a\Delta t$ $s_{\rm f} = s_{\rm i} + v_{\rm i}\Delta t + \frac{1}{2}a\Delta t^2$ $v_{\rm f}^2 = v_{\rm i}^2 + 2a\Delta s$ $q = 9.8 \text{ m/s}^2$ $f(t) = t \quad \frac{df}{dt} = 1 \quad F(t) = \int f(t) \, dt = \frac{t^2}{2} + C$ f(t) = a $\frac{df}{dt} = 0$ $F(t) = \int f(t) dt = at + C$ F(t) =anti-derivative = indefinite integral area under the curve f(t) between limits t_1 and t_2 : $F(t_2) - F(t_1)$ $x^{2} + px + q = 0$ factored by: $x_{1,2} = -\frac{p}{2} \pm \sqrt{\frac{p^{2}}{4} - q}$ uniform circular m. $\vec{r}(t) = R(\cos \omega t \ \hat{\mathbf{i}} + \sin \omega t \ \hat{\mathbf{j}}); \ \vec{v}(t) = \frac{d\vec{r}}{dt} = ...; \ \vec{a}(t) = \frac{d\vec{v}}{dt} =$ $\exp' = \exp; \quad \sin' = \cos; \quad \cos' = -\sin. \qquad \frac{d}{dx} [f(g(x))] = \frac{df}{dg} \frac{dg}{dx}; \qquad (fg)' = f'g + fg'$ $m\vec{a} = \vec{F}_{\rm net}; \quad F_G = \frac{Gm_1m_2}{r^2}; \ g = \frac{GM_E}{R_E^2}; \ R_E = 6370 \ {\rm km}; \ G = 6.67 \times 10^{-11} \frac{{\rm Nm}^2}{{\rm kg}^2}; \ M_E = 6.0 \times 10^{24} {\rm kg}$ $f_{\rm s} \le \mu_{\rm s} n;$ $f_{\rm k} = \mu_{\rm k} n;$ $f_{\rm r} = \mu_{\rm r} n;$ $\mu_{\rm r} << \mu_{\rm k} < \mu_{\rm s}.$ $F_H = -k\Delta x = -k(x - x_0).$ $\vec{F}_{\rm d} \sim -\vec{v}$; linear: $F_{\rm d} = dv$; quadratic: $F_{\rm d} = 0.5 \rho A v^2$; A =cross sectional area $W = F\Delta x = F(\Delta r)\cos\theta$. $W = \text{area under } F_x(x)$. $PE_{\rm H} = \frac{k}{2}(\Delta x)^2$; $PE_q = mg\Delta y$. $\Delta \vec{p} = \vec{J} = \int \vec{F}(t) dt; \ \Delta p_x = J_x = \text{area under } F_x(t) = F_x^{\text{avg}} \Delta t \ ; \quad \vec{p} = m\vec{v}; \ K = \frac{m}{2}v^2$ $\Delta \vec{p_1} + \Delta \vec{p_2} = 0$; $K_1^{\text{in}} + K_2^{\text{in}} = K_1^{\text{fin}} + K_2^{\text{fin}}$ for elastic collisions. $\vec{a}_{\text{CM}} = \frac{m_1 \vec{a}_1 + m_2 \vec{a}_2}{m_1 + m_2}$ $\vec{\tau} = \vec{r} \times \vec{F}$; $\tau_z = rF\sin(\alpha)$ for \vec{r} , \vec{F} in xy plane. $I = \sum_i m_i r_i^2$; $I\alpha_z = \tau_z$; $(\hat{k} = \text{rot. axis})$ $K_{\rm rot} = \frac{I}{2}\omega^2; \ L_z = I\omega_z; \ \frac{d}{dt}L_z = \tau_z; \ \vec{L} = \vec{r} \times \vec{p}; \ \frac{d}{dt}\vec{L} = \vec{\tau}$ $x(t) = A\cos(\omega t + \phi);$ $\omega = \frac{2\pi}{T} = 2\pi f;$ $v_x(t) = ...;$ $v_{\max} = ...$ $m_{\rm e} = 9.11 \times 10^{-31} \text{kg}$ $m_{\rm p} = 1.67 \times 10^{-27} \text{kg}$ $e = 1.60 \times 10^{-19} \text{C}$ $k = \frac{1}{4\pi\epsilon_0} = 9.0 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}$ $\vec{F}_{\rm C} = \frac{kq_1q_2}{r^2} \hat{\mathbf{r}} \quad \vec{F}_{\rm E} = q\vec{E} \quad E_{\rm line} = \frac{2k|\lambda|}{r} = \frac{2K|Q|}{Lr} \quad E_{\rm plane} = \frac{|\sigma|}{2\epsilon_0} = \frac{|Q|}{2A\epsilon_0} \quad \vec{E}_{\rm cap} = \left(\frac{Q}{\epsilon_0 A}, \text{pos} \to \text{neg}\right)$ $\frac{mv^2}{2} + U_{\rm el}(s) = \frac{mv_0^2}{2} + U_{\rm el}(s_0), \ (U \equiv PE_{\rm el}) \quad U_{\rm el} = qEx \text{ for } \vec{E} = -E \hat{i} \quad V_{\rm el} = U_{\rm el}/q \quad E_x = -\frac{dV_{\rm el}}{dx}$ point charge: $V_{\rm el} = \frac{kQ}{r}$ $Q = C\Delta V_C$ farad $= F = \frac{C}{V}$ $C = \frac{\epsilon_0 A}{d}$ $\epsilon_0 = 8.85 \times 10^{-12} \frac{C^2}{Nm^2}$ parallel C_1, C_2 : $C_{eq} = C_1 + C_2$ series C_1, C_2 : $C_{eq}^{-1} = C_1^{-1} + C_2^{-1}$ resistance vs resisitivity: $R = \rho \frac{L}{A}$ (L = length, A = cross section); copper: $\rho = 1.7 \times 10^{-8} \Omega m$ $\Delta V_{\text{loop}} = \sum_i \Delta V_i = 0$ $\sum I_{\text{in}} = \sum I_{\text{out}}$ $P = \Delta VI$ watt = W = VA $P_R = \Delta V_R I = I^2 R$ $\tau = RC \qquad Q(t) = Q_0 e^{-t/\tau} \qquad I(t) = -\frac{dQ}{dt} = \frac{\Delta V_0}{R} e^{-t/\tau}$ $\vec{B} = \frac{\mu_0}{4\pi} \frac{q\vec{v} \times \vec{r}}{r^3} = \frac{\mu_0}{4\pi} \frac{I\Delta \vec{s} \times \vec{r}}{r^3} \qquad B_{\text{wire}} = \frac{\mu_0}{2\pi} \frac{I}{d} \text{ (use RH rule)} \qquad \frac{\mu_0}{4\pi} = 10^{-7} \frac{\text{Tm}}{\text{A}} \qquad \text{tesla} = \text{T} = \frac{\text{N}}{\text{Am}}$ short coil, R >> L (N turns): $B_{\text{coil,centre}} = \frac{\mu_0 NI}{2R}$ solenoid, L >> R: $B_{\text{sol,inside}} = \frac{\mu_0 NI}{L}$ mag dipole: $\vec{\mu} = (AI, \text{from south to north})$ $\vec{B}_{dip} = \frac{\mu_0}{4\pi} \frac{2\vec{\mu}}{r^3}$ on axis, far away $\vec{F}_{onq} = q\vec{v} \times \vec{B}$ force on current \perp to \vec{B} : $F_{wire} = ILB$ force betw. parallel wires: $F_{2\text{wires}} = \frac{\mu_0 L I_1 I_2}{2\pi d}$ torque on mag dipole: $\vec{\mu}$ in \vec{B} : $\vec{\tau} = \vec{\mu} \times \vec{B}$ bar (length L) moves w. $\vec{v} \perp \vec{B}$ gen. EMF: $\varepsilon = vLB$; $\Phi_m = \vec{A} \cdot \vec{B} \quad \Phi_m = AB \cos \theta \quad \varepsilon = \left| \frac{d\Phi_m}{dt} \right| = \left| \vec{B} \cdot \frac{d\vec{A}}{dt} + \vec{A} \cdot \frac{d\vec{B}}{dt} \right|$