

LAST NAME:

STUDENT NR:

PHYS 1010 6.0: CLASS TEST 6

Time: 50 minutes; Calculators & formulae provided at the end = only aid; Total = 20 points.

1) A current loop with a resistance $R = 250 \Omega$ and an area $A = 0.4 \text{ m}^2$ is oriented perpendicular to a magnetic field that varies in time according to $B(t) = 0.5t(1-t)$ (t and B are in SI units). What is the current induced in the loop at $t = 0$ s, at $t = 0.5$ s, and at $t = 1$ s?

Faraday: $\mathcal{E} = -\frac{d\Phi_M}{dt} = -\frac{d}{dt} (B(t)A)$ (orientation doesn't change) ①

$$= -A \frac{dB}{dt} = -A \left(\frac{1}{2}(1-t) + \frac{1}{2}t(-1) \right)$$
$$\mathcal{E} = -\frac{A}{2} (1-2t) \quad (\text{Volts; in SI}) \quad \text{①}$$

Ohm's law: $I = \frac{\mathcal{E}}{R} = \frac{2t-1}{500} 0.4 = (2t-1) 0.8 \times 10^{-3}$ ① (A; in SI)

(orientation from lenz, not required here)

- a) $t = 0$: -0.8 mA
- b) $t = 0.5 \text{ s}$: 0 mA
- c) $t = 1.0 \text{ s}$: $+0.8 \text{ mA}$


} absolute sign doesn't matter, but a) relative to b) does, i.e., direction reversal!

① for values

① for relative sign



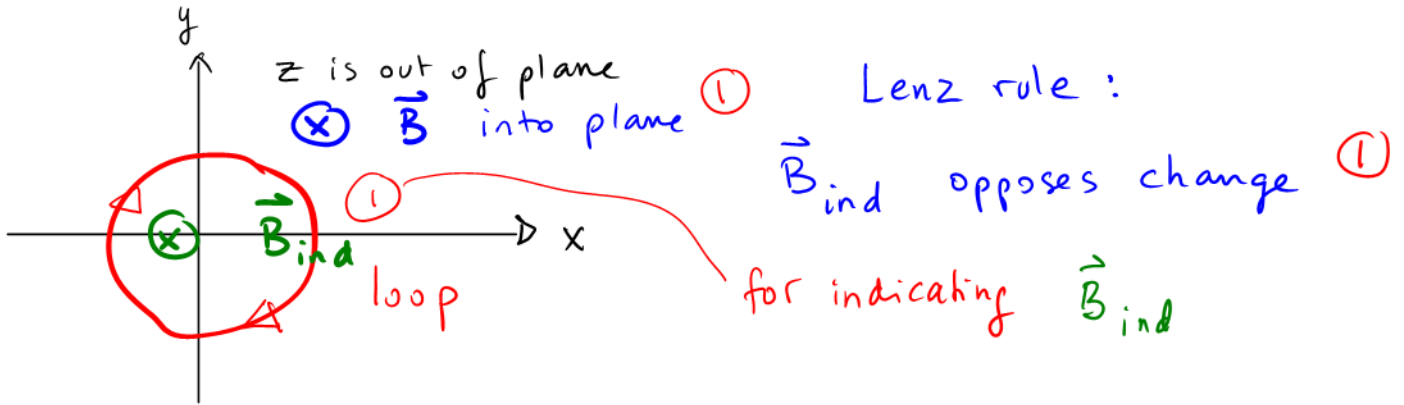2) A circular loop of wire lies in the $x - y$ plane so that the axis of the loop lies along z . A homogeneous (spatially uniform) magnetic field $B(t)$ is anti-parallel to the z -axis. ($B_z(t) < 0$, $B_x = B_y = 0$). If $B(t)$ is decreasing with time, what is the direction of the induced current when viewed from above? Start with a drawing, and explain your steps and reasoning!




Since $\vec{B} = (0, 0, B_z(t))$ is pointing into the plane, but is decreasing, \vec{B}_{ind} points into the plane

RH rule:

The direction of the current is CW (as viewed from above)

real

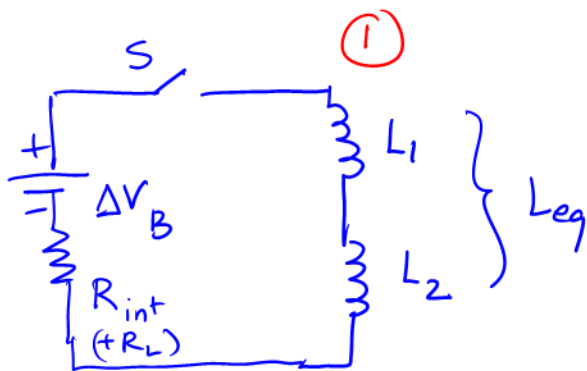3) Two inductors L_1 and L_2 are connected in series to form an equivalent inductor L_{eq} . Together they are connected to a battery of voltage ΔV_B via a switch. Draw a circuit diagram depicting the situation. Formulate Kirchhoff's loop law for the circuit. Derive how L_{eq} depends on L_1 and L_2 .



$$\Delta V_B - RI - L_1 \frac{dI}{dt} - L_2 \frac{dI}{dt} = 0$$

$\rightarrow R_{int} + R_L + R_{wire}$


The same current passes through L_1 and $L_2 \Rightarrow$ the same

$\frac{dI}{dt}$ acts in both

(We should add R for the ohmic resistance in series in a realistic setting)

The least we need is R_{int} from the battery!

Equivalent circuit:

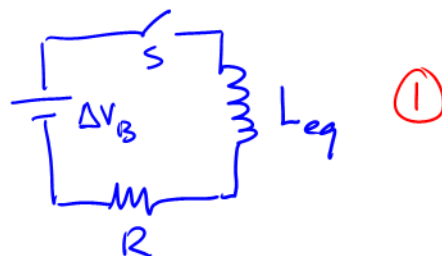

(can be shown as part of original circuit)

$$\left. \begin{array}{l} \dots \quad \Delta V_B - RI - L_1 \frac{dI}{dt} - L_2 \frac{dI}{dt} = 0 \\ \text{vs} \quad \Delta V_B - RI - L_{eq} \frac{dI}{dt} = 0 \end{array} \right\}$$

$$L_{eq} = (L_1 + L_2) \quad (1)$$

4a) Consider a simple LC circuit (L and C in parallel) with values $C = 1500 \text{ pF}$ and $L = 20 \text{ mH}$. At $t = 0$ the current is $I = 45 \text{ mA}$ and the charge on C is zero. Calculate the energy stored in the inductor at this time. At which time t_1 will the current be zero (first occurrence after $t = 0$). What is the charge in C at this time? Provide an accurate sketch of the charge as a function of time for two complete cycles.



$$I_0 = 45 \times 10^{-3} \text{ A}$$


$$C = 1.5 \times 10^3 \times 10^{-12} \text{ F}$$

$$L = 2 \times 10^{-2} \text{ H}$$

$$PE_L = \frac{1}{2} L I^2 = 10^{-2} \times 45^2 \times 10^{-6} \text{ J (inst)}$$

$$= 2.025 \times 10^3 \times 10^{-8} \text{ J}$$
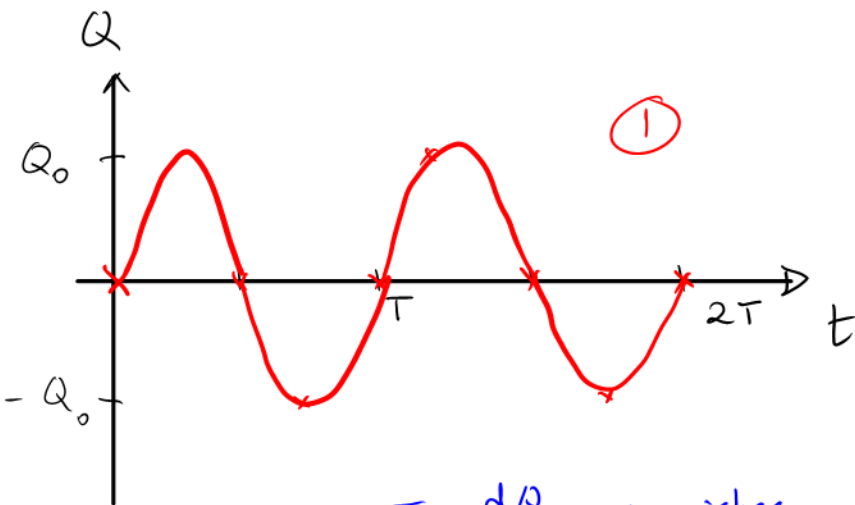
$$= 2.0 \times 10^{-5} \text{ J} \quad (0.5)$$



Current $I = \frac{dQ}{dt}$ vanishes when $t = T/4, 3T/4, \dots$ (0.5)

$$t_1 = 8.6 \mu\text{s} \quad (0.5)$$

Period of oscillation:

$$\omega = \frac{1}{\sqrt{LC}} = \frac{2\pi}{T}$$

$$T = 2\pi \sqrt{LC} = 6.28 \times \sqrt{1.5 \times 10^{-9} \times 0.02} \text{ s}$$

$$= 0.344 \text{ E-4} = 3.4 \times 10^{-5} \text{ s}$$

$$= 34 \mu\text{s} \quad (0.5)$$

Energy conservation: $\frac{C}{2} \Delta V^2 = \frac{L}{2} I^2$

$$\Delta V_C = \frac{Q}{C} \quad \therefore \frac{Q^2}{C} = LI^2 \quad \therefore Q = \sqrt{LC} I = \sqrt{3.0 \times 10^{-11}} \times 0.045 = 25 \text{ nC} \quad (0.5)$$

4b) The LC circuit of question 4 has the inductor replaced by a $L = 20 \mu\text{H}$ coil. What is the wavelength of the radiowaves that this circuit will catch on resonance?

$$\omega = \frac{1}{\sqrt{LC}} = 2\pi f \quad f = \frac{1}{2\pi\sqrt{LC}} = 0.92 \times 10^6 \text{ Hz}$$

$$\lambda f = c \quad \therefore \lambda = \frac{c}{f} = \frac{3.0 \times 10^8 \text{ m/s}}{0.92 \times 10^6 \text{ Hz}} = 326 \text{ m} \approx 330 \text{ m. } \textcircled{1}$$

FORMULA SHEET

$$v(t_f) = v(t_i) + \int_{t_i}^{t_f} a(t) dt \quad s(t_f) = s(t_i) + \int_{t_i}^{t_f} v(t) dt$$

$$v_f = v_i + a\Delta t \quad s_f = s_i + v_i\Delta t + \frac{1}{2}a\Delta t^2 \quad v_f^2 = v_i^2 + 2a\Delta s \quad g = 9.8 \text{ m/s}^2$$

$$f(t) = t \quad \frac{df}{dt} = 1 \quad F(t) = \int f(t) dt = \frac{t^2}{2} + C$$

$$f(t) = a \quad \frac{df}{dt} = 0 \quad F(t) = \int f(t) dt = at + C \quad F(t) = \text{anti-derivative} = \text{indefinite integral}$$

area under the curve $f(t)$ between limits t_1 and t_2 : $F(t_2) - F(t_1)$

$$x^2 + px + q = 0 \text{ factored by: } x_{1,2} = -\frac{p}{2} \pm \sqrt{\frac{p^2}{4} - q}$$

$$\text{uniform circular m. } \vec{r}(t) = R(\cos \omega t \hat{i} + \sin \omega t \hat{j}); \quad \vec{v}(t) = \frac{d\vec{r}}{dt} = \dots; \quad \vec{a}(t) = \frac{d\vec{v}}{dt} = \dots$$

$$\exp' = \exp; \quad \sin' = \cos; \quad \cos' = -\sin. \quad \frac{d}{dx}[f(g(x))] = \frac{df}{dg} \frac{dg}{dx}; \quad (fg)' = f'g + fg'$$

$$m\vec{a} = \vec{F}_{\text{net}}; \quad F_G = \frac{Gm_1m_2}{r^2}; \quad g = \frac{GM_E}{R_E^2}; \quad R_E = 6370 \text{ km}; \quad G = 6.67 \times 10^{-11} \frac{\text{Nm}^2}{\text{kg}^2}; \quad M_E = 6.0 \times 10^{24} \text{ kg}$$

$$f_s \leq \mu_s n; \quad f_k = \mu_k n; \quad f_r = \mu_r n; \quad \mu_r \ll \mu_k < \mu_s. \quad F_H = -k\Delta x = -k(x - x_0).$$

$$\vec{F}_d \sim -\vec{v}; \text{ linear: } F_d = dv; \text{ quadratic: } F_d = 0.5\rho A v^2; \quad A = \text{cross sectional area}$$

$$W = F\Delta x = F(\Delta r) \cos \theta. \quad W = \text{area under } F_x(x). \quad PE_H = \frac{k}{2}(\Delta x)^2; \quad PE_g = mg\Delta y.$$

$$\Delta \vec{p} = \vec{J} = \int \vec{F}(t) dt; \quad \Delta p_x = J_x = \text{area under } F_x(t) = F_x^{\text{avg}} \Delta t; \quad \vec{p} = m\vec{v}; \quad K = \frac{m}{2}v^2$$

$$\Delta \vec{p}_1 + \Delta \vec{p}_2 = 0; \quad K_1^{\text{in}} + K_2^{\text{in}} = K_1^{\text{fin}} + K_2^{\text{fin}} \text{ for elastic collisions.} \quad \vec{a}_{\text{CM}} = \frac{m_1\vec{a}_1 + m_2\vec{a}_2}{m_1 + m_2}$$

$$\vec{\tau} = \vec{r} \times \vec{F}; \quad \tau_z = rF \sin(\alpha) \text{ for } \vec{r}, \vec{F} \text{ in } xy \text{ plane.} \quad I = \sum_i m_i r_i^2; \quad I\alpha_z = \tau_z; \quad (\hat{k} = \text{rot. axis})$$

$$K_{\text{rot}} = \frac{1}{2}I\omega^2; \quad L_z = I\omega_z; \quad \frac{d}{dt}L_z = \tau_z; \quad \vec{L} = \vec{r} \times \vec{p}; \quad \frac{d}{dt}\vec{L} = \vec{\tau}$$

$$x(t) = A \cos(\omega t + \phi); \quad \omega = \frac{2\pi}{T} = 2\pi f; \quad v_x(t) = \dots; \quad v_{\text{max}} = \dots$$

$$m_e = 9.11 \times 10^{-31} \text{ kg} \quad m_p = 1.67 \times 10^{-27} \text{ kg} \quad e = 1.60 \times 10^{-19} \text{ C} \quad K = \frac{1}{4\pi\epsilon_0} = 9.0 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}$$

$$\vec{F}_C = \frac{Kq_1q_2}{r^2} \hat{r} \quad \vec{F}_E = q\vec{E} \quad E_{\text{line}} = \frac{2K|\lambda|}{r} = \frac{2K|Q|}{Lr} \quad E_{\text{plane}} = \frac{|\eta|}{2\epsilon_0} = \frac{|Q|}{2A\epsilon_0} \quad \vec{E}_{\text{cap}} = \left(\frac{Q}{\epsilon_0 A}, \text{ pos} \rightarrow \text{neg} \right)$$

$$\frac{mv^2}{2} + U_{\text{el}}(s) = \frac{mv_0^2}{2} + U_{\text{el}}(s_0), \quad (U \equiv PE_{\text{el}}) \quad U_{\text{el}} = qEx \text{ for } \vec{E} = -E \hat{i} \quad V_{\text{el}} = U_{\text{el}}/q \quad E_x = -\frac{dV_{\text{el}}}{dx}$$

$$\begin{aligned}
Q &= C\Delta V_C \quad \text{farad} = \text{F} = \frac{\text{C}}{\text{V}} \quad C = \frac{\epsilon_0 A}{d} \quad \epsilon_0 = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}^2} \quad \text{PE}_C = \frac{C}{2} \Delta V_C^2 \\
\text{parallel } C_1, C_2: C_{\text{eq}} &= C_1 + C_2 \quad \text{series } C_1, C_2: C_{\text{eq}}^{-1} = C_1^{-1} + C_2^{-1} \\
\Delta V_{\text{loop}} &= \sum_i \Delta V_i = 0 \quad \sum I_{\text{in}} = \sum I_{\text{out}} \\
P &= \Delta VI \quad \text{watt} = \text{W} = \text{VA} \quad P_R = \Delta V_R I = I^2 R \\
\tau &= RC \quad Q(t) = Q_0 e^{-t/\tau} \quad I(t) = -\frac{dQ}{dt} = \frac{\Delta V_0}{R} e^{-t/\tau} \\
\vec{B} &= \frac{\mu_0}{4\pi} \frac{q\vec{v} \times \vec{r}}{r^3} = \frac{\mu_0}{4\pi} \frac{I\Delta\vec{s} \times \vec{r}}{r^3} \quad B_{\text{wire}} = \frac{\mu_0 I}{2\pi d} \quad (\text{use RH rule}) \quad \frac{\mu_0}{4\pi} = 10^{-7} \frac{\text{Tm}}{\text{A}} \quad \text{tesla} = \text{T} = \frac{\text{N}}{\text{Am}} \\
\text{short coil, } R \gg L \text{ (} N \text{ turns): } B_{\text{coil,centre}} &= \frac{\mu_0 NI}{2R} \quad \text{solenoid, } L \gg R: B_{\text{sol,inside}} = \frac{\mu_0 NI}{L} \\
\text{mag dipole: } \vec{\mu} &= (AI, \text{ from south to north}) \quad \vec{B}_{\text{dip}} = \frac{\mu_0}{4\pi} \frac{2\vec{\mu}}{z^3} \text{ on axis, far away} \\
\vec{F}_{\text{onq}} &= q\vec{v} \times \vec{B} \quad \text{force on current } \perp \text{ to } \vec{B}: F_{\text{wire}} = ILB \\
\text{force betw. parallel wires: } F_{2\text{wires}} &= \frac{\mu_0 I_1 I_2}{2\pi d} \quad \text{torque on mag dipole: } \vec{\mu} \text{ in } \vec{B}: \vec{\tau} = \vec{\mu} \times \vec{B} \\
\text{bar (length } L) \text{ moves w. } \vec{v} \perp \vec{B} \text{ gen. EMF: } \varepsilon &= vLB ; \\
\Phi_m &= \vec{A} \cdot \vec{B} \quad \Phi_m = AB \cos \theta \quad \varepsilon = \left| \frac{d\Phi_m}{dt} \right| = \left| \vec{B} \cdot \frac{d\vec{A}}{dt} + \vec{A} \cdot \frac{d\vec{B}}{dt} \right| \\
L &= \frac{\Phi_m}{I} \quad \text{henry} = \text{H} = \frac{\text{Tm}^2}{\text{A}} \quad \varepsilon_{\text{coil}} = L \left| \frac{dI}{dt} \right| \quad \Delta V_L = -L \frac{dI}{dt} \quad \text{PE}_L = \frac{1}{2} I^2 L \\
\text{series L and R: } \tau &= \frac{L}{R} \quad I(t) = I_0 e^{-t/\tau} ; \text{ parallel L and C: } \omega = \sqrt{\frac{1}{LC}} \quad I(t) = \omega Q_0 \sin \omega t \\
\lambda f &= v_w \quad \text{sinusoid travelling in pos dir'n: } D(x, t) = A \sin(2\pi(\frac{x}{\lambda} - \frac{t}{T}) + \phi_0) = A \sin(kx - \omega t + \phi_0) \\
\text{transverse wave on a string: } v_w &= \sqrt{\frac{T}{\mu}} \text{ where } T \text{ is tension, } \mu = M/L \\
\omega &= v_w k \quad v_{\text{sound}} = 343 \text{m/s in air at } T = 20^\circ\text{C} \quad \text{in water: } v_{\text{sound}} = 1480 \text{m/s} \\
\text{light in vac.: } v_w &= c = 3.00 \times 10^8 \text{m/s} \quad \text{visible: } \lambda = 400 \text{nm (blue/UV); } \lambda = 700 \text{nm (red/IR)} \\
\text{refraction: } n_{\text{glass}} &= 1.5; n_{\text{water}} = 1.333; \text{ light in medium: } c/n; \text{ wavelength: } \lambda_{\text{vac}}/n \\
\text{approaching source (speed } v_s) &: f_+ = \frac{f_0}{1 - v_s/v_w} \quad \text{receding: } f_- = \frac{f_0}{1 + v_s/v_w} \\
\sin(\alpha \pm \beta) &= \sin \alpha \cos \beta \pm \cos \alpha \sin \beta \quad \sin \alpha + \sin \beta = 2 \cos \frac{\alpha - \beta}{2} \sin \frac{\alpha + \beta}{2} \\
\text{transverse standing wave, string length } L &: \lambda_n = \frac{2L}{n} \quad n = 1, 2, \dots \quad f_n \text{ from } \lambda_n f_n = c_w
\end{aligned}$$